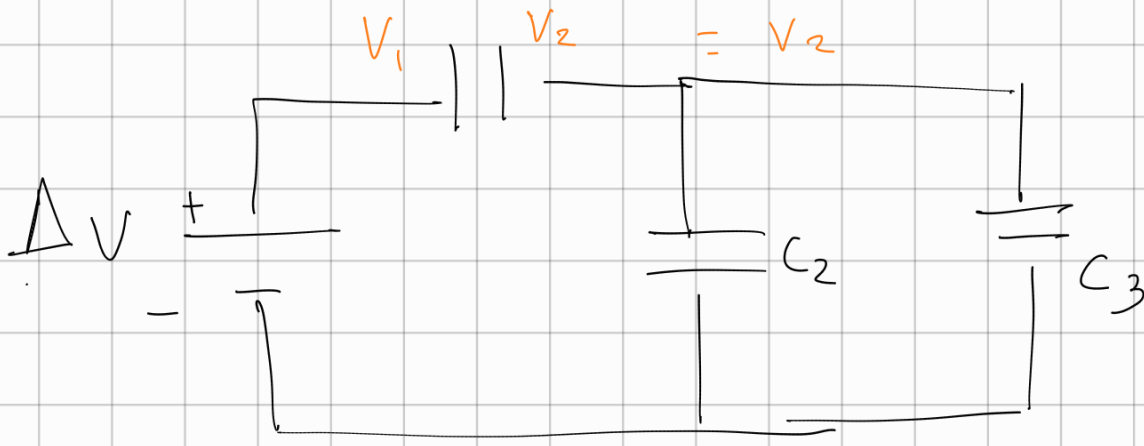


ES. 1



$$C_1 = 3C \quad C_2 = C \quad C_3 = 5C$$

1) Ceq

2) Ordinano i condensatori in
ordine crescente di carica

3) u u Skalar- & Tensor


4) Cosa succede se si apre C?


$$C = \frac{Q}{\Delta V}$$

$$C_{eq}^{2,3} = C_2 + C_3 = 6C$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_{eq}^{2,3}}} = \frac{1}{\frac{1}{3} + \frac{1}{6}} =$$
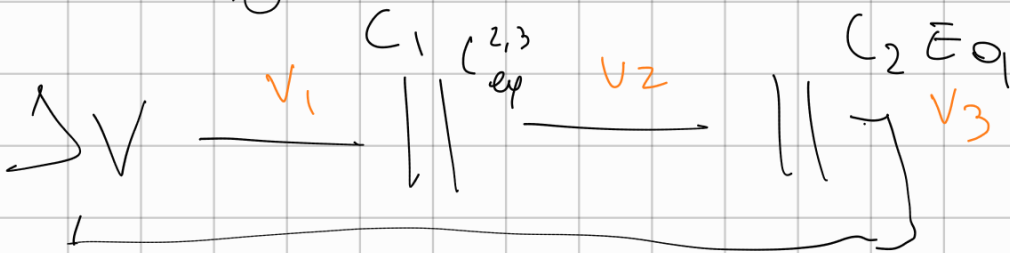
$$11 \quad \frac{2+1}{6} = 2 \quad 11 \quad > \quad C_{eq} = 2 \quad C$$



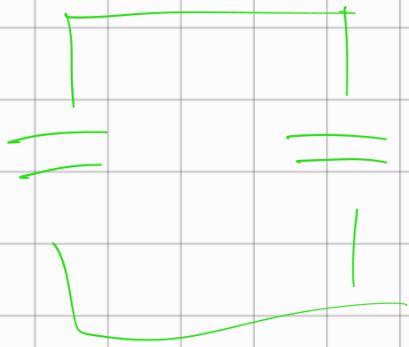

$$C = \frac{Q}{\Delta V}$$

$$Q = C \Delta V_{32}$$

$$= (V_3 - V_2)$$

$$C = (C_2 + C_3)$$

$$Q_2 + Q_3 = \underset{\substack{'' \\ C}}{C_2} + \underset{\substack{'' \\ C_3}}{C_3} (V_3 - V_2)$$


$$\frac{Q_2 + Q_3}{\Delta V} = 6C$$

$$\frac{Q_2}{\Delta V} = C < \frac{Q_3}{\Delta V} = 5C$$

$$V_e - V_1 = \frac{Q}{6C} + V_e$$



$$C_{2eq} = C_2 + C_3$$

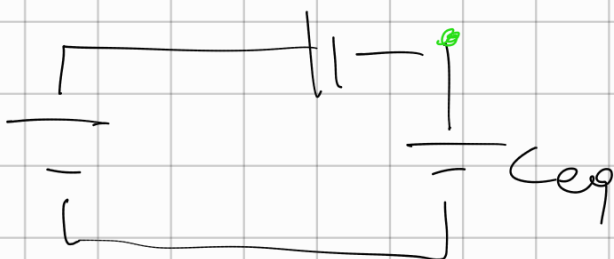

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_{2eq}} = .2C$$



$$Q_1 = Q_2 + Q_3$$

$$Q_1 = 3C \Delta V$$

$$\Delta V_1 = \frac{Q_1}{3C} = \frac{2C \Delta V}{3C}$$

$$\Delta V_2 = \Delta V - \Delta V_1 = \Delta V - \frac{2}{3} \Delta V = \frac{1}{3} \Delta V$$

$$Q_2 = \Delta V_2 \cdot C$$

$$Q_3 = \Delta V_2 \cdot 5C$$

$$Q_2 = \frac{Q_3}{5}$$

$$\Rightarrow 5Q_2 = Q_3$$

$$Q_1 = Q_2 + 5Q_2 = 6Q_2$$

$$C_3 = \alpha C \Rightarrow 5$$


Se aumenta Q_3

$$Q_2 = \frac{Q_3}{\alpha}$$

$$Q_1 = \frac{Q_3}{\alpha} + Q = \frac{(\alpha+1)Q_3}{\alpha}$$

Se aumenta α , aumenta Q_1

ES

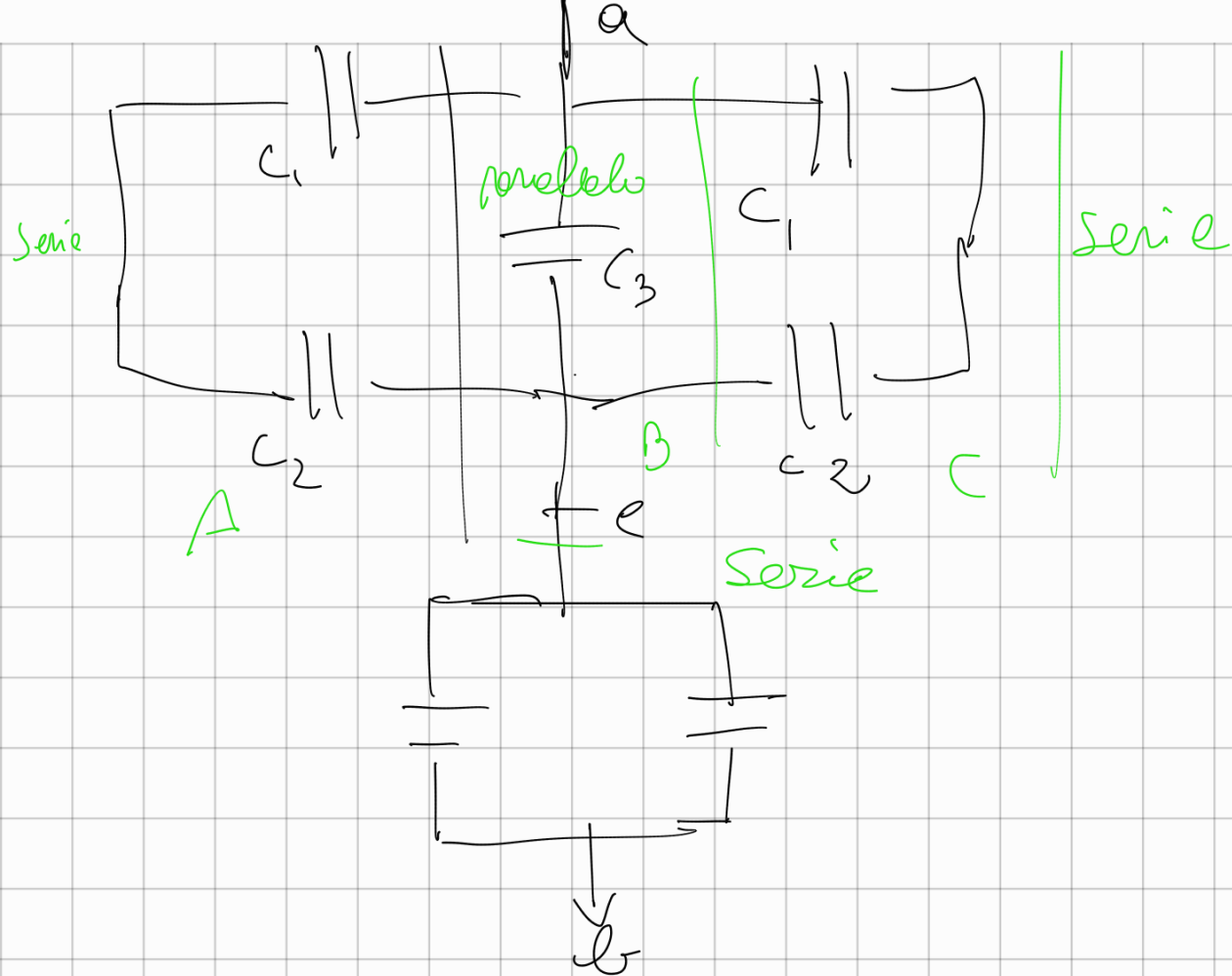

1) C_{eq} Q_3 se $\Delta V_{a-b} = 60V$

$$C_{eq}^A = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{1}{\frac{1}{5 \cdot 10^{-6}} + \frac{1}{10 \cdot 10^{-6}}} = \frac{1}{\frac{2+1}{10 \cdot 10^{-6}}} = \frac{10}{3} \mu F$$

$$C_{eq}^B = \frac{1}{\frac{3}{10} + \frac{1}{2}} = \frac{1}{\frac{3+5}{10}} = \frac{5}{4} \mu F$$

$$C_{eq}^C = \frac{1}{\frac{4}{5} + \frac{3}{10}} = \frac{8+3}{10} = \frac{11}{10} \mu F$$

$$= C_{eq}^{ABC} + C_{eq}^B \quad 20 \mu F$$

$$\frac{1}{\frac{1}{19} + \frac{19}{20}} =$$

$$C_{eq}^A = C_{eq}^C = \frac{20}{3} \mu F$$

$$C_{eq}^B = C_{eq}^A + C_{eq}^B + C_3 = 8,66 \mu F$$

$$C_{eq} = \frac{1}{\frac{1}{C_{eq}^B} + \frac{1}{C_3}} = 8,66 \mu F$$

$$Q = \Delta V C_{eq} = 363 \mu C$$

$$\Delta V_{Ac} = \frac{Q}{C_{eq}} = 41,2 V$$


$$\Delta V_{Ac} \cdot C_3 = 83,8 \mu C = Q_3$$

Es. 3

STato iniziale



STato finale

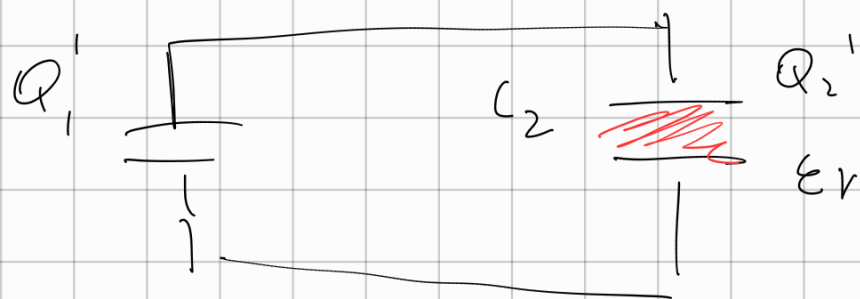

$$\epsilon_r = 3$$

$$Q = Q_1 + Q_2 = 2 \mu C$$

$$C_1 = 1 \mu F$$

$$C_2 = 2 \mu F$$

1) Calcolare Q_1' e Q_2'

$$2) \Delta U = U_{fin} - U_{in}$$

$$C_2' = \epsilon_r C_2$$

$$C_{eq} = C_1 + C_2 = 3 \mu F$$

$$C_1 + C_2 = \frac{Q_1 + Q_2}{V_2 - V_1} = \frac{2 \mu C}{\Delta V} = 3 \mu F$$

$$\frac{2 \mu C}{3 \mu F} = \Delta V = \frac{2}{3} V$$

$$(C_1 + \epsilon_r C_2) = \frac{Q_1' + Q_2'}{\Delta V}$$

$$7 \mu F = \frac{2 \mu C}{\Delta V} \Rightarrow \Delta V = \frac{2}{7} V$$

$$C_{eq} = C_1 \parallel C_2'$$

$$\Delta V_f = \frac{Q}{C_1'} = \frac{Q}{C_1 + \epsilon_r C_2}$$

$$Q_1' = C_1 \Delta V_f = \frac{C_1 Q}{C_1 + \epsilon_r C_2} = 0,29 \mu C$$

$$Q_2' = C_2' \Delta V_h = \frac{\epsilon_v C_2 Q}{C_1 + \epsilon_v C_2} \quad : 1, 2, \text{nc}$$

$$U_M = \frac{1}{2} \frac{Q^2}{C_M} = \frac{1}{2} \frac{Q^2}{(C_1 + C_2)}$$

$$U_{\text{fin}} = \frac{1}{2} \frac{Q^2}{C''} = \frac{1}{2} \frac{Q^2}{(C_1 + \epsilon_v C_2)}$$

$$\Delta U = -3,8 \cdot 10^{-9} \text{ J}$$