
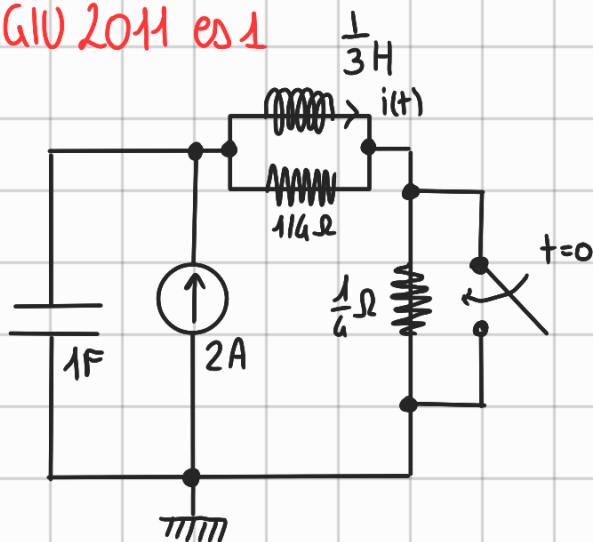



27 GIU 2011 es 1

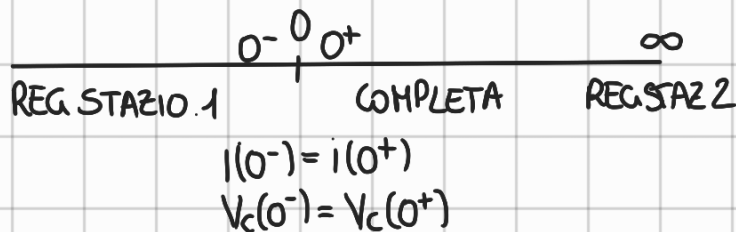


Determina $i(t)$ risposta completa $t \geq 0$



$t = 0^-$


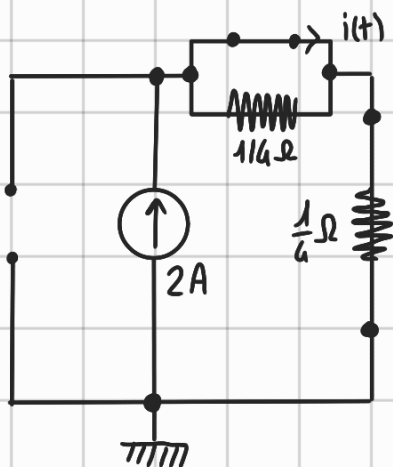


quindi $i(0^-) = 2A = i(0^+)$

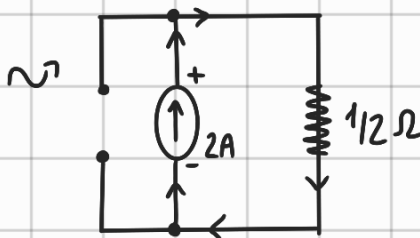

$V_C(0^-) = 0$

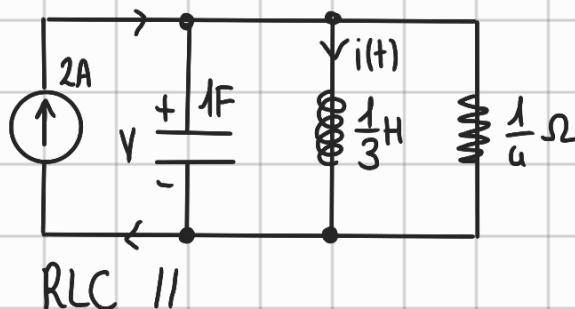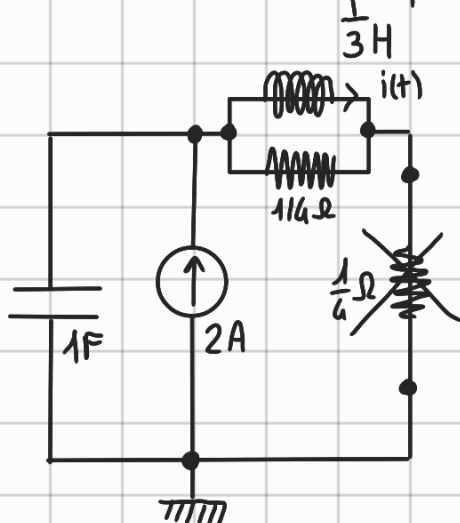trovate le variabili di stato, passo a $t = \infty$



$$d_p = \frac{G_p}{2C} = \frac{4}{2} = 2$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1/3}} = \sqrt{3}$$

$\sim d_p > \omega_0$ caso sovrasmorzato



radici $S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -2 \pm \sqrt{4 - 3} = -2 \pm 1 = \begin{matrix} \nearrow -1 \\ \searrow -3 \end{matrix}$

$$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t} = k_1 e^{-t} + k_2 e^{-3t}$$

$$C = T_C + \text{regime 2} \quad \downarrow = 2A$$

$$i(t) = k_1 e^{-t} + k_2 e^{-3t} + 2$$

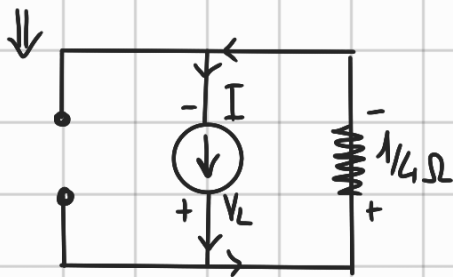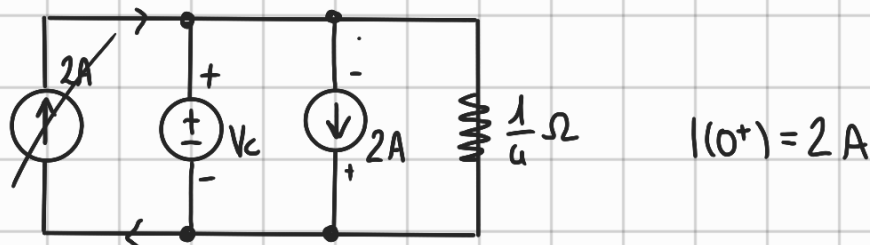Ora devo trovare k_1 e k_2 , $\Rightarrow$ studio a 0^+



$$V_L(0^+) = L \frac{di(0^+)}{dt}$$


$$V_L = \frac{1}{4} \cdot 2 \quad \frac{1}{3} \frac{di(0^+)}{dt} = \frac{1}{2}$$

$$\Rightarrow \begin{cases} i(t) = k_1 e^{-t} + k_2 e^{-3t} + 2 \\ i(0^+) = 2 \\ \frac{di(0^+)}{dt} = 3/2 \end{cases}$$

$$\begin{cases} 2 = k_1 + k_2 + 2 \\ 3/2 = -k_1 - 3k_2 \end{cases} \quad \begin{cases} k_1 = -k_2 = 3/4 \\ 3/2 = k_2 - 3k_2 \Rightarrow k_2 = -3/4 \end{cases}$$

$$\Rightarrow i(t) = +\frac{3}{4} e^{-t} - \frac{3}{4} e^{-3t} + 2$$

ES 1.

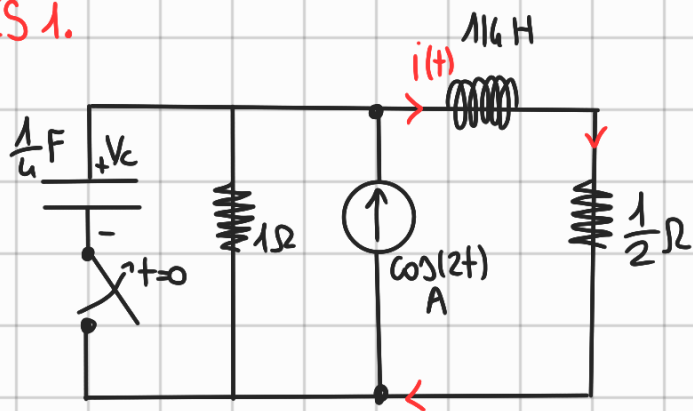


Determinare $i(t)$ completa


REGIME SIN 1 0⁻ 0 0⁺ COMPLETA REG SIN 2 ∞

$$i_L(0^-) = i_L(0^+) \\ V_C(0^-) = V_C(0^+)$$

t = 0⁻

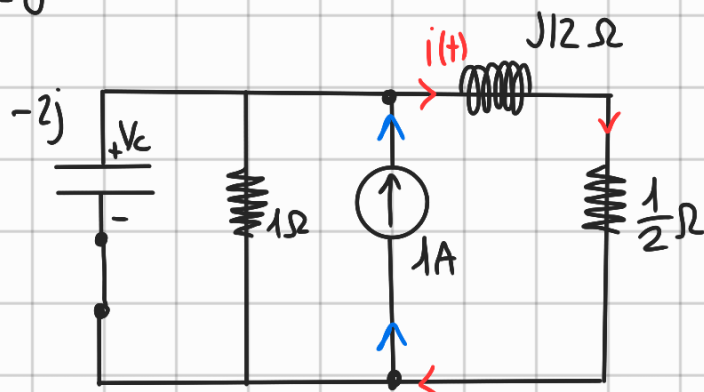

semplifico

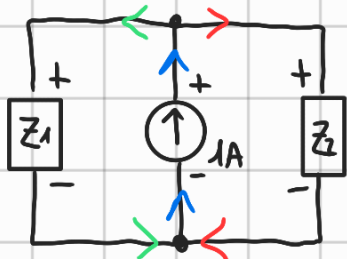

$$KI \Rightarrow \begin{cases} 1 = i(0^-) + i_1 \\ Z_2 i(0^-) - V_g = 0 \\ V_g = Z_1 i_1 \end{cases}$$

$$Z_1 = \frac{4-2j}{5} \quad Z_2 = \frac{1+j}{2}$$

$$i(0^-) = \frac{\frac{1}{Z_2}}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{2}{1+j} \cdot \frac{1}{\frac{5}{4-2j} + \frac{2}{1+j}} = \frac{10}{17} - \frac{6j}{17}$$






$$i(t) = \text{Re}[\bar{I}]$$

$$i(0^-) = \frac{10}{17}$$

$$\tau = \frac{L}{R} = \frac{1/4}{\frac{1}{2} + 1} = \frac{1}{6}$$

$$i(t) = \frac{10}{17} e^{-6t} \text{ A}$$

$$t = \infty$$

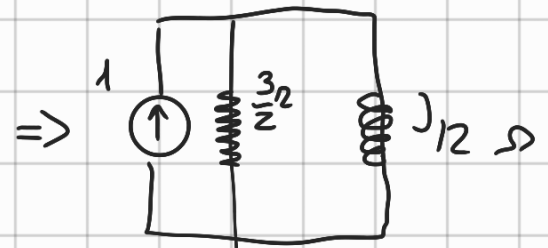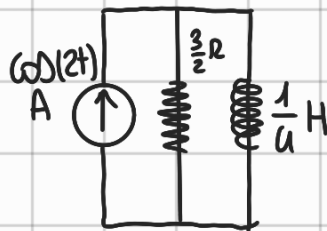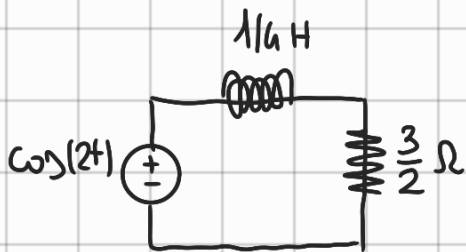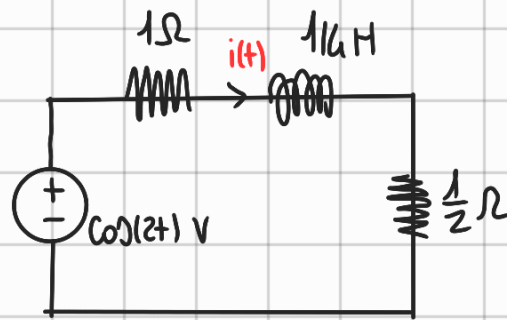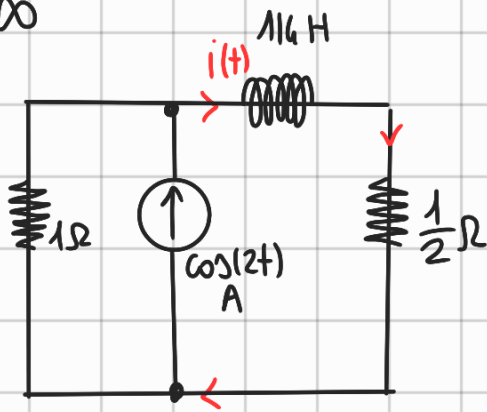


$$V = RI =$$

$$i(t) = - \frac{1}{\sqrt{\left(\frac{3}{2}\right)^2 + 2^2 \left(\frac{1}{4}\right)^2}} \cos\left(\arctan\left(\frac{2 \cdot \frac{1}{4}}{\frac{3}{2}}\right)\right) e^{-t \frac{3}{8} \cdot 2} + \frac{1}{\sqrt{\left(\frac{3}{2}\right)^2 + 2^2 \frac{1}{4^2}}} \cos\left(2t - \arctan\left(\frac{\omega L}{R}\right)\right)$$

$$= - \frac{2}{\sqrt{10}} 0,96 + \frac{2}{\sqrt{10}} \cos(2t + 18^\circ)$$

$$= -0,6 e^{-6t} + 0,632 \cos(2t + 18^\circ)$$


29 GIUGNO 2020 ED3

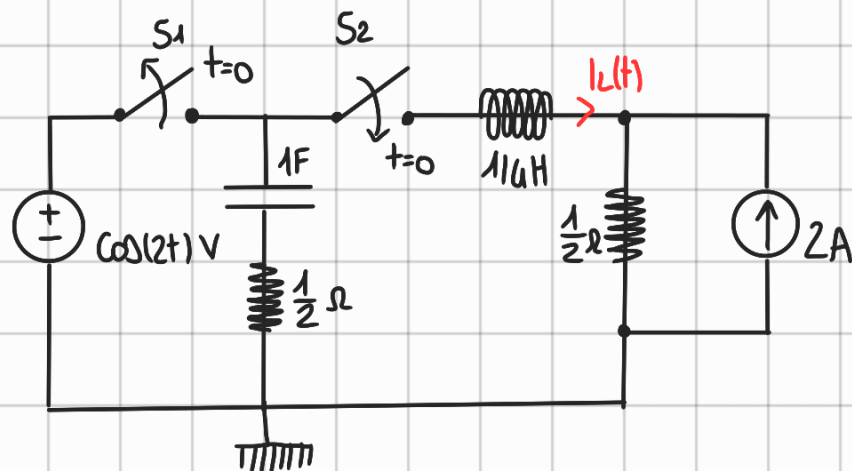

Determina $I_L(t)$


Faccio una semplificazione:

$$V = RI$$

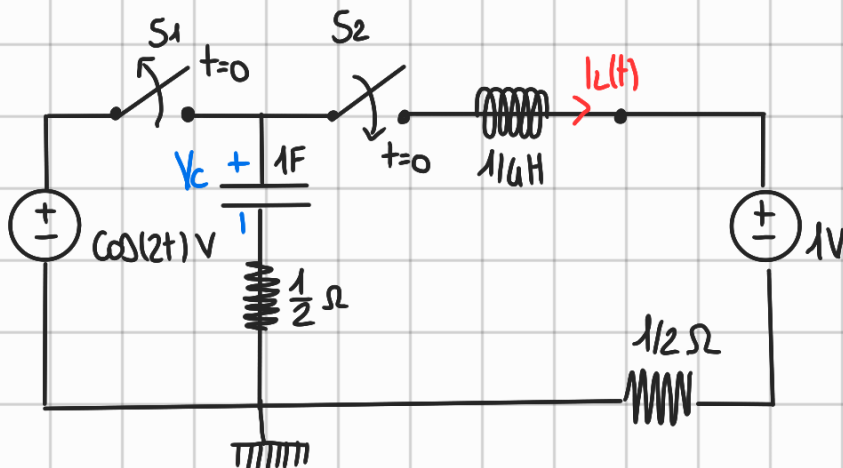

$0^- \quad 0 \quad 0^+$
 REGIME SINUSOIDALE COMPLETA REGIME STAZIONARIO
 $V(0^-) = V(0^+)$
 $I_L(0^-) = I_L(0^+)$

• Analisi a 0^-

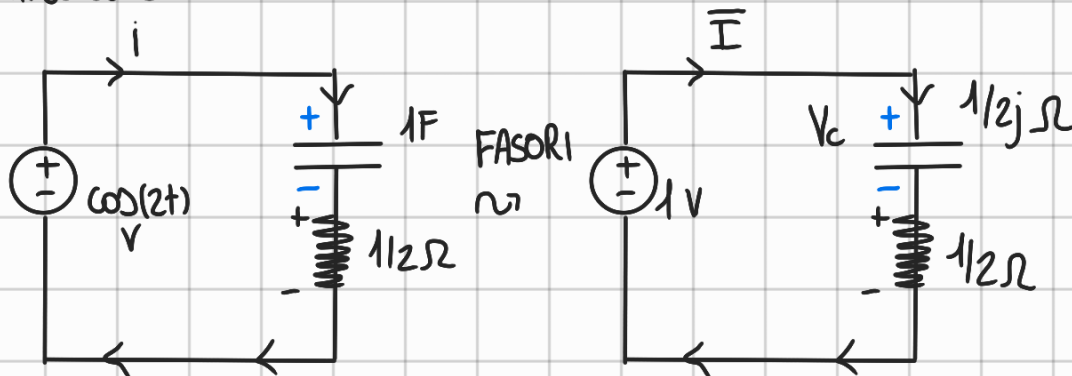

$$\text{trovo } \bar{I} = \frac{V}{Z} = \frac{1}{\frac{1}{j} + \frac{1}{2}} = \frac{2j(1-j)}{1+j(1-j)} = \frac{2j+2}{1+1} = 1+j \text{ A}$$

$$\text{KV: } V_C + V_R - V = 0$$



$$\Rightarrow V_C = V - V_R = 1 - \frac{1}{2}(1+j) = \frac{2-1-j}{2} = \frac{1-j}{2}$$

$$R_e = \frac{1}{2}$$

$$V_C(0^-) = \frac{1}{2} \text{ V} = V_C(0^+)$$

quindi $V_C(0^-) = V_C(0^+) = 1/2 \text{ V}$
 $I_L(0^-) = I_L(0^+) = 0 \text{ A}$

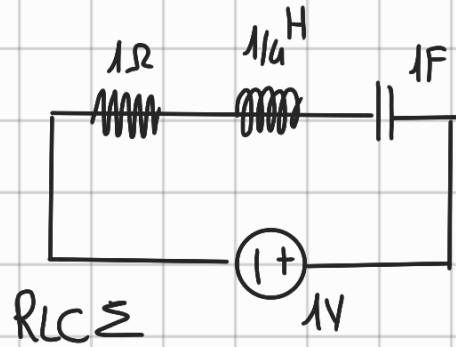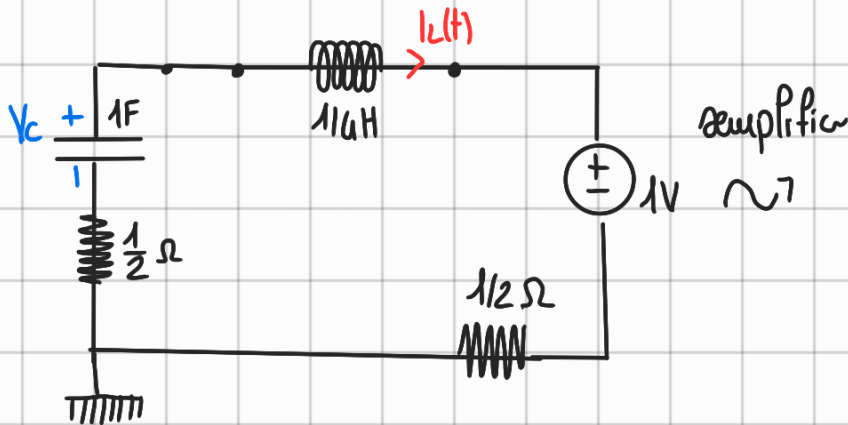Ora studio a $t = \infty$ ho un REGIME STAZIONARIO




$$\omega_0 = \frac{1}{\sqrt{LC}} = 2 \quad ds = \frac{R_s}{2L} = \frac{1}{2 \cdot \frac{1}{4}} = 2$$

$\omega_0 = ds$ CRITICAMENTE SMORZATO $S_{1,2} = -2$

$$I_L(t) = K_1 e^{-2t} + K_2 t e^{-2t} + 0$$

REGIME

Studio a 0^+

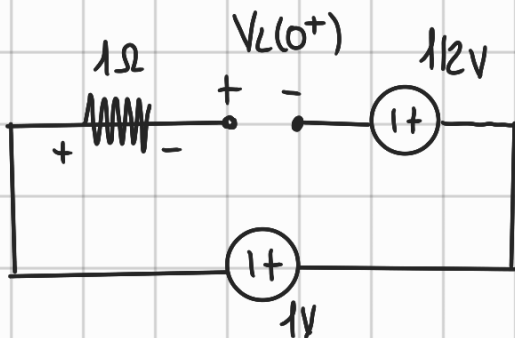

$$-1/2 + 1 + L \frac{d}{dt} I_L(t) =$$

$$\frac{1}{4} \frac{dI_L(t)}{dt} = \left(\frac{1}{2} - 1 \right) \cdot 4 = -2$$

$$\left\{ \begin{array}{l} I_L(t) = K_1 e^{-2t} + K_2 t e^{-2t} \\ I_L(0^+) = 0 \\ \frac{dI_L(0^+)}{dt} = -2 \end{array} \right.$$


$$\bullet K_1 = 0$$

$$\bullet K_2 = -2$$

$$I_L(t) = -2te^{2t}$$

$$-2 = \cancel{K_1 \cdot 2e^{2t}} + \cancel{K_2 e^{2t}} + \cancel{K_2 + 2e^{2t}} \quad K_2 = -2$$

Ora verifichiamo con Laplace

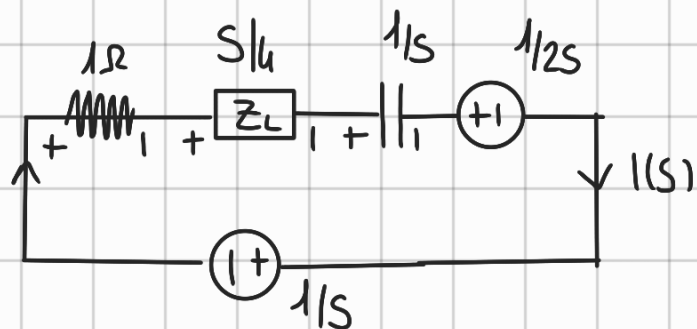

$$KV \quad R I + Z_L I + Z_C I + \frac{1}{2s} + \frac{1}{s} = 0$$


$$I(s) + \frac{S}{4} I(s) + \frac{1}{S} I(s) + \frac{1}{2s} + \frac{1}{s} = 0$$

$$I(s) = -\frac{2}{(s+2)^2} = -\frac{2}{(s+2)(s+2)} = -\left(\frac{1}{s+2} + \frac{1}{s+2}\right)$$


$$= -\frac{1}{s+2} - \frac{1}{s+2} =$$

$$= -e^{-2t} - e^{-2t} = -2e^{-2t} \mathcal{I}(t)$$


16 LUGLIO 2020 es.3

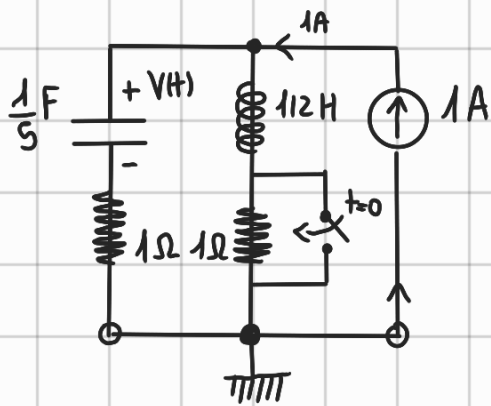

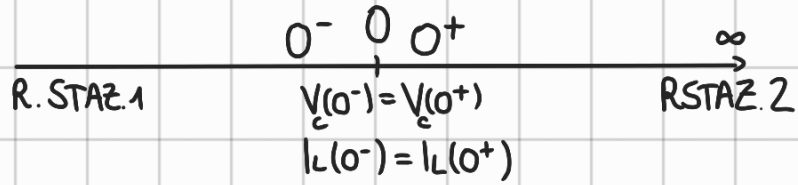Determina $v(t)$ $t \geq 0$ risposta completa
Verificare poi con Laplace



• $t=0^-$ trovo le variabili di stato

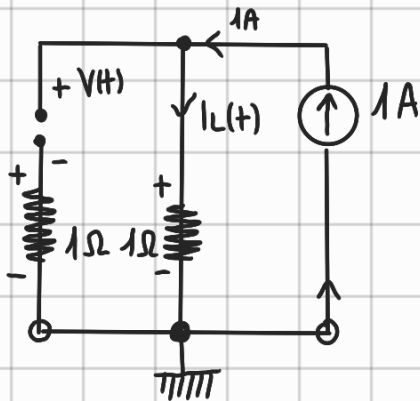

REGIME STAZIONARIO $C \rightarrow CA$ $L \rightarrow CC$


su C.A. non passa corrente quindi

$$I_L(0^-) = 1A = I_L(0^+)$$

$$\text{KV} \quad R I_L(t) - V(t) = 0$$

$$\text{V}(t) = R I_L(t) \quad V_C(0^-) = 1V = V_C(0^+)$$

• Studio a $t=\infty$ (R. STAZ. 2)

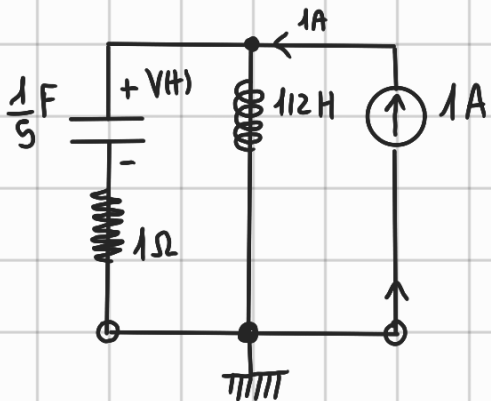

il resistore si scarica e si annulla

Ho un "RLC II"

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{2} \cdot \frac{1}{5}}} = \sqrt{10} \sim 3,16$$


$$d_s = \frac{R_s}{2L} = \frac{1}{2 \cdot \frac{1}{2}} = 1$$

$$d_s < \omega_0$$

SOTTOSMORZATO


$$S_{1,2} = -1 \pm \sqrt{(\sqrt{10})^2 - 1^2} j = -1 \pm 3j$$
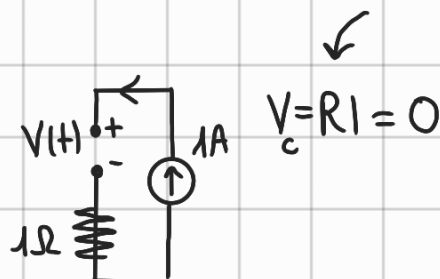
$$V(t) = k_1 e^{-t} \cos(3t) + k_2 e^{-t} \sin(3t) + V_{RS2}$$



$$V_c = R I = 0$$

• Studio a 0⁺

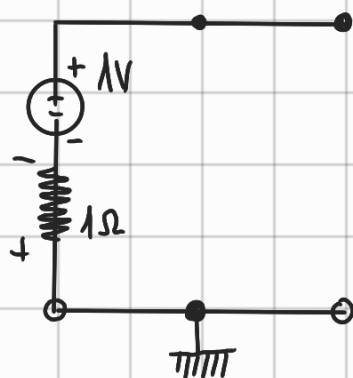

$$dV(t)/dt = 0$$

Quindi

$$\begin{cases} V(t) = K_1 e^{-t} \cos(3t) + K_2 e^{-t} \sin(3t) \\ V(0^+) = 1 \text{ V} \\ dV(0^+)/dt = 0 \text{ V/s} \end{cases}$$



$$1 = K_1 \quad K_2 = 1$$

$$0 = K_1 (-e^{-t} \cos(3t) - e^{-t} 3 \sin(3t)) + K_2 (-e^{-t} \sin(3t) + 3e^{-t} \cos(3t))$$

$$0 = -1 + K_2 3 \quad K_2 = 1/3$$

$$V_c(t) = e^{-t} \cos(3t) + \frac{1}{3} e^{-t} \sin(3t)$$

Ora Laplace

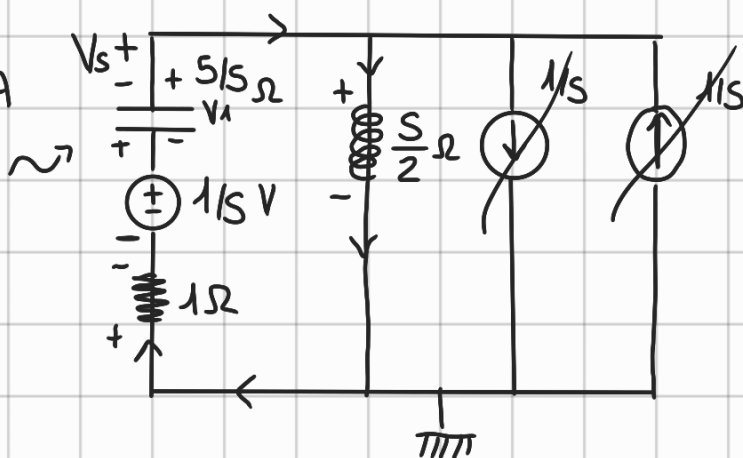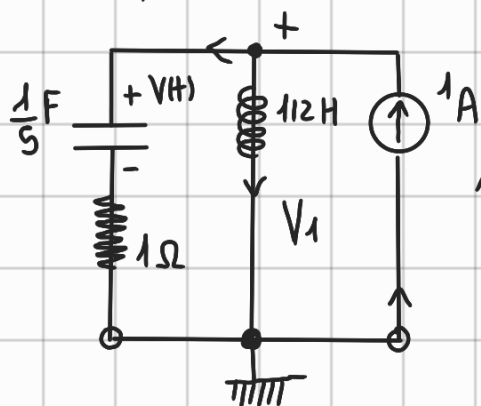


$$V(s) - V_1 - \frac{1}{s} = 0$$

$$V_1 = \frac{1}{s} \frac{5/s}{\frac{5}{s} + 1 + \frac{s}{2}}$$

$$\hookrightarrow V(s) = V_1 + \frac{1}{s} = \frac{s+2}{s^2+2s+10} = \frac{A}{s-(-1+j3)} + \frac{A^*}{s-(-1-j3)}$$



✓

15 SETTEMBRE 2020 ED.3

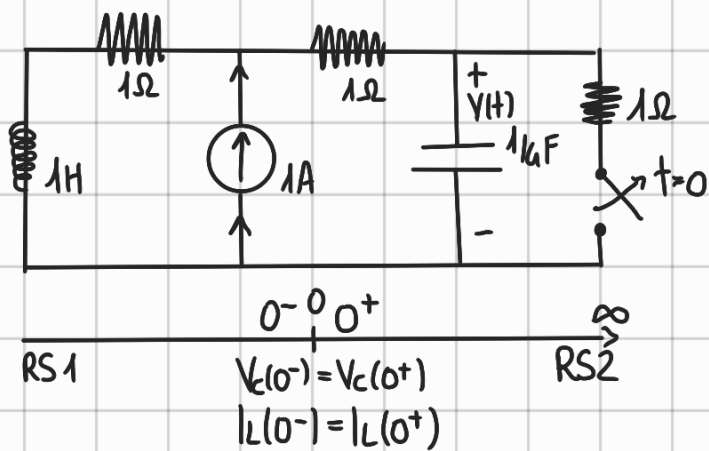

Determina $V(t)$ $t \geq 0$ completa
 Verifica con Laplace

• $t=0^-$ trova le var di stato

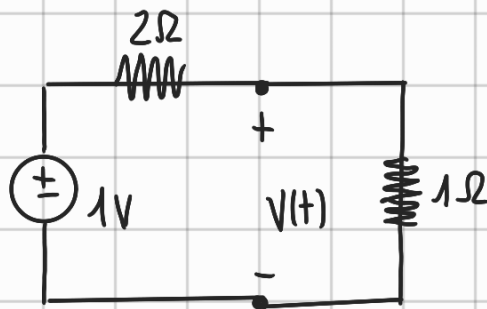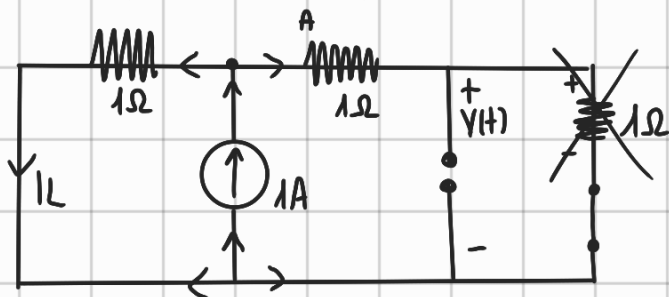


$$V(t) = \frac{\frac{1}{2}}{\frac{1}{2} + 1} = \frac{\frac{1}{2}}{\frac{3}{2}} = \frac{1}{2} \cdot \frac{2}{3} = \frac{1}{3} \text{ V}$$

$$V(0^-) = \frac{1}{3} \text{ V} = V(0^+)$$

$$I_L(0^-) = \frac{1}{\frac{1}{2} + 1} = \frac{2}{3} \text{ A} = I_L(0^+)$$

• $t=\infty$ serie

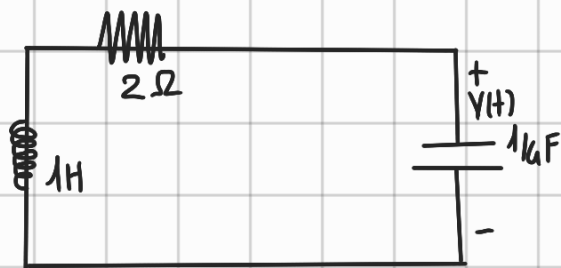

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4}}} = 2$$

$$\zeta = \frac{R_s}{2L} = \frac{2}{2} = 1$$

$$\zeta < \omega_0$$

SOTTOSMORZATO


$$s_{1,2} = -1 \pm \sqrt{2^2 - 1^2} j = -1 \pm \sqrt{4 - 1} j = -1 \pm \sqrt{3} j$$

$$V(t) = k_1 e^{+} \cos(\sqrt{3}t) + k_2 e^{+} \sin(\sqrt{3}t) + RS2$$

↓

$$V_C(t) = 1$$

• Studio a 0^+ per trovare $dV(t)/dt$

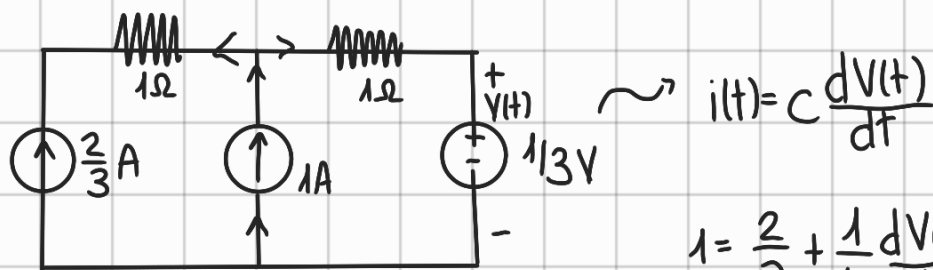

$$1 = \frac{2}{3} + \frac{1}{4} \frac{dV(t)}{dt}$$

$$\frac{1}{4} \frac{dV(t)}{dt} = \frac{1}{3}$$



$$dV(t)/dt = 4/3 \text{ V}$$

$$\Rightarrow \begin{cases} V(t) = K_1 e^{-t} \cos(\sqrt{3}t) + K_2 e^{-t} \sin(\sqrt{3}t) + 1 \\ \frac{dV(0^+)}{dt} = \frac{4}{3} \text{ V/s} \\ V(0^+) = 1/3 \text{ V} \end{cases}$$


$$K_1 = -2/3$$

$$K_2 = 2\sqrt{3}/9$$

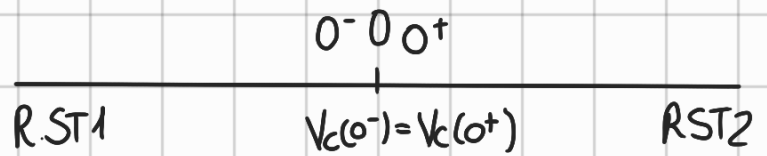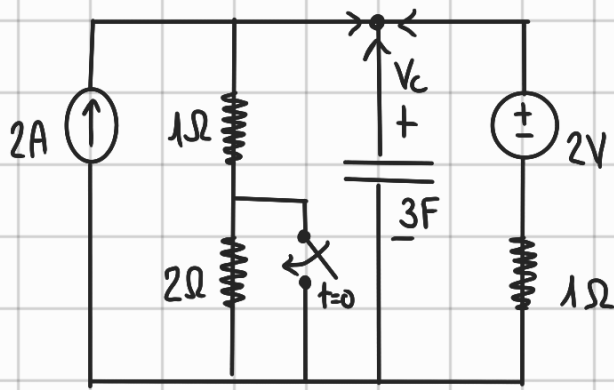2 2006 es 3 Determina $V_C(t)$ risposta libera + forzata OK



• $t=0^-$ trasformo

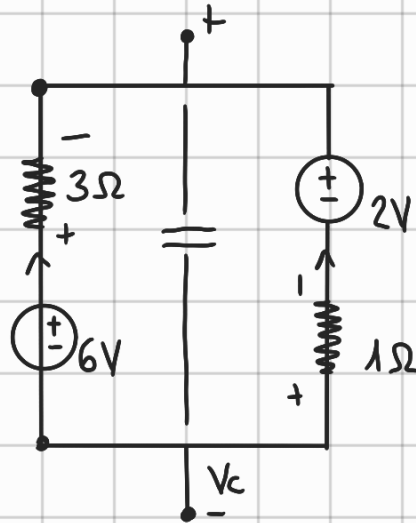


$$\text{Millman } V_C = \frac{2 \cdot 1 + 6 \cdot \frac{1}{3}}{1 + \frac{1}{3}} = 3$$

$$V_C(0^-) = V_C(0^+) = 3 \text{ V}$$

$$V_P(t) = 3e^{-t/RC} = 3e^{-t/2/3} \text{ V}$$

$$R(0^+) \quad 1 \parallel 1 = \frac{1}{1+1} = \frac{1}{2}$$

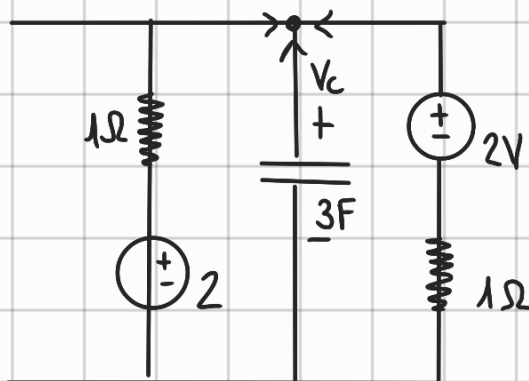
$$RC = \frac{1}{2} \cdot 3 = \frac{3}{2}$$



$$V(\infty) = 2 \text{ V}$$

$$V_{\text{for}} = 2(1 - e^{-t/2/3}) \text{ V}$$

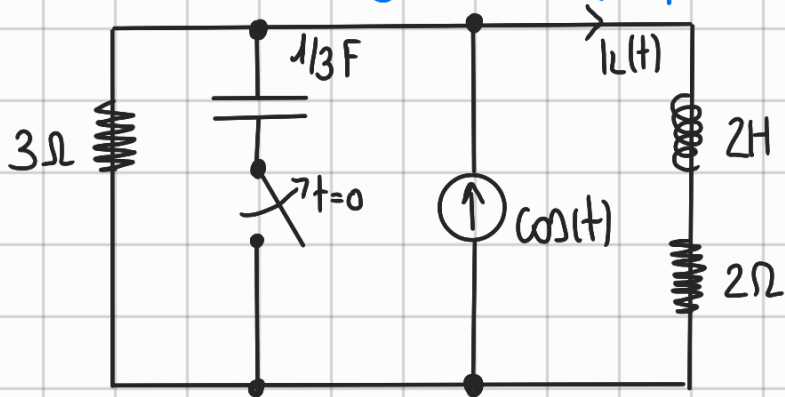
16 DIC 2006 053 OK Determina $i_L(t)$ per $t > 0$ risposta libera e forzata



$t = 0^-$

LIBERA $i_L(t) = i_0 e^{-t/\tau_{eq}}$


$\tau_{eq} = \frac{L}{R_{eq}}$

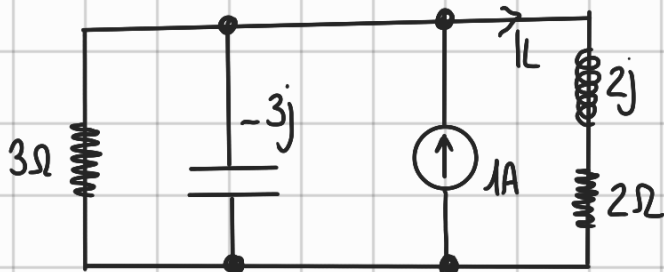

$i_L(0^-)? = i_L(0^+)$

$\Downarrow$

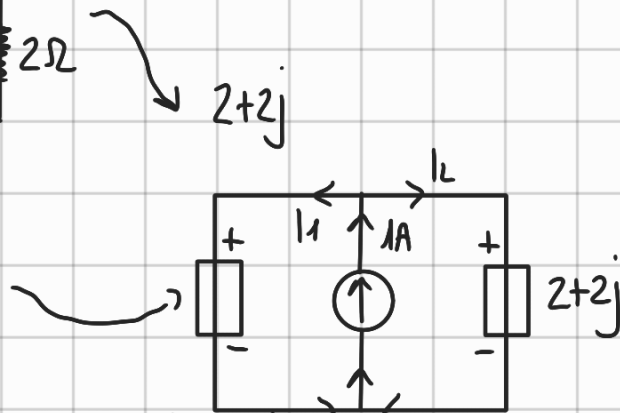$\parallel \frac{-3j \cdot 3}{3 - 3j} = \frac{3}{2} - \frac{3}{2}j$



KI: $1 = i_1 + i_L \quad i_L = 1 - i_1$

KV: $(2 + 2j)i_L - \left(\frac{3}{2} - \frac{3}{2}j\right)i_1 = 0 \quad i_L = \frac{9}{25} - \frac{12}{25}j$


$i_L(0^-) = \frac{9}{25} \text{ A} = i_L(0^+)$

$R_{eq} = 3 + 2 = 5 \Omega$

$i_{lib}(t) = \frac{9}{25} e^{-\frac{5}{2}t} \text{ A}$

$\tau_{eq} = \frac{L}{R_{eq}} = \frac{2}{5}$


$t = 0^+$

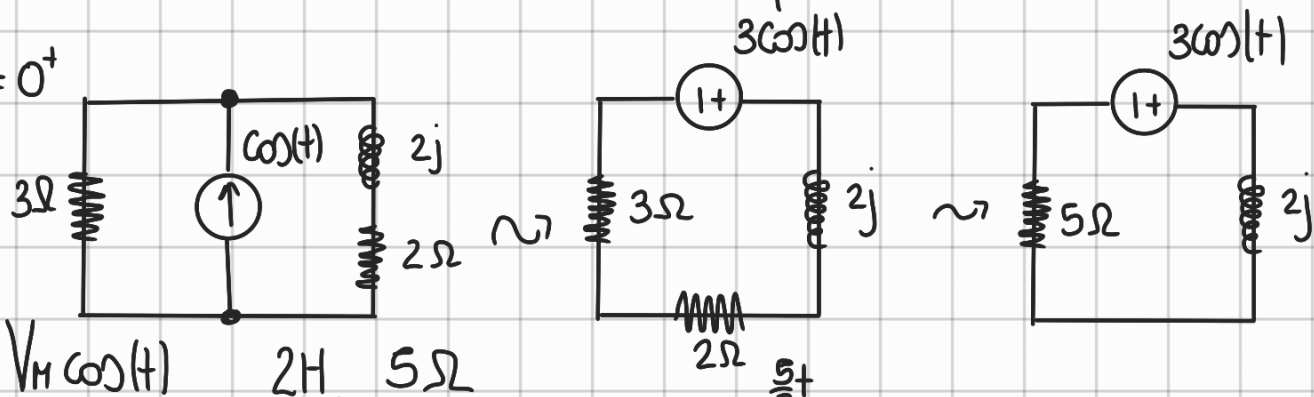

$V_H \cos(t) = \frac{3}{5} \cos(t)$


$i_L(t) = -\frac{3}{\sqrt{5^2 + 2^2}} \cos\left(\arctan\left(\frac{2}{5}\right)\right) e^{-\frac{5}{2}t} + \frac{3}{\sqrt{5^2 + 2^2}} \cos\left(t - \arctan\left(\frac{2}{5}\right)\right) =$
 $= -0,51 e^{-5,12t} + 0,557 \cos(t - 21,80^\circ)$

7 GIU 2012 OK

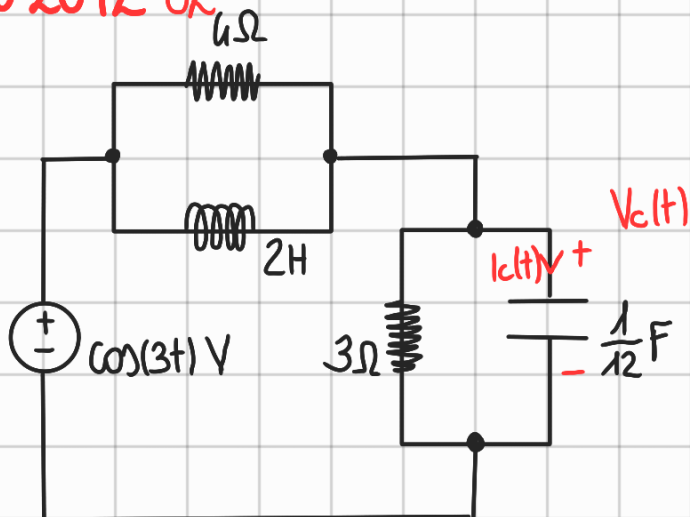

Determina $V_c(t)$ e $I_c(t)$ in regime permanente sinusoidale

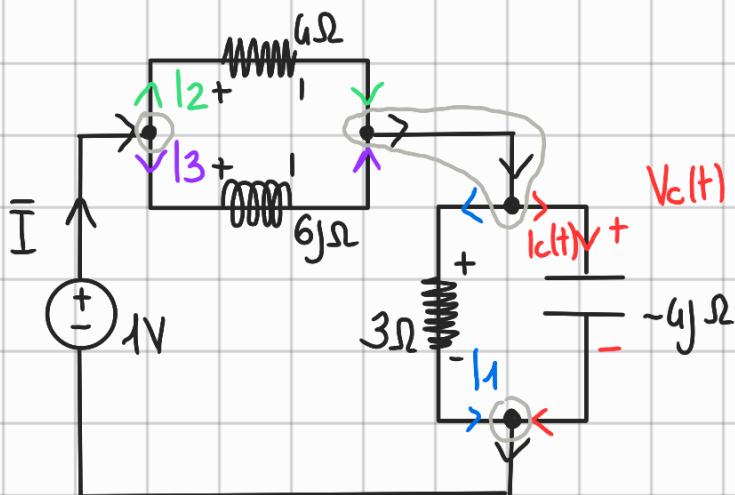Porto tutto nel dominio dei fasori $\omega = 3 \text{ rad/s}$



$$Z_L = j\omega L = 6j \Omega$$

$$Z_C = \frac{1}{j\omega C} = -4j \Omega$$

$$\bar{V}_g = e^{j0} = 1 \text{ V}$$

Trovo I semplificando


$$Z_1 = 4 \parallel 6j = \frac{4 \cdot 6j}{4 + 6j} = \frac{24j}{4 + 6j} \cdot \frac{4 - 6j}{4 - 6j} = \frac{96j + 144}{16 + 36} = \frac{96j + 144}{52}$$

$$= \frac{72 + 48j}{26} = \frac{36 + 24j}{13} \Omega$$

$$Z_2 = 3 \parallel (-4j) = \frac{3(-4j)}{3 - 4j} = \frac{48 - 36j}{25} \Omega$$

$$Z_3 = Z_1 + Z_2 = \frac{36 + 24j}{13} + \frac{48 - 36j}{25} = \frac{1524}{325} + \frac{132j}{325}$$
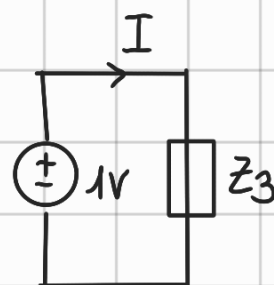
$$\bar{V} = Z_3 \bar{I} \quad \bar{I} = \frac{\bar{V}}{Z_3} = \frac{127}{600} - \frac{11j}{600}$$



Trova tutte le altre correnti con KV e KI

$$\text{KI: } \begin{cases} I_2 + I_3 = I_1 + I_c \\ I_1 + I_c = I \\ I_2 + I_3 = I \end{cases} \quad \text{KV: } \begin{cases} -V_L + V_{R2} = 0 \\ V_c - V_{R1} = 0 \\ V_{R1} - 1 + V_L = 0 \end{cases} \sim \begin{cases} -6jI_3 + 6I_2 = 0 \\ V_c = 3I_1 \\ 3I_1 - 1 + 6jI_3 = 0 \end{cases}$$

$$V_c = 3I_1 \quad \text{basta trovare } I_1 \quad 3I_1 = 1 - 6jI_3$$
$$I_c = I - I_1 \quad \bullet I_1 = \frac{1}{3} - 2jI_3 \quad \bullet -3jI_3 + 2I_2 = 0$$

$$\sim 3jI_3 = 2I_2 \quad I_2 = I - I_3 \quad 3jI_3 = 2I - 2I_3 \quad (3j + 2)I_3 = 2I$$
$$I_3 = \frac{2I}{2 + 3j} \quad \Rightarrow I_1 = \frac{1}{3} - \frac{4jI}{2 + 3j}$$


$$\text{Quindi } V_c = 1 - \frac{12jI}{2 + 3j} = \frac{19}{50} - \frac{17}{50}j \quad V$$

$$I_c = I - \left(\frac{1}{3} - \frac{4jI}{2 + 3j} \right) = \frac{17}{200} + \frac{19}{200}j \quad A$$

$$V_c(t) = \sqrt{\left(\frac{19}{50}\right)^2 + \left(\frac{17}{50}\right)^2} \cos\left(3t - \arctan\left(\frac{17}{19}\right)\right) = 0,51 \cos(3t - 42^\circ) \quad V$$

$$I_c(t) = \sqrt{\left(\frac{17}{200}\right)^2 + \left(\frac{19}{200}\right)^2} \cos\left(3t + \arctan\left(\frac{19}{17}\right)\right) = 0,127 \cos(3t + 48^\circ) \quad A$$


26 FEB 2007

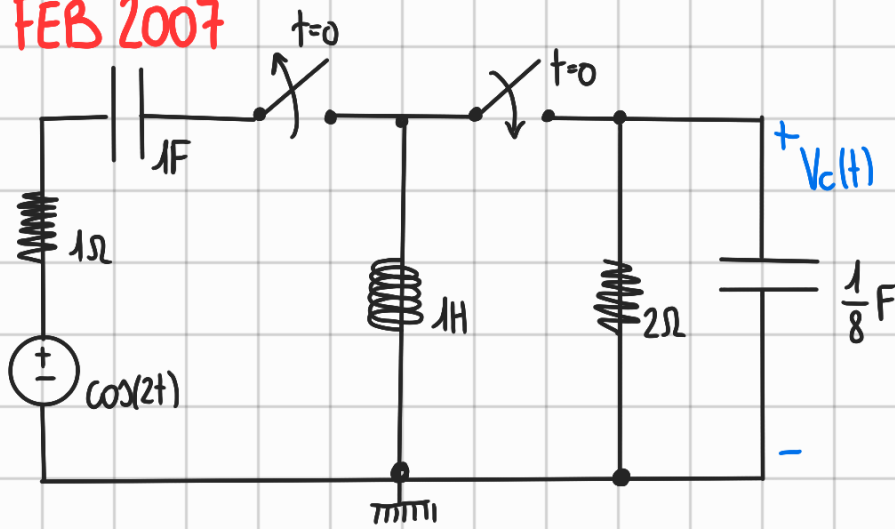

Determina $V_c(t)$

REG SINI
 $t=0^- \quad 0 \quad 0^+$
 $V_c(0^-) = V_c(0^+)$
 $I_L(0^-) = I_L(0^+)$

• $t=0^-$ REGIME SINUSOIDALE

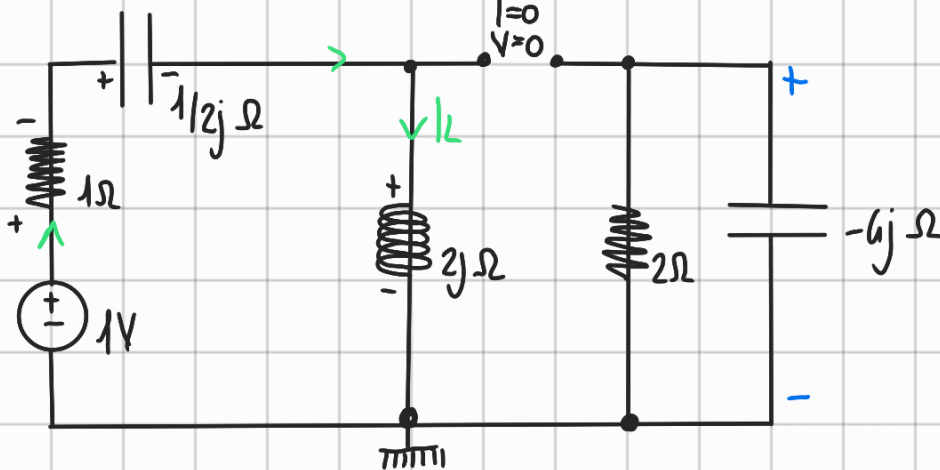


$$\text{KV: } +2jI_L - 1 + 1I_L + \frac{1}{2j}I_L = 0 \leadsto -4I_L - 2j + 2jI_L + I_L = 0$$

$$(2j - 3)I_L = 2j \quad I_L = \frac{2j}{2j - 3} = \frac{4}{13} - \frac{6}{13}j$$

• $I_L(0^-) = I_L(0^+) = 4/13 \text{ A}$

• $V_c(0^-) = 0$

• $t=\infty$

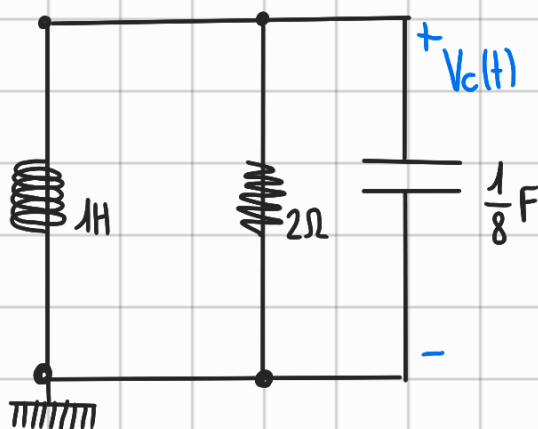

RLC parallelo

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1/8}} = 2\sqrt{2} \sim 2,82$$


$$d\rho = \frac{G_P}{2C} = \frac{1}{2 \cdot 2 \frac{1}{8}} = 2$$

$$d < \omega_0$$

SOTTOSMORZATO

$$s_{1,2} = -2 \pm \sqrt{(2\sqrt{2})^2 - (2)^2} j = -2 \pm 2j \quad \begin{matrix} \text{Re} = -2 \\ \text{Im} = 2 \end{matrix}$$
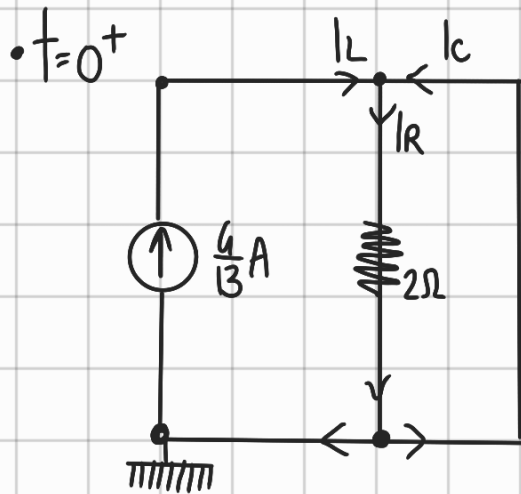
$$V_c(t) = K_1 e^{-2t} \cos(2t) + K_2 e^{-2t} \sin(2t) + \cancel{R/2}$$



$$\begin{matrix} V_c(0) = 0 \\ I_L(0) = 4/13 \text{ A} \end{matrix}$$


$$\begin{aligned} I_L + I_C &= I_R \\ \frac{4}{13} + C \frac{dV(t)}{dt} &= 0 \quad \frac{4}{13} - \frac{1}{8} \frac{dV(t)}{dt} = 0 \end{aligned}$$

$$dV(t)/dt = 32/13 \text{ V/s}$$

$$\Rightarrow \begin{cases} V_c(t) = K_1 e^{-2t} \cos(2t) + K_2 e^{-2t} \sin(2t) \\ V_c(0) = 0 \text{ V} \\ \frac{dV_c(t)}{dt} = -32/13 \text{ V/s} \end{cases}$$

$$\Rightarrow V_c(t) = -\frac{16}{13} e^{-2t} \sin(2t)$$

LAPLACE

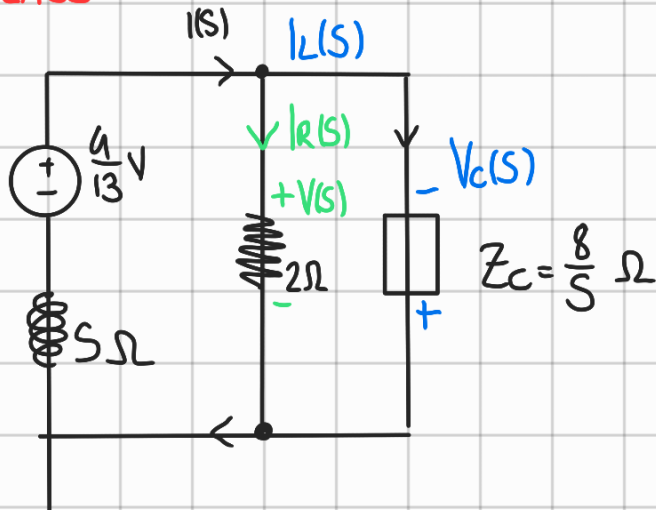

$$V_c(s) = \frac{\frac{4}{13} \frac{1}{s}}{\frac{1}{s} + \frac{1}{2} + \frac{s}{8}} = \frac{32}{13} \frac{1}{s^2 + 6s + 8} = \frac{2^5}{13 (s+2)^2 + 2^2} = \frac{8}{13} \frac{4}{(s+2)^2 + 4}$$

$$\mathcal{L}^{-1}\{V_c(s)\} = \frac{8}{13} e^{-2t} \sin(2t)$$