

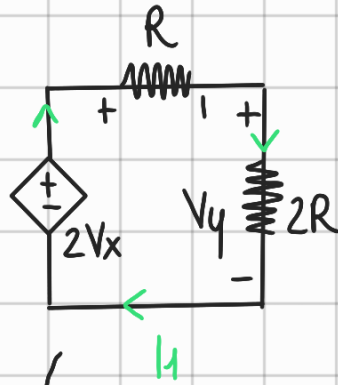


25 MAGGIO 2011 con il metodo rapido

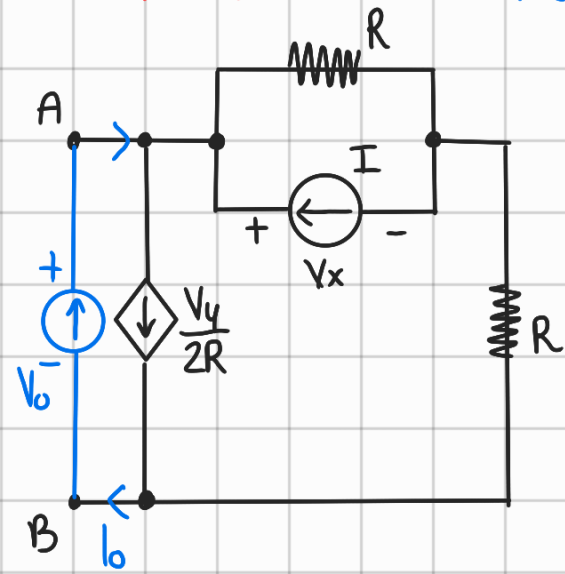

$$\text{KVL: } \begin{cases} R I_1 + V_y - 2V_x = 0 \\ V_y = 2R I_1 \end{cases}$$
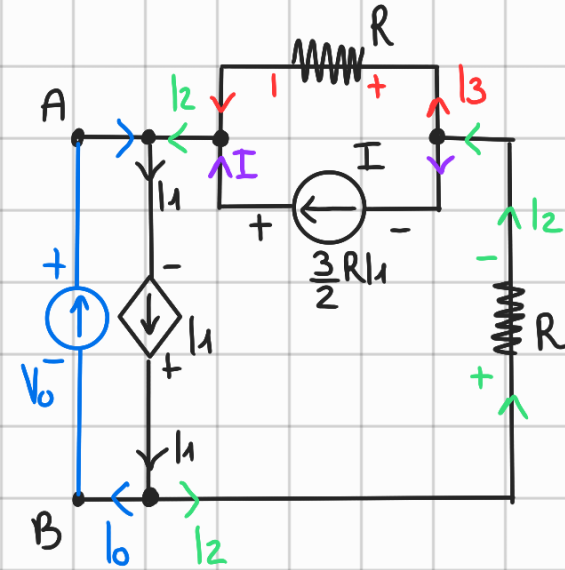
$$\begin{aligned} \Rightarrow V_y &= 2R I_1 \\ R I_1 + 2R I_1 - 2V_x &= 0 \\ 3R I_1 - 2V_x &= 0 \\ 2V_x &= 3R I_1 \\ \bullet V_x &= \frac{3}{2} R I_1 \end{aligned}$$



$$\text{K1: } \begin{cases} I_0 + I_2 = I_1 \\ I_1 + I_3 = I_2 \end{cases} \Rightarrow \boxed{I_0 + I_1 + I_3 = I_1}$$

$$\text{KV } +V_g + V_0 = 0 \quad \boxed{V_0 = -V_g}$$

$$-\frac{3}{2} R I_1 - R I_3 = 0 \sim \boxed{+\frac{3}{2} I_1 + I_3 = 0}$$

$$V_g = R I_2 - \frac{3}{2} R I_1$$

$$\hookrightarrow -R I_2 + V_g + \frac{3}{2} R I_1 = 0$$

$$\boxed{V_0 = \frac{3}{2} R I_1 - R I_2}$$

$$I_3 = -\frac{3}{2} I_1 \quad I_0 + I_1 - \frac{3}{2} I_1 = I_1 \quad 2I_0 + 2I_1 - 3I_1 - 2I_1 = 0$$

$$2I_0 + 2I_1 - 5I_1 = 0$$

$$I_2 = I_1 - I_0$$

$$I_1 = \frac{2I_0 + 2I_1}{5}$$

$$V_0 = \frac{3}{2} R \frac{2I_0 + 2I_1}{5} - R \left(\frac{2I_0 + 2I_1}{5} - I_0 \right)$$

$$= \frac{3(2I_0 + 2I_1)}{10} R - \frac{2I_0 + 2I_1}{5} R + R I_0 =$$


$$= \frac{6R I_0 + 6R I_1 - 4R I_0 - 4R I_1 + 10R I_0}{10} = \frac{12R I_0}{10} + \frac{2}{10} I_1 R$$

$$V_0 = \frac{6}{5} R I_0 + \frac{1}{5} R I_1$$

$$V_{eq} = \frac{1}{5} R I_1 \quad V$$

$$R_{eq} = \frac{6}{5} R \quad \Omega$$

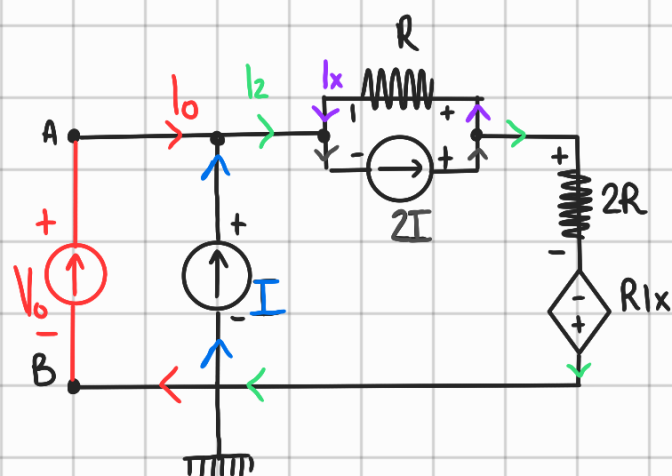1 LUGLIO 2011, ES 1 Thevenin con il metodo rapido



$$V_o = V_{eq} + R_{eq} I_o$$

$$K1: I_o + I - 2I + I_x = 0$$

$$I_o + I_x = I$$

$$I_2 = I_o + I$$

$$KV: \bullet V_{gc1} = V_o$$

$$\bullet V_{gc2} = R I_x$$

$$\bullet 2R I_2 - R I_x - V_{gc1} - V_{gc2} = 0$$

$$2R(I_o + I) - R(I - I_o) - V_o - R(I - I_o) = 0$$


$$2R I_o + 2R I - R I + R I_o - V_o - R I + R I_o = 0$$

$$V_o = 4R I_o$$


$$V_{eq} = 0$$

$$R_{eq} = 4R$$

29 GIUGNO 2020 equivalente di Thevenin

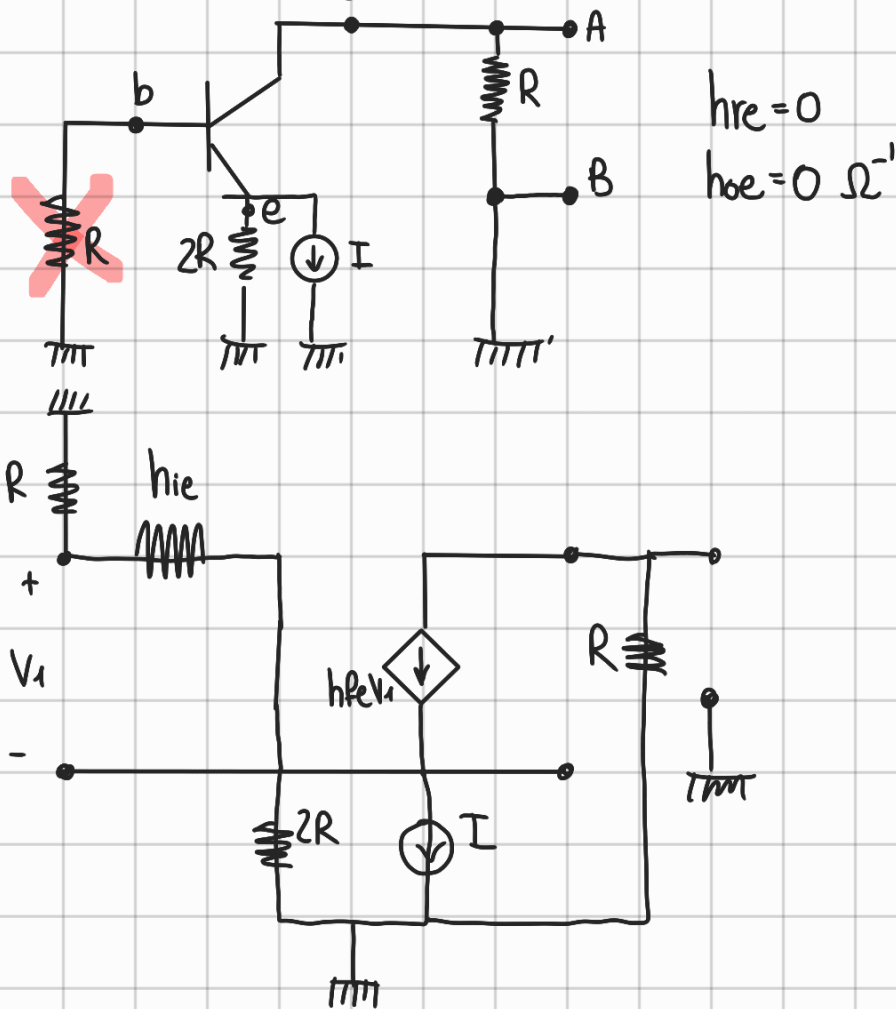

Riduzione di tutto

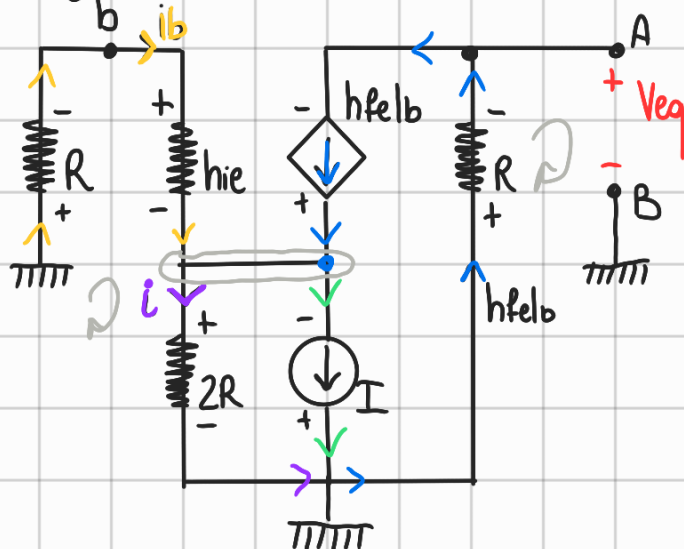

$$KI \quad I_b + h_{fe} I_b = i + I \quad \Rightarrow \quad I_b = \frac{2RI}{R + h_{ie} + 2R(1 + h_{fe})}$$



$$KV \quad R I_b + h_{ie} I_b + 2R i = 0$$

$$V_{eq} + R h_{fe} I_b = 0$$

$$\leadsto V_{eq} = -R h_{fe} I_b = -R h_{fe} \frac{2RI}{R + h_{ie} + 2R(1 + h_{fe})}$$



Trovo R_{eq}

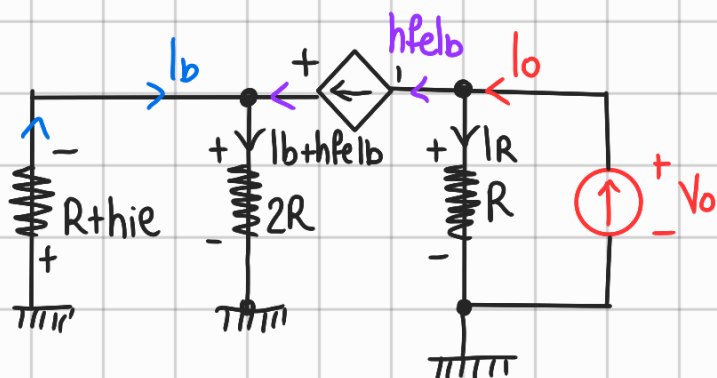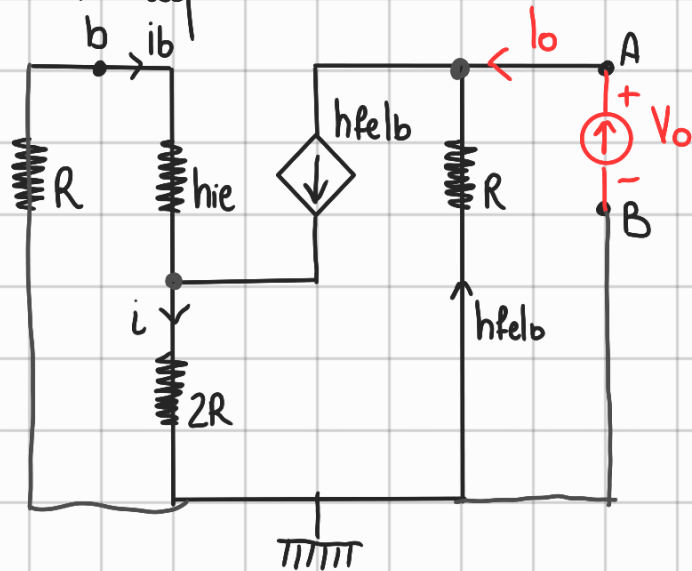


$$\begin{aligned} \text{KV } 2R I_b (1+hfe) + (R+hie) I_b &= 0 \\ I_b (2R(1+hfe) + R+hie) &= 0 \\ I_b &= 0 \end{aligned}$$

$$\begin{aligned} \Rightarrow I_o &= I_R \\ V_o &= R I_R \end{aligned}$$

$$R_{eq} = \frac{R I_R}{I_R} = R$$

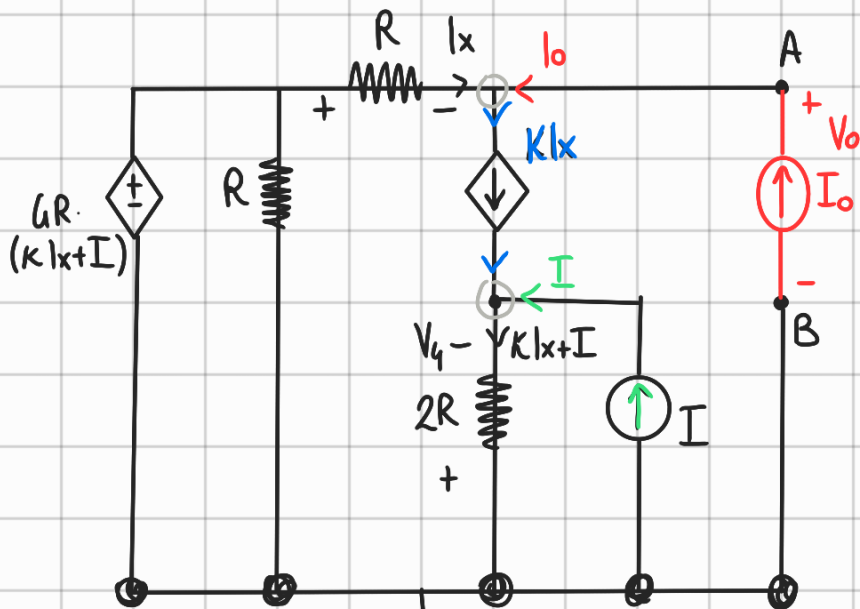ESERCIZIO IN CLASSE Thevenin con metodo rapido



trovo $V_q = 2R(kIx + I)$


$$kIx + I_o = kIx \quad \leadsto \quad I_o = kIx - I_x \quad I_x(k-1) = I_o$$

$$I_x = \frac{I_o}{k-1}$$

$$V_q = 2R\left(k \frac{I_o}{k-1} + I\right)$$

quindi ho trovato tutte le grandezze di controllo
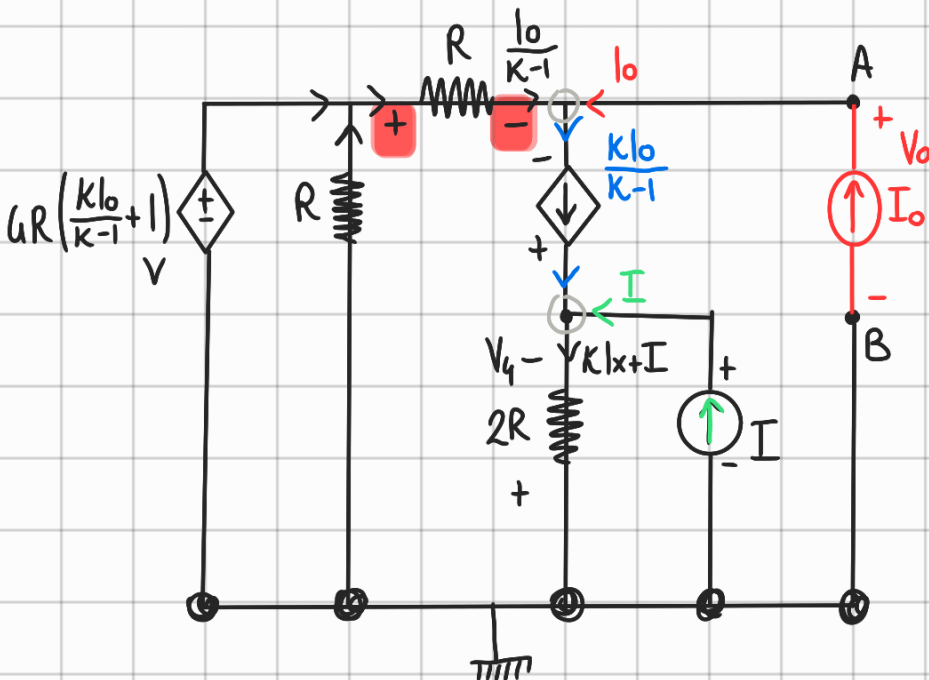
$$I_x = \frac{I_o}{k-1} \quad V_q = 2R\left(\frac{kI_o}{k-1} + I\right)$$




KV ↻

$$\begin{cases} V_o - V_{gI} + V_{gx} = 0 \\ V_{gI} + V_q = 0 \\ + V_{gx} - V_q - R \frac{I_o}{k-1} = 0 \end{cases}$$

$$\begin{aligned} V_{gI} &= -V_q \\ V_{gx} &= R \frac{I_o}{k-1} + V_q \\ V_o &= V_{gI} - V_{gx} = -V_q - \frac{R I_o}{k-1} - V_q = -\frac{R I_o}{k-1} - 2V_q = \end{aligned}$$

e vai a calcoli

13 NOV 2008 es 1 Thevenin OK

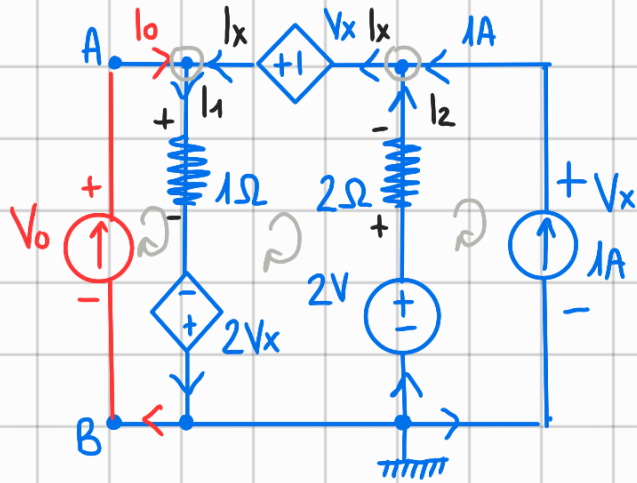

Usa il metodo rapido $V_0 = V_{eq} + R_{eq} I_0$

• Studio le correnti

$$V = RI \quad I = \frac{V}{R}$$

$$\begin{array}{l|l} \text{KI} & I_0 - I_1 + I_2 + 1 = 0 \\ \text{KV} & \left. \begin{array}{l} V_x - 2 + 2I_2 = 0 \\ -2I_2 + 2 + 2V_x - 1 + V_x = 0 \\ -I_1 + 2V_x + V_0 = 0 \end{array} \right\} \begin{array}{l} I_2 = I_1 - I_0 - 1 \\ V_x = 2 - 2I_2 \\ 3V_x - 2I_2 - I_1 + 2 = 0 \end{array} \right\} V_x = 2 - 2I_1 + 2I_0 + 2 \\ & \sim V_0 = I_1 - 2V_x \end{array}$$

$$3(2 - 2I_1 + 2I_0 + 2) - 2(I_1 - I_0 - 1) - I_1 + 2 = 0$$

$$6 - 6I_1 + 6I_0 + 6 - 2I_1 + 2I_0 + 2 - I_1 + 2 = 0$$

$$16 - 9I_1 + 8I_0 = 0$$

$$+9I_1 = \frac{16 + 8I_0}{9}$$

$$\Rightarrow V_0 = \frac{16 + 8I_0}{9} - 2 \left(I_1 - 2 \frac{16 + 8I_0}{9} + 2I_0 \right) =$$


$$= \frac{16 + 8I_0}{9} - 8 + \frac{4(16 + 8I_0)}{9} - 4I_0 = \frac{16 + 8I_0 - 72 + 64 + 32I_0 - 36I_0}{9} =$$

$$= \frac{4}{9}I_0 + \frac{8}{9}$$

$$V_{eq} = \frac{8}{9} \text{ V}$$

$$R_{eq} = \frac{4}{9} \Omega$$

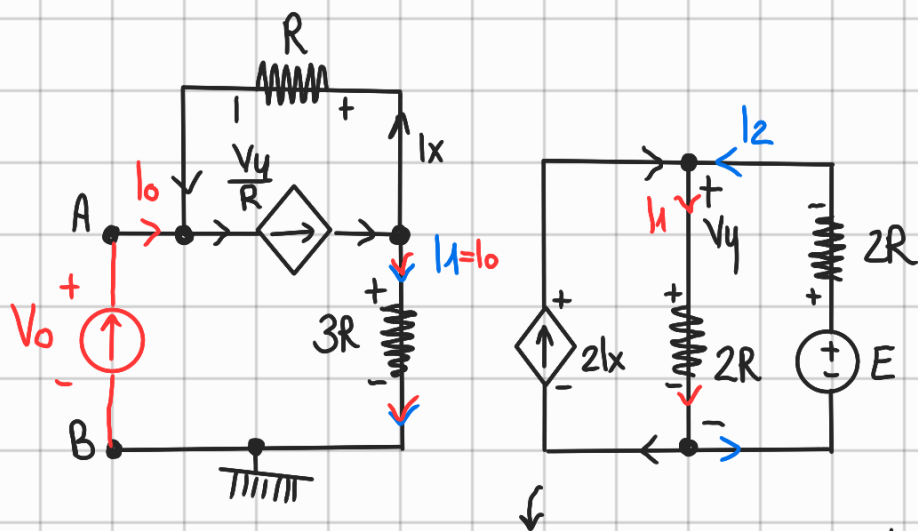9 Nov 2006 es 1 Therein AB conip metodo rapido OK



Studio questo circuito per trovare V_y

$$\begin{array}{l} \text{KI:} \\ \text{KV:} \end{array} \left\{ \begin{array}{l} 2|x + |z| = |1 \\ -2R|z| + E - V_4 = 0 \\ V_4 - V_{gI} = 0 \end{array} \right. \cdot |1 = \frac{V_4}{2R} \quad \leadsto \left\{ \begin{array}{l} 2|x + |z| = \frac{V_4}{2R} \\ |z| = \frac{V_4}{2R} - 2|x \\ V_g = +V_{gI} \end{array} \right.$$

$$-2R \left(\frac{V_4}{2R} - 2I_x \right) + E - V_4 = 0$$

$$-V_y + U R I_x + E - V_y = 0 \quad \leadsto \quad +2V_y = +U R I_x + E$$

$$V_4 = 2R|x + \frac{E}{2} \quad \checkmark$$

Gen. corrente

$$2Ix + \frac{E}{2R}$$

$$V_o = V_{eq} + R_{eq} I_o \quad \text{KI: } \begin{cases} I_o + I_x = 2I_x + \frac{E}{2R} = I_x + I_1 & \bullet I_o = I_1 \\ \text{KV: } \begin{cases} -RI_x + V_{GC} = 0 \\ -3RI_1 + V_o + V_{GC} = 0 \end{cases} \end{cases}$$

$$V_o = 3R I_o - V_{gc} \quad V_{gc} = R I_x \quad |x-2|x = \frac{E}{2R} - I_o$$

$$+ I_x = I_o - \frac{E}{2R}$$


$$= R \left(I_o - \frac{E}{2R} \right) - R I_o - \frac{E}{2}$$

$$V_o = 3R I_o - R I_o + \frac{E}{2} =$$

$$= 2RI_0 + \frac{E}{2}$$

$$R_{eq} = 2R \quad V_{eq} = E/2$$

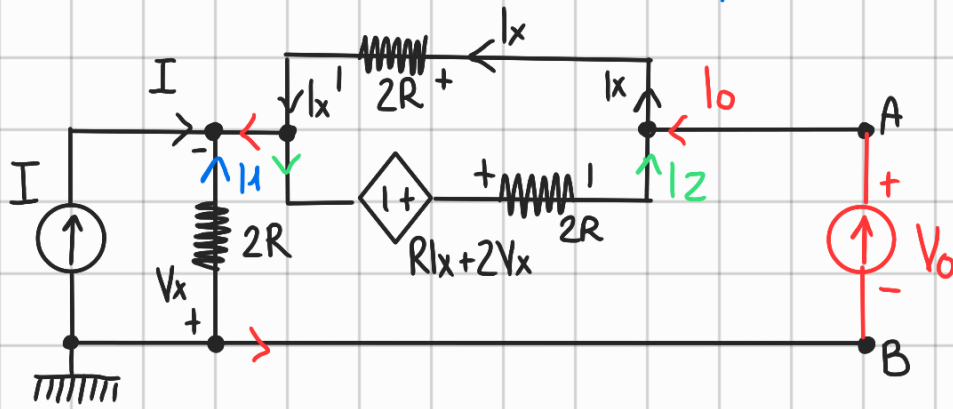3 2006 ex 1 Thevenin AB con il metodo rapido



$$V = RI$$

$$I = \frac{V}{R}$$

$$K1: \begin{cases} I + I_1 + I_x = I_2 \\ I_0 + I_2 = I_x \\ I_1 = \frac{V_x}{2R} \end{cases} \quad K2: \begin{cases} -2RI_2 + RI_x + 2V_x - 2RI_x = 0 \\ V_0 + V_x - RI_x - 2V_x + 2RI_2 = 0 \\ -V_x - V_0 = 0 \end{cases}$$

$$\downarrow$$

$$\begin{cases} I + \frac{V_x}{2R} + I_x = I_2 \\ I_x = I_0 + I_2 \\ V_x = -(I_0 + I_2)2R \end{cases} \quad \sim \begin{cases} I + \frac{V_x}{2R} + I_0 + I_2 = I_2 \\ I + \frac{V_x}{2R} + I_0 = 0 \end{cases}$$

$$\downarrow \quad \frac{V_x}{2R} = -(I_0 + I_1)2R$$

$$\bullet \quad 2V_x - RI_x - 2RI_2 = 0 \sim -4R(I_0 + I_1) - RI_0 - RI_2 - 2RI_2 = 0$$

$$+4RI_0 + 4RI_1 + RI_0 + RI_2 + 2RI_2 = 0$$

$$5RI_0 + 3RI_2 + 4RI_1 = 0$$

$$3RI_2 = \frac{-4RI_1 - 5RI_0}{3R} = -\frac{4}{3}I_1 - \frac{5}{3}I_0$$

$$I_2 = -\frac{4}{3}I_1 - \frac{5}{3}I_0$$

$$\bullet \quad V_0 - V_x - RI_x + 2RI_2 = 0 \quad V_0 = V_x + RI_x - 2RI_2 =$$

$$= -2RI_0 - 2RI_1 + RI_0 + RI_2 - 2RI_2 =$$

$$= -RI_0 - 2RI_1 - RI_2$$

$$= -RI_0 - 2RI_1 + R\frac{4}{3}I_1 + \frac{5}{3}RI_0 = \frac{2}{3}RI_0 - \frac{2}{3}RI_1$$

$$V_0 = V_{eq} + R_{eq}I_0$$

$$\downarrow R_{eq} = \frac{2}{3}R$$

$$V_{eq} = -\frac{2}{3}RI_1$$