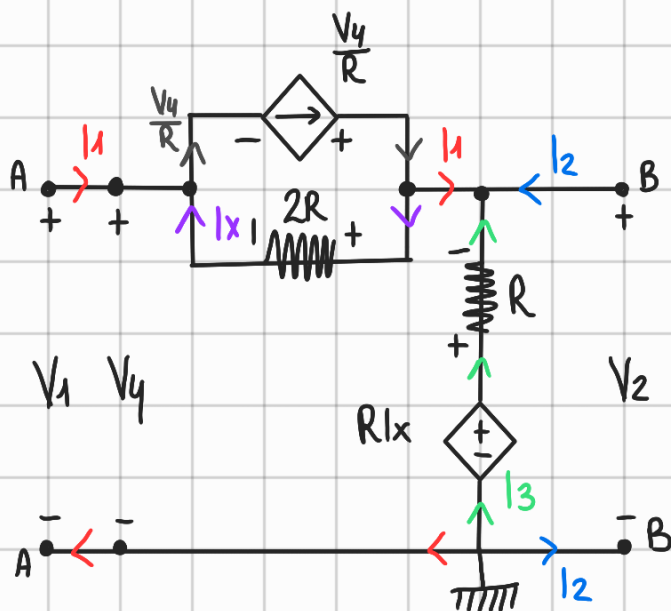


27 GIUGNO 2011, es 3 usa i parametri z



$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$KI \Rightarrow \begin{cases} I_1 + I_x = \frac{V_1}{R} \\ I_1 + I_2 + I_3 = 0 \end{cases}$$

$$KV \Rightarrow \begin{cases} 2RI_x = V_{gc} \\ V_2 - RI_x + RI_3 = 0 \\ -RI_3 + RI_x - V_1 - 2RI_x = 0 \end{cases}$$

$$\boxed{V_4 = V_1}$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad \begin{matrix} I_1 + I_x = \frac{V_1}{R} \\ I_1 + I_3 = 0 \end{matrix} \quad \sim \quad \begin{matrix} I_x = \frac{V_1}{R} - I_1 \\ I_3 = -I_1 \end{matrix}$$

$$\sim \begin{cases} 2R\left(\frac{V_1}{R} - I_1\right) = V_{gc} \\ V_2 - R\left(\frac{V_1}{R} - I_1\right) - RI_1 = 0 \\ RI_1 + R\left(\frac{V_1}{R} - I_1\right) - V_1 - 2R\left(\frac{V_1}{R} - I_1\right) = 0 \end{cases}$$

$$\begin{cases} 2V_1 - 2RI_1 = V_{gc} \\ V_2 - V_1 + RI_1 - RI_1 = 0 \\ \cancel{RI_1} + V_1 - \cancel{RI_1} - V_1 - \cancel{2V_1} + \underline{2RI_1} = 0 \end{cases}$$

$$\sim V_2 = V_1$$

$$RI_1 = V_1$$

$$\frac{V_1}{I_1} = Z_{11} = R \quad \checkmark$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = R$$

$$I_1=0 \left\{ \begin{array}{l} I_x = \frac{V_1}{R} \\ I_2 + I_3 = 0 \\ I_3 = -I_2 \end{array} \right\} \begin{cases} 2R \frac{V_1}{R} = V_{gc} \\ V_2 - R \frac{V_1}{R} - R I_2 = 0 \\ +R I_2 + R \frac{V_1}{R} - V_1 - 2R \frac{V_1}{R} = 0 \end{cases}$$

$$\leadsto 2V_1 = V_{gc}$$

$$V_2 - V_1 - R I_2 = 0$$

$$R I_2 + \cancel{V_1} - \cancel{V_1} - 2V_1 = 0$$

$$V_2 - \frac{R}{2} I_2 - R I_2 = 0$$


$$R I_2 = 2V_1 \quad V_1 = \frac{R}{2} I_2$$

$$V_2 = \frac{3}{2} I_2$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{3}{2} R \quad \checkmark$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{R}{2} \quad \checkmark$$

ESERCIZIO IN CLASSE parametri Z e y

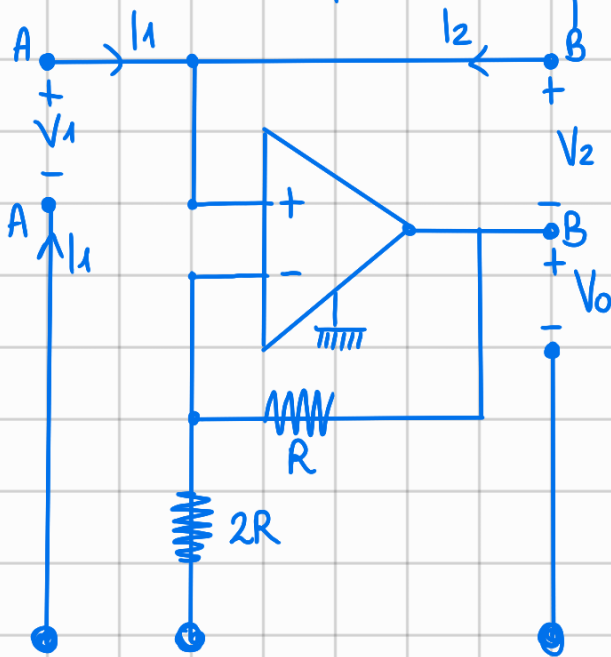

Ho che $I_1 = -I_2$ quindi $\nexists$ parametri Z