
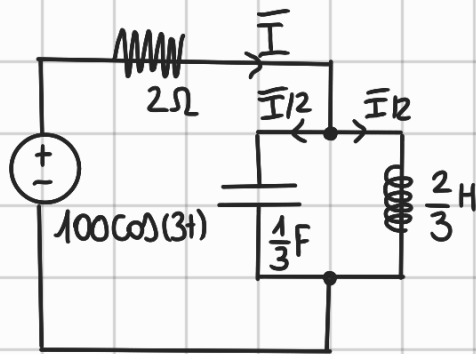


25 MAGGIO 2014 es. 5 OK

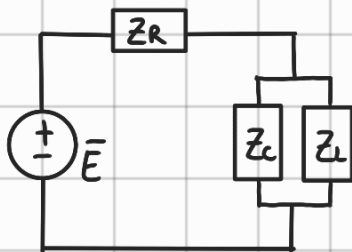

Determina potenza attiva, reattiva e potenza istantanea erogata dal generatore

DOMINIO DEI FASORI



$$\bar{E} = 100 \text{ V}$$

$$Z_R = 2 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j3 \cdot \frac{1}{3}} = -j \Omega$$

$$Z_L = j\omega L = j3 \cdot \frac{2}{3} = 2j \Omega$$

Troviamo la corrente

$$Z_C \parallel Z_L = \frac{-j(2j)}{2j-j} = \frac{2}{j} = -2j$$

$$+ Z_R = 2 - 2j \Omega$$

$$\bar{I} = \frac{\bar{E}}{\underline{Z}} = \frac{100}{2-2j} = \frac{50}{1-j} \frac{1+j}{1+j} = \frac{50+50j}{1+1} = 25+25j \text{ A}$$

$$\bar{P}_g = \frac{1}{2} \bar{E} \cdot \bar{I}^* = \frac{1}{2} \cdot 100 (25 - 25j) = 1250 - 1250j \text{ VA}$$

$$P_g = 1250 \text{ W}$$


$$Q_g = -1250 \text{ VAR}$$

$$A = \sqrt{P_g^2 + Q_g^2} = 1767$$

$$P_{\text{MAX}} = P + A = 3017 \text{ W}$$


$$P_{\text{MIN}} = P - A = -517 \text{ W}$$

15 DIC 2008 es.2 OK

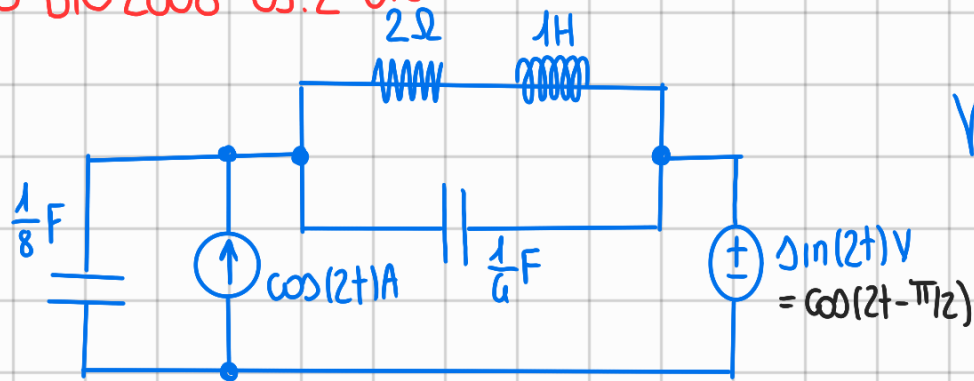


Verifica Boucherot

DOMINIO DEI FASORI

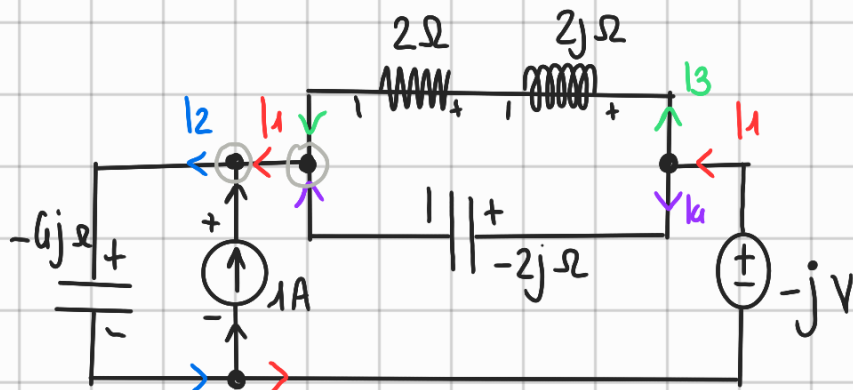
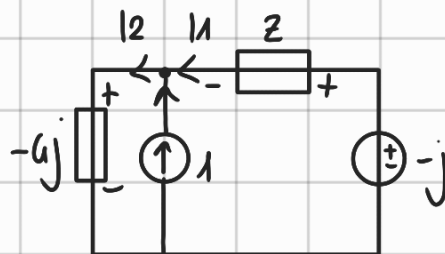
$$Z = \frac{(2+2j)(-2j)}{2+2j-2j} = 2-2j$$



$$\begin{cases} I_2 = I_1 + 1 \end{cases}$$

$$\begin{cases} -j + 6jI_2 - ZI_1 = 0 & -j + 6j(I_1 + 1) - (2-2j)I_1 = 0 \end{cases}$$

$$-j + 6jI_1 + 6j - 2I_1 + 2jI_1 = 0$$

$$6jI_1 - 2I_1 = -3j \quad I_1(6j-2) = -3j \quad I_1 = -\frac{9}{20} + \frac{3}{20}j$$

$$|I_1| = \frac{3\sqrt{10}}{20} \text{ A}$$

$$|I_2| = \frac{\sqrt{130}}{20} \text{ A}$$

$$I_2 = \frac{11}{20} + \frac{3}{20}j$$

Condensatori $Q_{C1} = \frac{1}{2} \begin{pmatrix} -6 \\ j \end{pmatrix} \left(\frac{\sqrt{130}}{20} \right)^2 = -\frac{13}{20} \text{ VAR}$

$$V_L + V_R - V_C = 0$$

$$\begin{cases} 2I_3 + 2I_3 + 2jI_4 = 0 \end{cases}$$

$$\begin{cases} I_3 + I_4 = I_1 = -\frac{9}{20} + \frac{3}{20}j & I_4 = -\frac{9}{20} + \frac{3}{20}j - I_3 \end{cases}$$

$$2jI_3 + 2I_3 + 2j\left(-\frac{9}{20} + \frac{3}{20}j - I_3\right) = 0$$

$$\cancel{2jI_3} + 2I_3 - \frac{9}{10}j - \frac{3}{10} - \cancel{2jI_3} = 0 \quad I_3 = \frac{3}{20} + \frac{9}{20}j \quad |I_3| = \frac{3\sqrt{10}}{20}$$

$$I_4 = -\frac{9}{20} + \frac{3}{20}j - \frac{3}{20} - \frac{9}{20}j = -\frac{3}{5} - \frac{3}{10}j \quad |I_4| = \frac{3\sqrt{5}}{10}$$

$$\text{Resistore } P_R = \frac{1}{2} 2 |I_3|^2 = \frac{9}{40} \text{ W}$$

$$\text{Induttore } Q_L = \frac{1}{2} 2j |I_3|^2 = \frac{9}{40} (j) \text{ VAR}$$


$$\text{Condensatore } Q_C = \frac{1}{2} (-2j) |I_4|^2 = -\frac{9}{20} (j) \text{ VAR}$$

$$\text{Generatore corrente } \bar{P}_I = \frac{1}{2} \left(-4j \left(\frac{11}{20} + \frac{3}{20}j\right)\right)(1) =$$

$$-j \left(\frac{11}{10} + \frac{3}{10}j\right) = -\frac{11}{10}j + \frac{3}{10}$$


$$\text{tensione } \bar{P}_T = \frac{1}{2} (-j) \left(-\frac{9}{20} - \frac{3}{20}j\right) = -\frac{3}{40} + \frac{9}{40}j$$

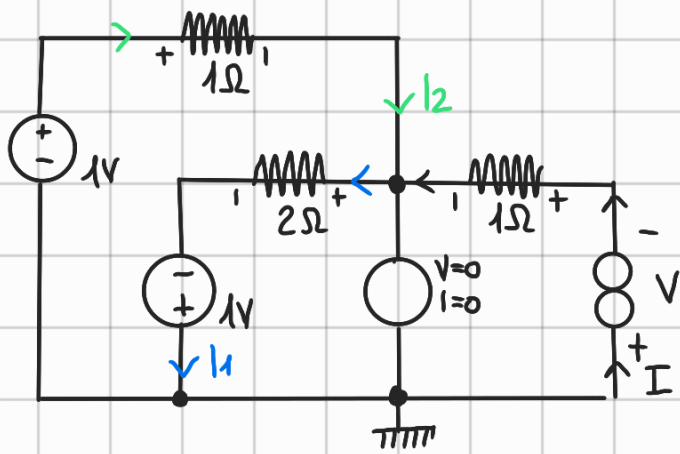9 NOV 2006 es.2 Verifica il teorema di Tellegen OK



$$P = V \cdot I$$

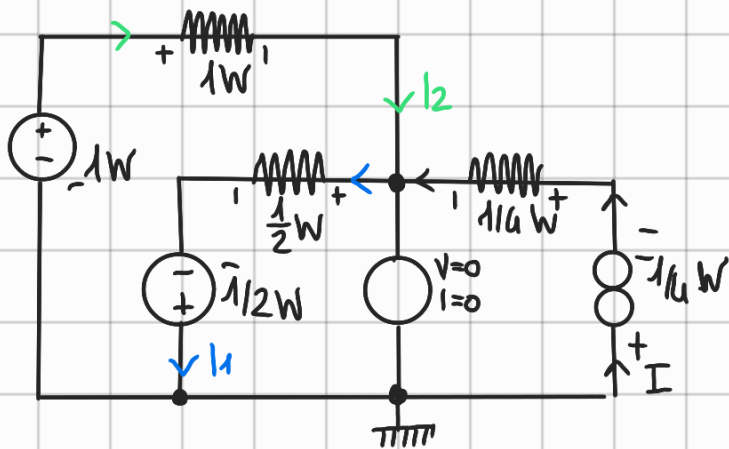
$$\begin{aligned} \text{KI} \quad & I_2 + I = I_1 \quad I = -1/2 \text{ A} \\ \text{KV} \quad & +1I + V = 0 \quad V = -1\left(-\frac{1}{2}\right) = 1/2 \\ & +1 - 2I_1 = 0 \quad I_1 = 1/2 \text{ A} \\ & 2I_1 - 1 - 1 + I_2 = 0 \quad I_2 = 1 \text{ A} \end{aligned}$$



$$\begin{aligned} P_{gv} &= 1 \cdot I_2 = 1 \\ P_{R1} &= R I_2 I_2 = 1 \cdot 1 = 1 \\ P_{R2} &= R I_1 I_1 = 2 \cdot \frac{1}{2} = 1/2 \\ P_g &= 1 I_1 = 1/2 \\ P_{R1} &= R I I = 1 \left(-\frac{1}{2}\right) \left(-\frac{1}{2}\right) = \frac{1}{4} \\ P &= V I = \frac{1}{2} \left(-\frac{1}{2}\right) = -\frac{1}{4} \end{aligned}$$

$$-1 + 1 + \frac{1}{2} - \frac{1}{2} + \frac{1}{4} - \frac{1}{4} = 0 \quad \checkmark$$

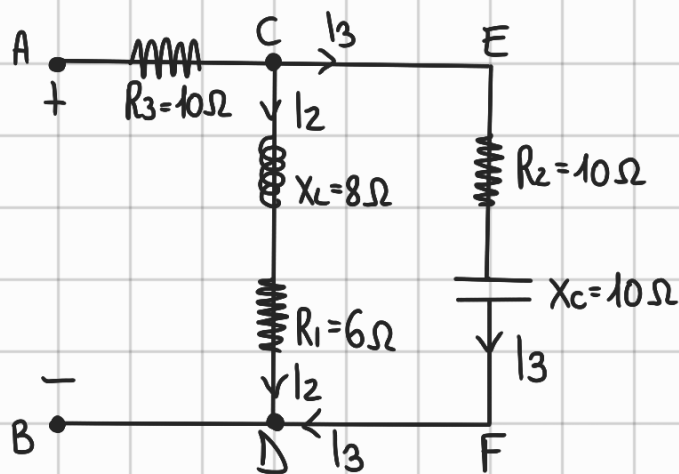22006 es1 Determina tramite Boucherot P e Q di AB OK



$$Q_C = -10^3 \text{ VAR}$$

Trovo I_3 $Q_C = X_C |I_3|^2 \rightarrow |I_3|^2 = \frac{Q_C}{X_C} = \frac{10^3}{10} = 10^2 \quad I_3 = 10 \text{ Aeff}$

$$P_2 = R_2 |I_3|^2 = 10 \cdot 10^2 = 1000 \text{ W}$$

$$V_C = X_C I_3 = 10 \cdot 10 = 100 \text{ Veff} \quad V_2 = R_2 I_3 = 10 \cdot 10 = 100 \text{ Veff}$$

$$V_{CD} = (V_C + V_2) = \frac{200}{\sqrt{2}} = 141,42 \text{ Veff}$$

$$A_{EF} = \sqrt{Q_C^2 + P_2^2} = \sqrt{10^3 + 1000^2} = 1414,21 \text{ VA}$$

$$A = V I \sim V = \frac{A_{EF}}{I_3} = \frac{1414,21}{10} = 141,42 \text{ Veff}$$

$$V_{EF} = V_{CD} = 141,32 \text{ Veff}$$

$$Q_L = X_L I_2^2 = \frac{V_L^2}{X_L} \quad P_1 = R_1 I_2^2 = \frac{V_1^2}{R_1}$$

$$A_{CD} = \sqrt{Q_L^2 + P_1^2} = \frac{V_{CD}}{I_2} \Rightarrow \sqrt{(X_L I_2^2)^2 + (R_1 I_2^2)^2} = \frac{V_{CD}}{I_2}$$

$$\sim X_L^2 I_2^4 + R_1^2 I_2^4 = \frac{V_{CD}^2}{I_2^2} \sim \sqrt{X_L^2 + R_1^2} I_2^2 = \frac{V_{CD}}{I_2}$$

$$X_L^2 I_2^2 + R_1^2 I_2^2 = V_{CD}^2 \quad I_2^2 (X_L^2 + R_1^2) = \frac{V_{CD}^2}{I_2^2}$$

$$I_2 = \sqrt{\frac{V_{CD}^2}{X_L^2 + R_1^2}} = \sqrt{\frac{(141,32)^2}{8^2 + 6^2}} = 14,13 \text{ Aeff}$$

$$Q_L = X_L I_2^2 = 8 (14,13)^2 = 1597,7 \text{ VAR}$$

$$P_1 = R_1 I_2^2 = 6 \cdot (14,13)^2 = 1197,96 \text{ W}$$

$$Q_{AB} \Rightarrow Q_L - Q_C = 1597,7 - 1000 \approx 600 \text{ VAR}$$

$$P_{CD} = P_1 + P_2 = 1197 + 1000 = 2197 \text{ W}$$


$$A = \sqrt{Q_{AB}^2 + P_{CD}^2} = \sqrt{2197^2 + 600^2} = 2277 \text{ VA}$$

$$A = VI \quad I = \frac{A}{V} = \frac{2277}{141,32} = 16,11 \text{ A}_{eff}$$

$$P_{R3} = 10 \cdot 16,11^2 = 2595,32 \text{ W}$$

$$P_{Tot} = 2197 + 2595,32 = 4792,32 \text{ W}$$

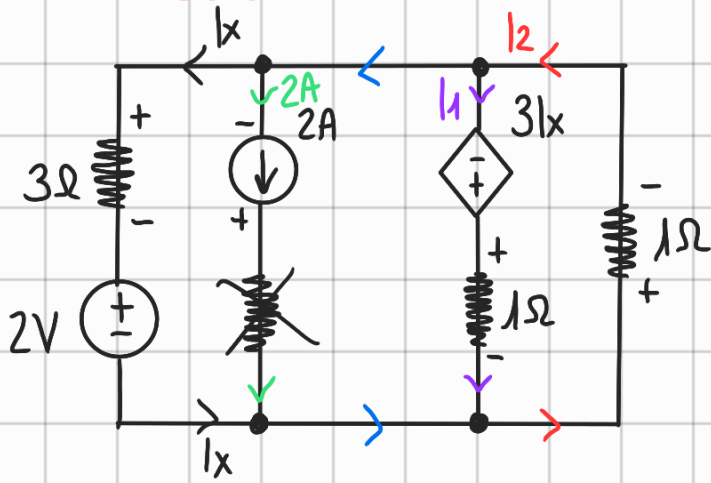16 DIC 2006 ES2 OK Determina la potenza erogata dal generatore contr.



$$K1: +I_x + 2 + I_1 = I_2$$

$$KV: +V_c + 2V + 3I_x = 0$$

$$-3I_x + 1I_1 + V_c = 0$$

$$-1I_2 - 1I_1 + 3I_x = 0$$

$$I_x = I_2 - I_1 - 2$$

$$V_c = -2 - 3(I_2 - I_1 - 2) = -2 - 3I_2 + 3I_1 + 6 = 3I_1 - 3I_2 + 4$$

$$\begin{cases} -3(I_2 - I_1 - 2) + 1I_1 + 3I_1 - 3I_2 + 4 = 0 \\ -I_2 - I_1 + 3(I_2 - I_1 - 2) = 0 \end{cases}$$

$$\begin{cases} -3I_2 + 3I_1 + 6 + 1I_1 + 3I_1 - 3I_2 + 4 = 0 \\ -I_2 - I_1 + 3I_2 - 3I_1 - 6 = 0 \end{cases}$$

$$\begin{cases} -3I_2 + 3I_1 + 6 + 1I_1 + 3I_1 - 3I_2 + 4 = 0 \\ -I_2 - I_1 + 3I_2 - 3I_1 - 6 = 0 \end{cases}$$

$$\begin{cases} -3I_2 + 3I_1 + 6 + 1I_1 + 3I_1 - 3I_2 + 4 = 0 \\ -I_2 - I_1 + 3I_2 - 3I_1 - 6 = 0 \end{cases} \quad -4I_1 + 2I_2 - 6 = 0 \quad 2I_2 = 6 + 4I_1$$

$$\bullet I_2 = 3 + 2I_1$$

$$7I_1 - 6I_2 + 10 = 0$$

$$7I_1 - 18 - 12I_1 + 10 = 0$$

$$-5I_1 = 8$$

$$I_1 = -8/5 \text{ A}$$

$$I_2 = -1/5 \text{ A}$$


$$I_x = -\frac{1}{5} + \frac{8}{5} - 2 = -\frac{3}{5} \text{ A}$$

$$V_x = 3I_x = -9/5 \text{ V}$$

$$P = V I = -\frac{9}{5} \cdot \left(-\frac{3}{5}\right) = \frac{27}{25} \text{ W}$$



16 DIC 2006 ES 2 Trova Qe P del carico RC OK
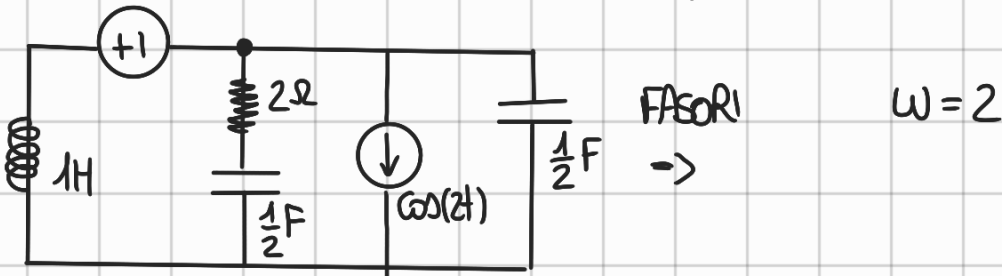
$$\sqrt{2} \sin(2t - \pi/4) = \sqrt{2} \cos(2t - \frac{3\pi}{4})$$



FASORI
→

$$\omega = 2$$

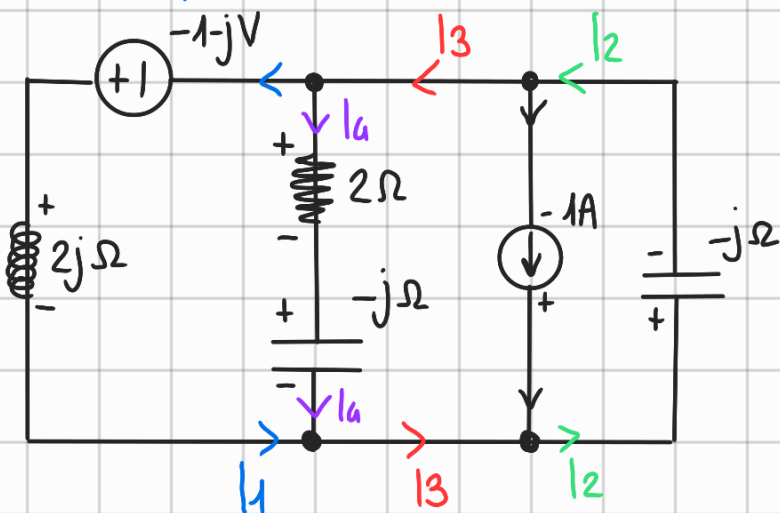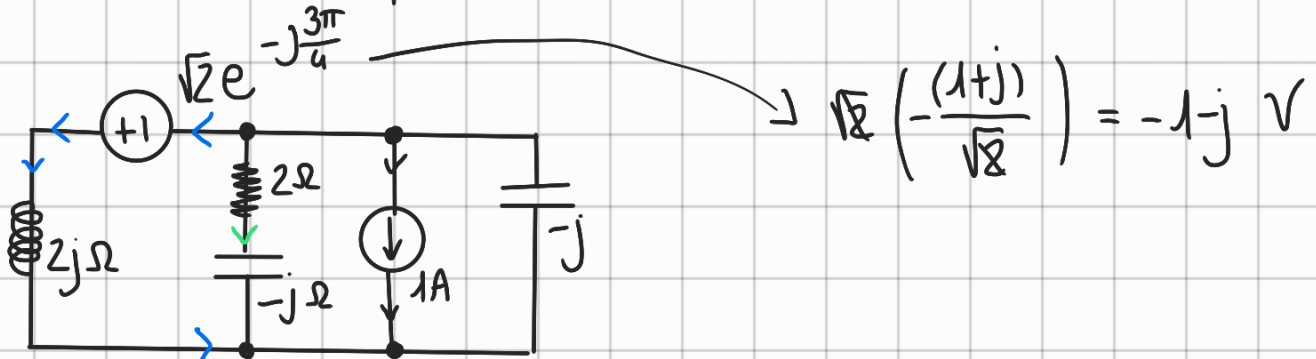

$$KI \quad I_1 - I_a - 1 + I_2 = 0$$

$$\bullet \quad I_1 + I_2 = 1 + I_a$$

$$KV \quad \begin{cases} 2I_a - jI_a - 2jI_1 - 1 - j = 0 \\ +jI_2 + jI_a - 2I_a = 0 \\ I_1 + I_2 = 1 + I_a \end{cases} \quad \begin{cases} (2-j)I_a - 2jI_1 - 1-j = 0 \\ jI_2 + (j-2)I_a = 0 \\ I_a = I_1 + I_2 - 1 \end{cases}$$

$$x \quad I_1 = -\frac{3}{61} + \frac{28j}{61}$$

$$y \quad I_2 = \frac{55}{61} - \frac{5j}{61}$$



$$z \quad I_a = -\frac{9}{61} + \frac{23j}{61} \rightsquigarrow$$

$$|I_a| = 0,40$$

$$P_R = \frac{1}{2} 2 \cdot |I_a|^2 = 0,16 \text{ W} \quad \checkmark$$

$$Q_C = \frac{1}{2} (-1) |I_a|^2 = -0,08 \quad \checkmark$$

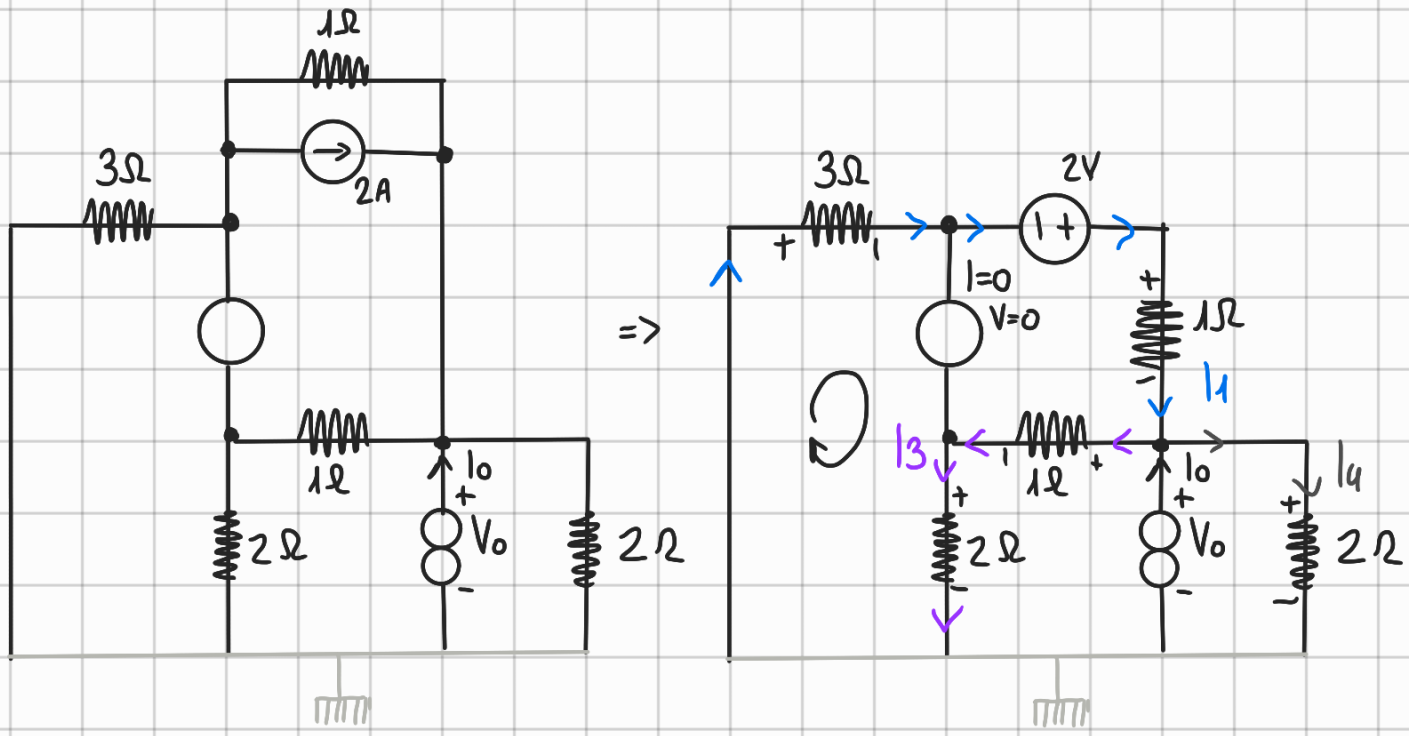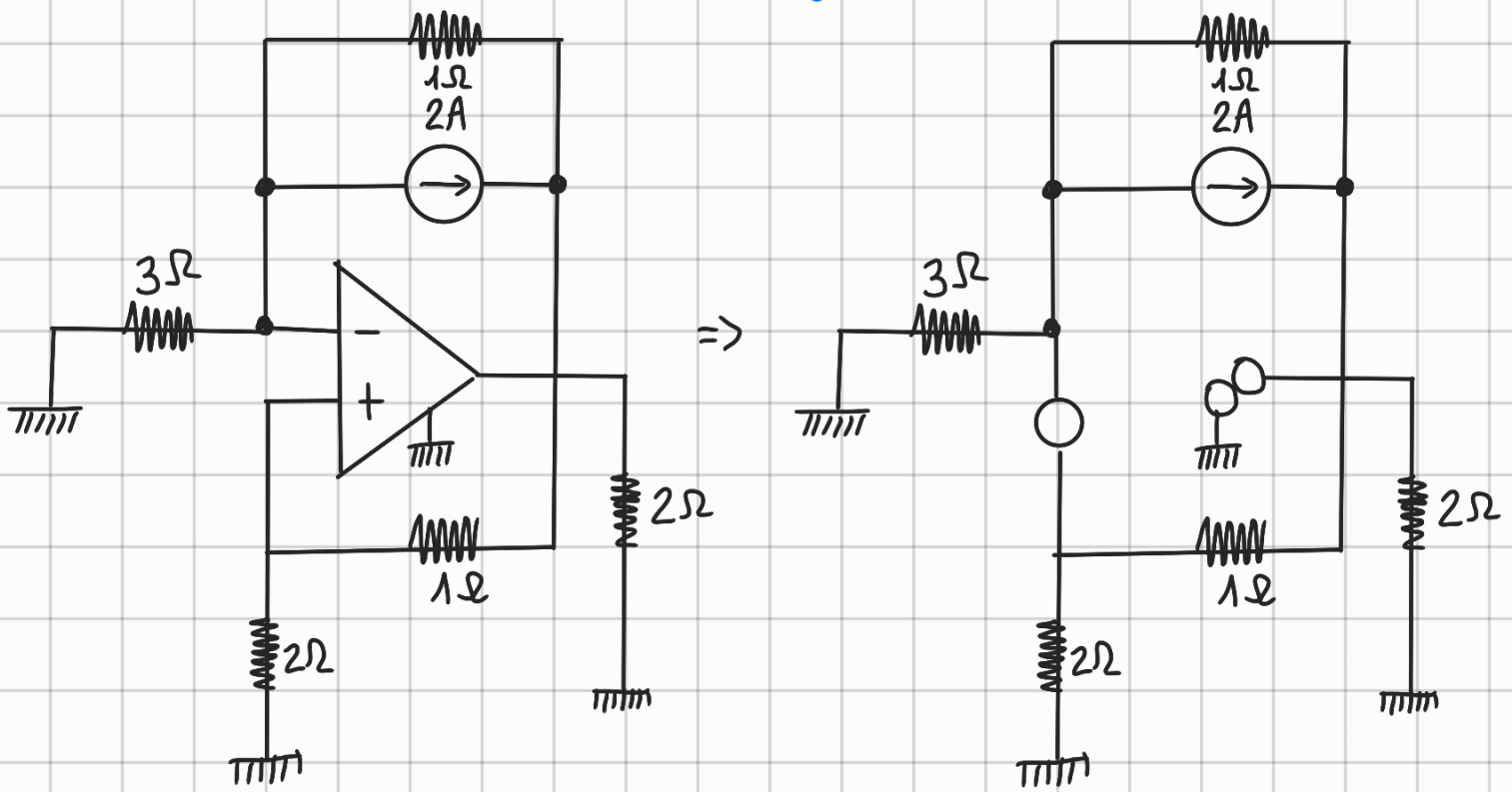3 2006 es2 Determina $P_{di\ ao}$ e P_{del} generatore di corrente



$$\begin{aligned}
 & \begin{cases} 2I_3 + 3I_1 = 0 \\ I_0 + I_1 = I_3 + I_4 \\ 2I_4 - 2I_3 - 1I_3 = 0 \\ -2 + 1I_4 + 1I_3 = 0 \\ 2I_4 - 3 \cdot 6 = 0 \\ 2I_4 = 18 \\ I_4 = 9A \end{cases} \\
 & \begin{cases} 2I_4 - V_0 = 0 \cdot V_0 = 2I_4 \\ I_1 = \frac{-2I_3}{3} = -6A \\ -6 - 2I_3 + 3I_3 = 0 \\ -2 - \frac{2}{3}I_3 + I_3 = 0 \\ I_3 = 6A \end{cases} \\
 & I_0 = 19A \quad P = I_0 V_0 = 19 \cdot 18 = 342W \quad V_0 = 18V
 \end{aligned}$$