

RISULTATI PROVE SCRITTE DI ELETTROTECNICA

1/4

19 MARZO '97 A.A. 95/96 e 96/97

1) $P_{AA} \approx 8466 \text{ W}$

$Q_{AA} \approx 5055 \text{ VAR}$

2)
$$\frac{V_o(s)}{V_g(s)} = \frac{h_{fe} R_c (1 + s R_c C)}{(R_s + h_{ie})(1 + s R_c C) + (1 + h_{fe}) R_e}$$

3) $\bar{Z}_u = 0.05 + j0.5 \Omega$
 $P_{MAX} \approx 2.49 \text{ W}$

17 FEBBRAIO '97

1) $v_u(t) = \sqrt{5} \cos(2t - 63.5^\circ) + 0.25 e^{-t}$

2) $\frac{V_u(s)}{V_i(s)} = -\frac{2}{R^2 C^2} \frac{1}{s^2 - s \frac{1}{RC} + \frac{2}{R^2 C^2}}$; instabile

3)
$$Y = \begin{bmatrix} \frac{1}{2} + \frac{1+6s^2}{2s(5s^2+1)} & \frac{s}{5s^2+1} - \frac{1}{2} \\ \frac{s}{5s^2+1} - \frac{1}{2} & 1 + \frac{2s}{5s^2+1} \end{bmatrix}$$

16 DICEMBRE '96

1) $v(t) = \frac{10}{\sqrt{3}} e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t - 30^\circ\right)$

2) $V_{eq} = -\frac{5}{2} \text{ V} ; R_{eq} = 15 \Omega$

23 OTTOBRE '96

$$1) i(t) = \frac{5}{3} + \frac{2}{3} e^{-\frac{3}{10}t} \text{ A}; t \geq 0$$

$$2) \bar{P}_C = 35'000 + j 24'000 \text{ W}$$

$$3) \frac{I_0}{I_1} = -\frac{R_3}{R_1}; \quad Z_{in} = R_1 \frac{s}{s - \frac{1}{R_1 C_1}}$$

2 OTTOBRE '96

$$1) \bar{V}_{eq} = 2.87 + j 0.0264 \text{ V}$$


$$\bar{Z}_{eq} = 1.385 + j 0.923 \Omega$$

$$2) v_{op}(t) = \frac{3}{2} e^{-\frac{3}{8}t} u(t) \quad (\text{libera})$$

$$v_{oa}(t) = \left(2 - \frac{3}{2} e^{-\frac{3}{8}t}\right) u(t) \quad (\text{forzata})$$

$$3) \quad \bar{Z} = \frac{1}{s(4s-1)} \begin{bmatrix} 12s^2 - s - 1 & 2s - 1 \\ 2s - 1 & 2s - 1 \end{bmatrix}$$

$\bar{Z}$ reciproca.

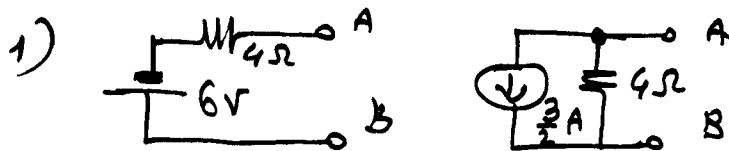18 SETTEMBRE '96

$$2) \bar{P}_C(i(t)) \simeq 841 + j 2201 \text{ W}$$

$$\bar{P}_C(i_o(t)) \simeq 1390 - j 29'500 \text{ W}$$

$$3) \quad Y = \frac{1}{2(2s+3)} \begin{bmatrix} 6s+5 & -(6s+3) \\ -(6s+3) & 8s+3 \end{bmatrix}; \quad T_v(s) = \frac{5(6s+3)}{44s+21}$$

17 LUGLIO 96

3/4

$$1) v_o(t) = \cos(5t - 121^\circ) + 2.015 e^{-\frac{t}{8}} \quad t \geq 0$$

$$2) \frac{V_o}{V_i} = \frac{1}{R_s} \frac{g_m + \frac{1}{R_o}}{\left(g_m + \frac{1}{R_s} + \frac{1}{R_1} + \frac{1}{R_o}\right) \frac{1}{R_L} + \left(\frac{1}{R_s} + \frac{1}{R_1}\right) \frac{1}{R_o}}$$

$$R_L = R_o + (1 + g_m R_o) R_s \parallel R_1 \quad (\text{massima potenza})$$

$$3) \begin{bmatrix} A & B \\ C & D \end{bmatrix} = - \begin{bmatrix} n & n s L \\ n s C + \frac{1}{n R} & n s^2 L C + \frac{1}{n} \left(\frac{s L + R}{R} \right) \end{bmatrix}$$

È reciproca

19 GIUGNO 96

$$1) \frac{V_1}{V_{in}} = - \frac{s^2}{s^2 + s \frac{2}{RC} + \frac{1}{R^2 C^2}} \quad ; \quad \text{passo alto}$$

$$2) \underline{\underline{Z}} = \begin{bmatrix} 5 & 4(s+1) \\ 2 & 2(2s+1) \end{bmatrix} \frac{1}{6s+1} \quad \text{Non reciproca.}$$


$$3) P_{AA} \approx 9900 \text{ W}$$

$$Q_{AA} \approx 2370 \text{ VAR}$$

29 MAGGIO 96

$$1) \underline{\underline{Z}}_u = \frac{29 + j3}{10} \Omega$$
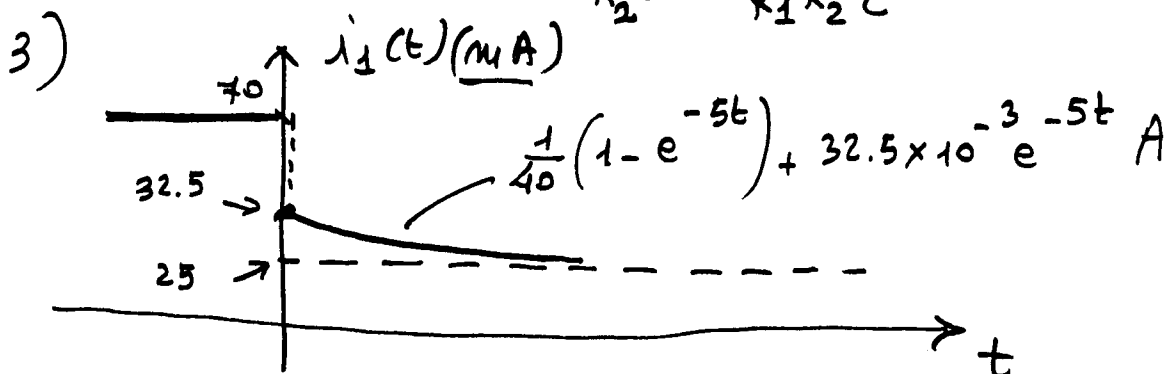
$$2) \frac{V_o}{V_i} = \frac{R_2}{2R_1 + R_2} \frac{s^2 + \frac{1}{R_1 R_2 C^2}}{s^2 + 2 \frac{s}{R_2 C} + \frac{1}{R_1 R_2 C^2}} \quad ; \quad \text{Elimina Banda.}$$




19 FEBBRAIO 96

4/4

1) $Z_{in}(s) = \frac{1}{s^2 R C^2}$

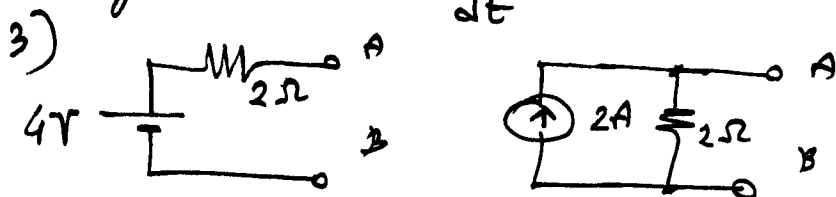2) $v_2(t) = E_0 \left(1 - e^{-\frac{t}{\tau}}\right) + E_0 \frac{C_1}{C_1 + C_2} e^{-\frac{t}{\tau}} ; \tau = R(C_1 + C_2)$

$i_{generatore} = C_2 \frac{dv_2}{dt} = \dots$



4 GENNAIO 96

1) $\frac{V_M}{V_i} = \frac{s^2 + s \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_1 C_2} \right) + \frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$

$Z_M(s) = 0 \Omega$

2) $i(t) = 10e^{-\frac{t}{2}} \left(u(t) - u(t-1) \right) + \left[5 + 1.1e^{-(t-1)} \right] u(t-1)$

3) $P_g \approx 0.155 \text{ W} \quad Q_g \approx 0.289 \text{ VAR}$
 $Q_{L1} \approx 0.269 \text{ VAR} ; Q_{L2} \approx 0.020 \text{ VAR}$

19 MARZO 96

1) $T_V(s) = \frac{s^2 R_1 R_2 C_1 C_2}{s^2 R_1 R_2 C_2 C_3 + s R_1 (C_1 + C_2 + C_3) + 1}$

Passo alto.

2) $V_{eq} = \frac{3}{2} \text{ V} ; R_{eq} = \frac{5}{2} \Omega$

$\bar{P}_C = -0.62 + j0.27 \quad P_D = \frac{9}{80} \text{ W} \quad P_C = 0.061 \text{ W}$

$P_R = 0.051 \text{ W}$

3) $H(s) = I(s)/V_g(s) = \frac{6s}{54s^2 + 4s + 1} \Rightarrow \text{circuito A.S.}$

$i(t) = 0.557 \cos(2t + 2.16^\circ) \text{ A}; (\text{a regime})$

RISULTATI PROVE SCRITTE DI ELETTROTECNICA 1/3
A.A. 1997/98

29 MAGGIO 1997

- 1) $V_{0 \text{ forata}} = 2 - \frac{4}{7} e^{-\frac{50}{21} t}$ $V_{0 \text{ libera}} = -\frac{20}{7} e^{-\frac{50}{21} t}$
- 2) $\bar{Z}_{cavo} = \frac{1}{2} + j \frac{1}{6} \Omega$ $P_{MAX} \simeq 0.236 W$
- 3) $V_0 = \left(1 + \frac{R_2}{R_1}\right) (V_{g2} - V_{g1})$; $P_{A.O.2} \simeq 1.2 mW$

18 GIUGNO 1997


- 1) $\bar{P}_c = \frac{1}{10} (3 + j4) W_{\text{generatore}} e(t)$
 $\bar{P}_c = \frac{1}{10} (7 + j9) W_{\text{generatore}} i_0(t)$
- 2) $v_u(t) = r(t) - p(t-1) + p(t-3) + r(t-3)$
 $r(t) = \frac{1}{2} (1 + e^{-t/3})$; $p(t) = \frac{1}{2} t - \frac{3}{2} [e^{-t/3} - 1]$
- 3) $g_{11} = \frac{1}{\Delta}$; $g_{21} = \frac{R_2 (1 + k_2)}{\Delta}$
 $g_{22} = \frac{R_1 R_2}{\Delta}$; $g_{12} = -\frac{R_2 (1 - k_1)}{\Delta}$
 $\Delta = R_1 + R_2 (1 - k_1)(1 + k_2)$

17 SETTEMBRE 1997

- 1) $i(t) = \frac{1}{7} e^{-\frac{15}{7} t} u(t)$

$$2/3$$

$$- 3.33 t$$

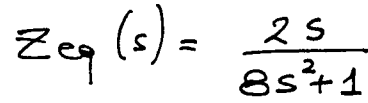

3) $\bar{P}_c \approx 6.3 + j 33 \text{ W}$ sul carico

$P_c = 6.3 + j 50.1 \text{ W}$ erogata dal generatore

1) $v(t) = 19 \cos\left(\frac{1}{\sqrt{2}} t\right) u(t) \text{ V}$



$$P_{MAX} \approx 8.27 \text{ W}$$

$$1) i_c(t) \approx -0.25 e^{-\frac{3}{2}t} + 4.47 \cos(3t + 26.6^\circ) A, t \geq 0$$

$$2) \quad V_{eq}(s) = V_i(s) \frac{1}{R_1} \frac{sC_2 - k}{s^2 C_1 C_2 + sC_2 (G_{12} + k)}$$

$$Z_{eq}(s) = \frac{G_{12} + s(C_1 + C_2)}{s^2 C_1 C_2 + s C_2 (G_{12} + k)}$$

$$G_{12} = \frac{1}{R_1} + \frac{1}{R_2}$$

9 MARZO 1998

$$1) a) H(s) = -\frac{1}{RC} \frac{s}{s^2 + \frac{2}{RC}s + \frac{1}{R^2 C^2}}$$

b) Filtro passa banda

c) stabilità asintotica

$$d) v_o(t) = 0.4 \cos(t + 143^\circ) \text{ V}$$

$$2) v_1(t) = 10 \left(1 - e^{-\frac{t}{4.8}}\right) + \frac{20}{3} e^{-\frac{t}{4.8}}$$


$$i_{c1}(t) = -\frac{20}{3} \delta(t) + \frac{25}{18} e^{-\frac{t}{4.8}} u(t) \text{ A}$$

$$E_{\text{tot}}(0^-) = 100 \text{ joule}; E_{\text{tot}}(0^+) = 66.7 \text{ joule}$$

$$E_{\text{tot}}(\infty) = 150 \text{ joule}.$$

29 OTTOBRE 1997

$$1) \bar{Z} = 4 + j8 \Omega$$

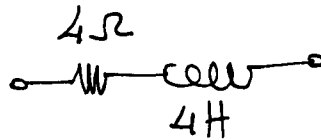

$$2) \frac{V_L}{V_g} = -\frac{\mu R_L}{R_L + R_p + (1 + \mu) R_k}$$

$$3) A-A \text{ aperti: } \varphi \simeq 6.9$$

$$A-A \text{ in corto circuito: } \varphi \simeq 15.9$$

16 LUGLIO 1997

$$1) \underline{\underline{Z}} = \begin{bmatrix} j9 & 0 \\ 0 & -j3 \end{bmatrix}$$

$$P_{\text{generatore}} = 0 \text{ W}$$

$$\varphi_{\text{generatore}} = 4.5 \text{ VAR}$$

$$2) i(t) \simeq 0.523 e^{-t} \cos(3t - 18.9^\circ) \text{ A}$$

$$3) v_2(t) = e^{-t} + e^{-\frac{1}{2}t} \left(-\cos \frac{\sqrt{3}}{2} t + \frac{\sqrt{3}}{3} \sin \frac{\sqrt{3}}{2} t \right) \quad t \geq 0$$

RISULTATI PROVE SCRITTE DI ELETTROTECNICA

DELL' A.A. 1998/99

1/3

27 MAGGIO 98

1) a) $\bar{P}_c = 484 - j242 \text{ W}$

b) $\bar{P}_c = 484 + j569 \text{ W}$; $\phi_H \approx 0.01 \text{ Wb}$ (a) e b))

2) $i_x = -\frac{22}{7} \text{ A}$ 3) $v_c(0^+) = 7 \text{ V}$; $i_2(0^+) = 5 \text{ A}$.

22 GIUGNO 98

1) $V_{eq} = 2 \text{ V}$; 2) $R_{eq} = -500 \Omega$;

Non ha senso parlare di carico che assorbe la massima potenza attiva.

2) $\bar{P}_c$ (esposta da $i_0(t)$) = $1 + j2 \text{ WATT}$

$\bar{P}_c$ (esposta da $e(t)$) = 1 WATT

3) Risposta forata a $x(t)$:

$$y_1(t) = -\frac{15}{39} e^{-\frac{5t}{39}} u(t) + \frac{3}{39} [5 \cos(3t) + 3 \sin(3t)] u(t)$$

14 LUGLIO 98

1) Energia media contenuta in C: 0.41 joule
= dissipata su R: 1.22 joule

2) $i_L(t) = \frac{4}{3} e^{-t} - \frac{1}{3} e^{-4t} \text{ A}$ ($t \geq 0$)

3) $Z_{in}(s) = -\frac{1}{25C}$

14 SETTEMBRE 98

1) $i(t) = -g(t) + 2g(t-1) - p(t-1) + p(t-2)$, dove
 $g(t) = \frac{1}{5} (1 - e^{-\frac{5}{12}t}) u(t)$; $p(t) = \frac{1}{5} t u(t) + \frac{12}{25} (e^{-\frac{5}{12}t} - 1) u(t)$

2) Esistono solo i parametri Y, h, T :

$$Y = \begin{bmatrix} \frac{1}{R} & 0 \\ -a & 0 \end{bmatrix}; h = \begin{bmatrix} R & 0 \\ -aR & 0 \end{bmatrix}; T = \begin{bmatrix} 0 & \frac{1}{a} \\ 0 & \frac{1}{aR} \end{bmatrix}$$

3) $R_{AB} = R \parallel R_g \parallel R'_{AB}$

$$R'_{AB} = h_{ie} + (1 - h_{re})(1 + h_{fe}) R_e$$

7 OTTOBRE 98

2/3

2) $p(t) = 15 + 25 \cos(4t + 53^\circ) \text{ W}$

3) $i_c(0^+) = 2 \text{ A} ; \frac{di_c}{dt}(0^+) = -16 \text{ A/sec.}$

21 DICEMBRE 98

1) $\overline{Y}_{in} = -2(1+j) \Omega^{-1}$

2) $i_{\text{COMPLETA}}(t) \simeq -0.4e^{-4t} + 0.447 \cos(2t - 26.6^\circ) \text{ A } (t \geq 0)$

21 DICEMBRE 98 (D.U.)

1) $R_{eq} = \frac{11}{2} \Omega$; 2) $\overline{V}_{eq} = \frac{6-j^2}{5} \text{ V}$ $\overline{Z}_{eq} = \frac{3-j}{5}$
 $\overline{Z}_u = \overline{Z}_{eq}^* = \frac{3+j}{5}$; $P_{MAX} = \frac{1}{3} \text{ W.}$

13 FEBBRAIO 99

1) $P = 2.5 \text{ W} ; Q = 2.5 \text{ VAR.}$

2) $R_{eq} = 2 \Omega ; V_{eq} = \frac{E}{3}$

3) $v_{u\text{libera}}(t) = \frac{15}{2} e^{-2t} (t \geq 0) \text{ V}$

$v_{u\text{forzata}}(t) = \frac{15}{8} + \frac{25}{8} e^{-2t} \text{ V } (t \geq 0)$

$v_{u\text{permanente}}(t) = \frac{15}{8} \text{ V } (t \geq 0) ; v_{u\text{transitoria}} = \frac{25}{8} e^{-2t} \text{ V } (t \geq 0)$

1 MARZO 99

2) $i_{\text{COMPLETA}}(t) = 10e^{-2t} \cos(4t) \text{ A } (t \geq 0)$

3) $\overline{Z}_u = 3.2 + j2.4 \Omega$; $P_{MAX} \simeq 1.056 \text{ W}$

20 MARZO 99

1) $v_1(0^+) = 2 \text{ V} ; i_2(0^+) = -1 \text{ A} ;$

$v_2(0^+) = -1 \text{ V} ;$

2) $V_{eq} = -\frac{44}{3} \text{ V} ; R_{eq} = -\frac{4}{9} \Omega$

3) $v_1(t) = \frac{1}{4} [t - \frac{1}{2} \sin(2t)] u(t) \text{ V}$

26 OTTOBRE 98


3/3

1) $N \simeq 163$ spire

2) $N_{eq} = E \frac{R_2 + R_3}{R_1 + R_2}$; $R_{eq} = R_1 \frac{R_2 + R_3}{R_1 + R_2}$.

3) $\bar{Z}_u = 1 - j \Omega$;

$P_{MAX} = 0.0625 \text{ W}$

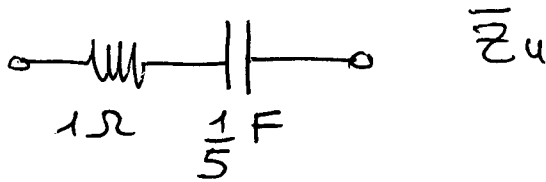

RISULTATI PROVE SCRITTE DI ELETTROTECNICA

A.A. 1999/2000

1/3

1 GIUGNO 99

$$2) i(t) = 4e^{-2t} \cos(t) - 6e^{-2t} \sin(t) \text{ A}$$

$$3) Z_{eq}(s) = sL ; Z_T(s) = 2sL.$$

23 GIUGNO 99

$$1) P_{AR} \approx 57900 \text{ W} ; Q_{AR} \approx -42000 \text{ VAR}$$

$$\cos \phi_{AR} \approx 0.81 \text{ capacitivo}$$

$$2) v_u(t) = -\frac{I_0}{C} \cos\left(\frac{1}{\sqrt{LC}} t\right) u(t)$$

14 LUGLIO 99 (C.d.L.)

$$1) v_c(t) = 5 - \frac{5}{3} e^{-t} \sin(3t) \text{ V} ; t \geq 0$$

$$2) T_v(s) = -\frac{G_1}{C_2} \frac{s}{s^2 + sG_2 \frac{C_1+C_2}{C_1C_2} + \frac{G_1G_2}{C_1C_2}}$$

$$3) \bar{Z}_u = 50(2-j) \Omega ;$$

$$P_{MAX} \approx 3.125 \text{ W}$$

14 LUGLIO 99 (D.U.)

$$2) v_u(t) \approx 3.6 e^{-1.5t} + 4.47 \cos(2t + 10.3^\circ) \text{ V}$$

16 SETTEMBRE 99

$$1) v_c(t) = 2.24 e^{-t} - 2.4 t e^{-t} + \frac{2}{5} \cos(2t + 233^\circ) \text{ V}$$

$$2) R_{eq} = \frac{3}{5} \Omega ; v_{ABeq} = -\frac{11}{2} \text{ V}$$

$$R_u = \frac{3}{5} \Omega ; P_{MAX} \approx 12.6 \text{ W}$$

6 OTTOBRE 99

2/3

$$2) \quad i_L(0^+) = 5A; \quad v_2(0^+) = 5V; \quad v_1(0^+) = -4V$$
$$\frac{dv_2}{dt}(0^+) = \frac{5}{2} V/sec$$

$$3) \quad \bar{P}_{\substack{\text{essente} \\ \text{de gen.re} \\ \text{ind. te}}} = \frac{1}{4} (1+j)$$

$$\bar{P}_{\substack{\text{essente} \\ \text{de gen.re} \\ \text{controllato}}} = -\frac{1}{2} J$$

$$Q_L = \frac{1}{4} VAR; \quad Q_C = -\frac{1}{2} VAR; \quad P_R = \frac{1}{4} W.$$

25 OTTOBRE 99

$$2) \quad i_{ABeq} = \frac{17}{6} A; \quad R_{eq} = \frac{6}{5} \Omega.$$

21 DICEMBRE 99

$$1) \quad R_{im} = \frac{h_{ie} - h_{re} h_{fe} R}{(1 + h_{fe})(1 - h_{re})}.$$

$$2) \quad v(t) \simeq 1.02 \cos(3t - 71^\circ) - 0.33 e^{-2t} \cos(3t) - 1.18 e^{-2t} \sin(3t) V$$

12 FEBBRAIO 2000

$$1) \quad v_{AB}(t) = 10 + 4e^{-3t} \cos(4t) + \frac{11}{2} e^{-3t} \sin(4t) V$$

$$2) \quad v_{eq} = \frac{35}{13} V; \quad R_{eq} = \frac{60}{13} \Omega.$$

4 MARZO 2000

3/3

$$1) \quad i_c(0^+) = -\frac{10}{7} \text{ A}$$

$$2) \quad E_{\text{MEDIA}} \simeq 0.174 \text{ joule}$$

$$3) \quad f_h(t) = \delta(t) + \frac{22}{3} u(t) - \frac{13}{3} e^{-3t} u(t).$$

25 MARZO 2000

$$1) \quad R_{eq} = \frac{RR_L}{R - AB R_L}$$

$$2) \quad i(t) = \frac{5}{4} \delta(t) + 20 u(t) - 15 e^{-2t} \cos(2t) u(t) + 20 e^{-2t} \sin(2t) u(t)$$

A.A 2000/200103/06/00

1) $C = 568 \mu F$ (Condensatore da rifasamento)

2) $V_{eq} = 0 V$ $R_{eq} = 2R$

3) $V_{eibers}(t) = \frac{5}{2} e^{-\frac{t}{\tau}}$; $V_{forzata} = -\frac{25}{12} e^{-\frac{t}{\tau}}$

$V_{trans.}(t) = -\frac{25}{12} e^{-\frac{t}{\tau}}$; $V_{perm.}(t) = 0$.

$\tau = \frac{12}{5} \text{ sec.}$

26/06/00

2) $i_c(0+) = -\frac{13}{16} A$; $i_R(0+) = -\frac{13}{32} A$

Energia dissipata ≈ 15.8 joule.

3) Potenza complessa erogata da generatore tensione: $\frac{7}{40} + j\frac{1}{40}$

Potenza complessa erogata da generatore controllato: $-\frac{1}{20} + j\frac{1}{20}$.

Potenza attiva assorbita da R: $\frac{1}{8} W$

Potenza reattiva assorbita da C: $-\frac{1}{40} VAR$

Potenza reattiva assorbita da L: $\frac{1}{10} VAR$.

19/07/00

1) $V_c(t) = -35 e^{-2t} \cos(t) - 70 e^{-2t} \sin(t) + 40 V (t \geq 0)$

2) $R_{eq} = \frac{R}{1+k}$; $V_{eq} = E \frac{2-k}{1+k}$; $k=2$.

3) $\bar{I} = 0.48 e^{-j17^\circ}$

$\bar{I}_1 = 0.2875 e^{-j17^\circ}$

$\bar{V} = 0.29 e^{j73^\circ}$

16 | 09 | 00

2 | 3

$$1) \quad v(t) = 0 \quad t \geq 0.$$

$$2) \quad \overline{P}_{(e(t))} = -0.396 - j0.073$$

$$\overline{P}_{(i_o(t))} = 1.046 - j0.77.$$

$$3) \quad R_{eq} = R \frac{3+k-2GR}{1+k-2GR}$$

7 | 10 | 00

$$1) \quad i_L(t) = \frac{5}{2} (e^{-5t} - e^{-t}) + 15 \text{ A} \quad t \geq 0$$

$$3) \quad \overline{Z}_N = 1.585 + j0.453 \Omega$$

$$P_{MAX} \approx 6.695 \text{ Watt}$$


28 | 10 | 00

$$1) \quad i_L(t) = A e^{-\frac{1}{2}t} \cos(t + \varphi) + 0.97 \cos(t + 14^\circ) \text{ A}$$


$$i_L(0+) = \frac{1}{2} \text{ A}$$

$$\frac{di_L}{dt}(0+) = \frac{1}{2} \text{ A/sec}$$

3)

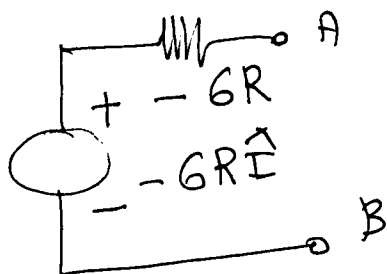

Thevenin's

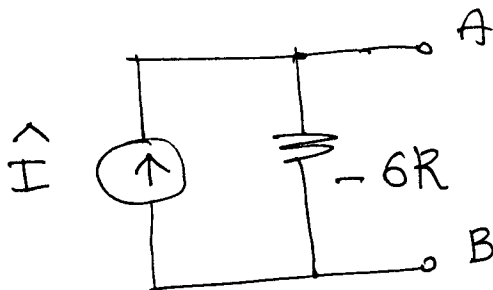

$$\frac{16}{12} / \frac{00}{00}$$

3/3

$$1) R_{eq} = R \frac{3 - 2A - 2RB}{1 - 2RAB}$$

$$2) V_{libera}(t) = \frac{8}{5} e^{-\frac{2}{5}t} \text{ V}$$

$$V_{forzata}(t) = 0.031 e^{-\frac{2}{5}t} + 0.784 \cos(2t + 11.3^\circ) \text{ V}$$

$$3) E_{trasfuso 1} \simeq 1.125 \times 10^{-2} \text{ joule}$$

$$E_{trasfuso 2} \simeq 0.375 \times 10^{-2} \text{ joule}$$

$$E_{fuso} = 0.$$

$$\frac{03}{02} / \frac{01}{01}$$

$$1) P_{MAX} \simeq 0.716 \text{ Watt}$$

$$\frac{28}{02} / \frac{01}{01}$$

$$1) v(t) = -\frac{2}{9} - \frac{1}{9} e^{-\frac{t}{\tau}} \quad t \geq 0; \quad \tau = \frac{5}{18} \text{ sec.}$$

$$2) R_{eq} = \frac{5}{2} R$$

$$\frac{17}{03} / \frac{01}{01}$$

$$1) v_c(t) = k_1 e^{-2t} + k_2 e^{-4t}$$

$$v_c(0^+) = \frac{27}{82} \text{ V}; \quad \frac{dv_c}{dt}(0^+) = -\frac{77}{41} \text{ V/sec.}$$

$$2) R_{eq} = \frac{6}{5} \Omega; \quad v_{eq} = -\frac{6}{5} \text{ V.}$$

$$3) \text{ Risposta forzata a } x(t):$$

$$2 \cos(2t) u(t) + \frac{2}{3} \sin(4t) u(t) - \frac{1}{3} \sin(2t) u(t).$$