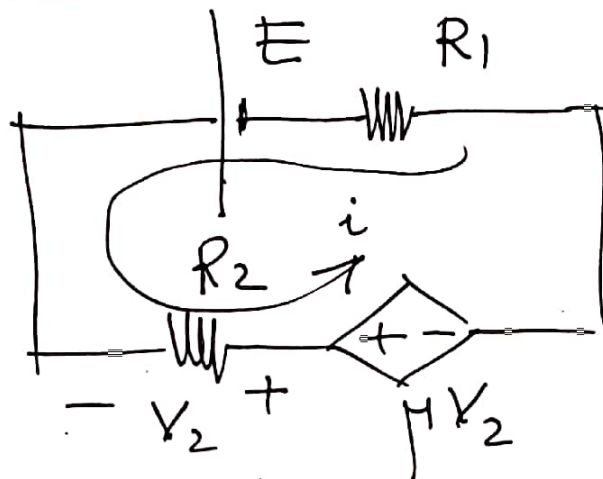


Esempio

①




? $\sqrt{2}$

Soluzione. Introduco la corrente incognita i

$$KV: -V_2 + \mu V_2 + R_1 i - E = 0$$

Elimino grandezze di controllo V_2 :

$$V_2 = -R_2 i$$

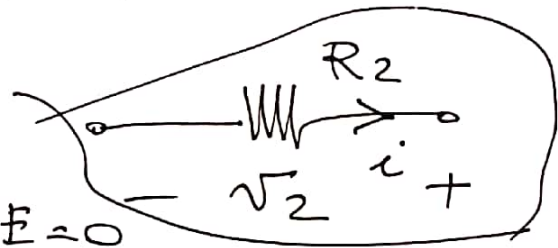

$$R_2 i - \mu R_2 i + R_1 i - E = 0$$




$$[(1-\mu)R_2 + R_1]i = E \Rightarrow$$

$$i = \frac{E}{(1-\mu)R_2 + R_1} \Rightarrow$$

$$\sqrt{2} = \frac{R_2 E}{(\mu-1)R_2 - R_1}.$$

Esercizio : Calcolare V_x usando
equivalenze per generatori.


(2)

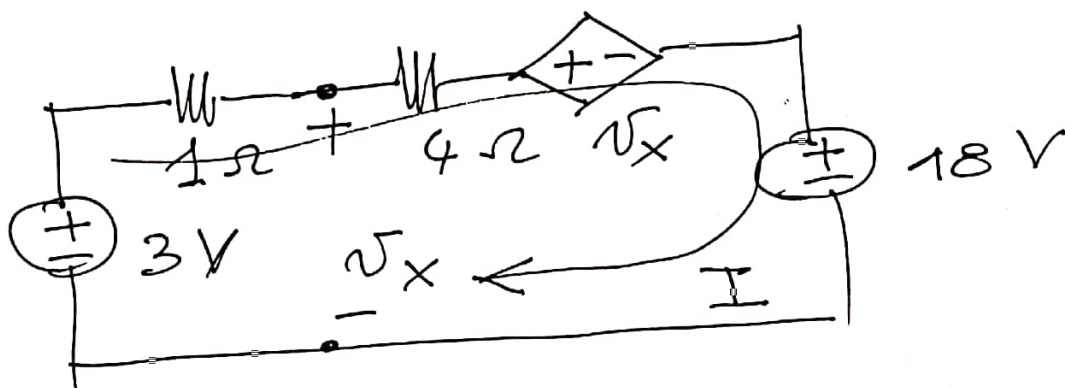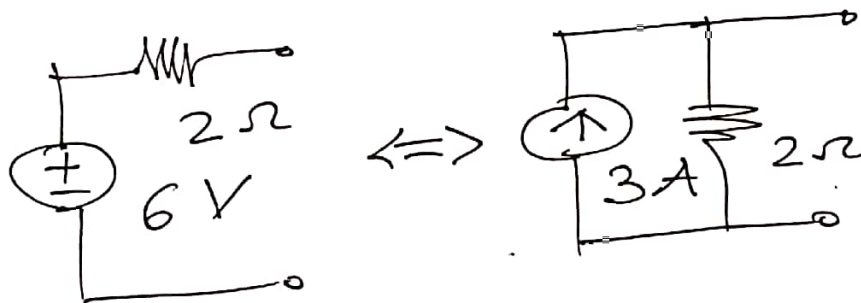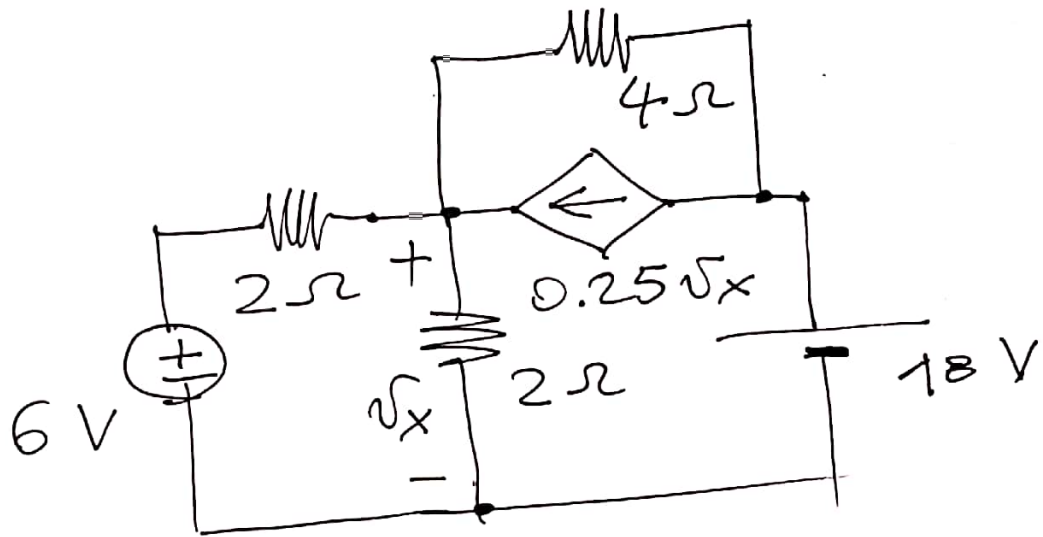

$$\begin{cases} 3 = 5I + v_x + 18 \\ v_x = -I + 3 \end{cases}$$


③

- 2 eq. in 2 incognite
- risolvendo:

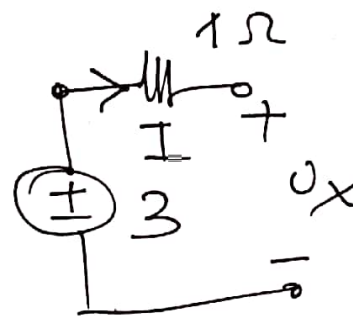

$$v_x = \frac{15}{2} \text{ Volt.}$$

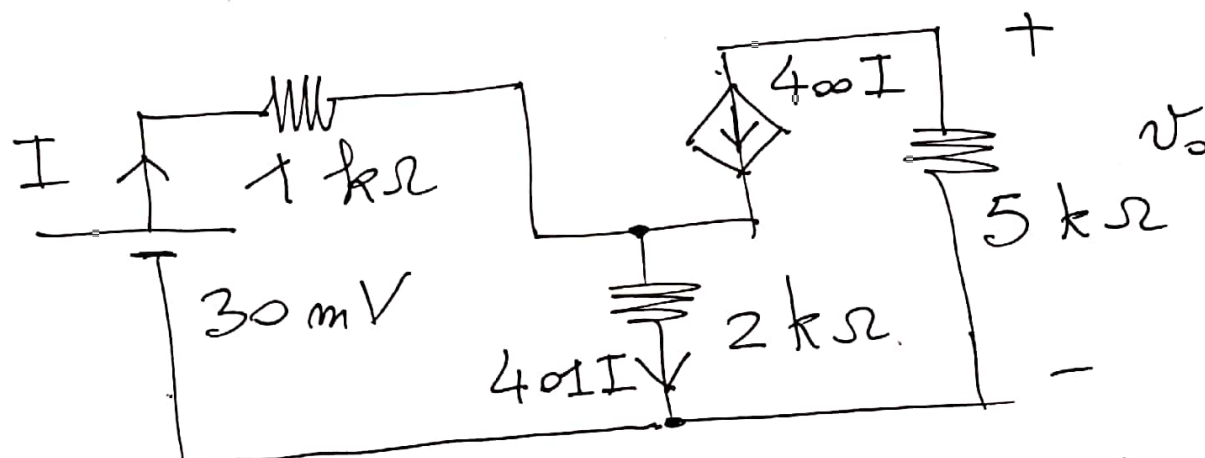Esempio Determinare v_o per il circuito a transistor.



$$\text{KV: } 30 \times 10^{-3} = 1000 I + 2000 \times 401 \times I = 803000 I \Rightarrow$$

$$I = 3.73 \times 10^{-8} \text{ Ampère}$$

$$v_o = -5000 \times 400 \times I = -0.075 \text{ V} = -75 \text{ mV}$$

