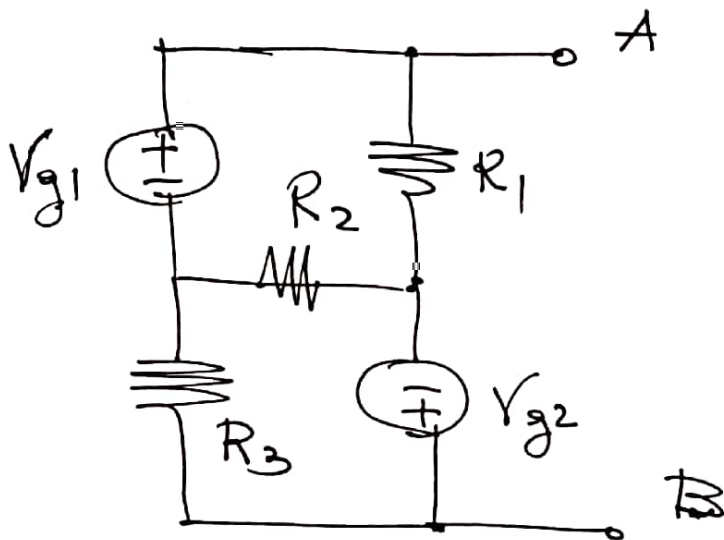


Esercizio ? Thevenin, Norton bipolo AB

①



$$R_1 = 9 \Omega$$



$$R_2 = 18 \Omega$$

$$R_3 = 6 \Omega$$

$$V_{g1} = 30 V$$


$$V_{g2} = 10 V$$

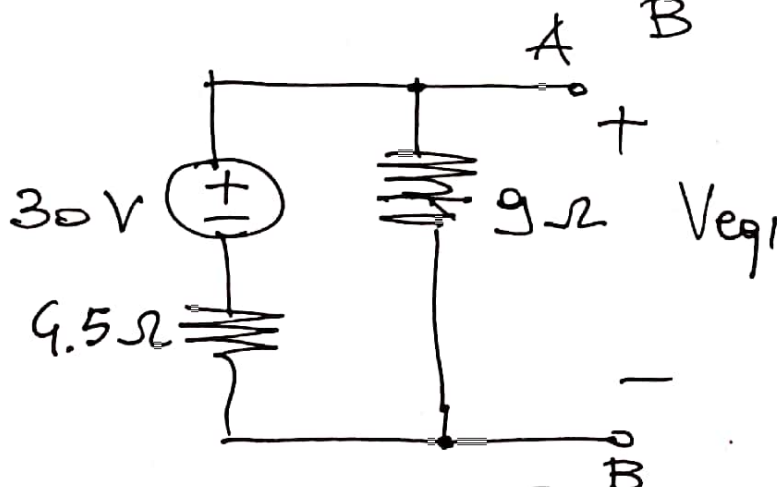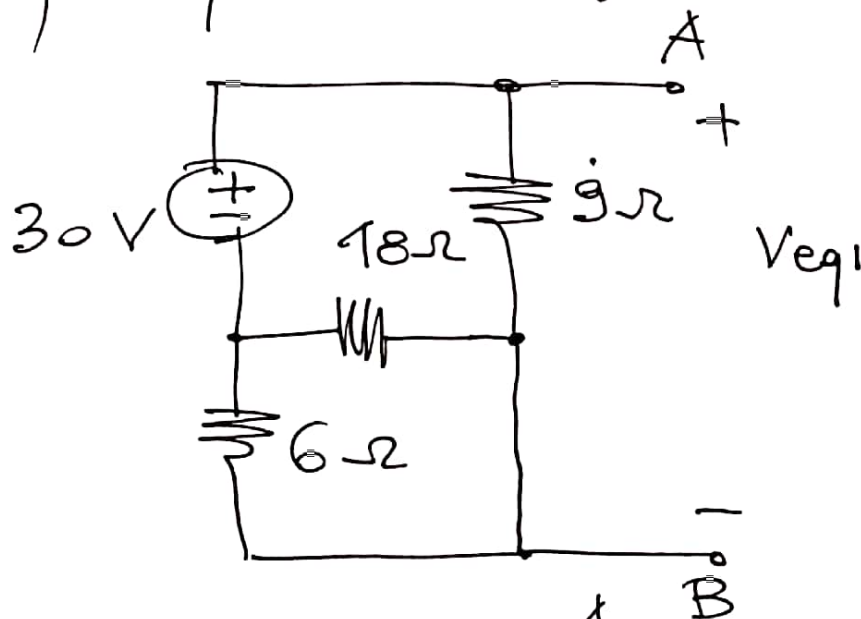Soluzioni Use p.s.e. for determine V_{eq} .





$$V_{eq1} = 30 \times \frac{9}{4.5 + 9} = 20 V$$

(2)

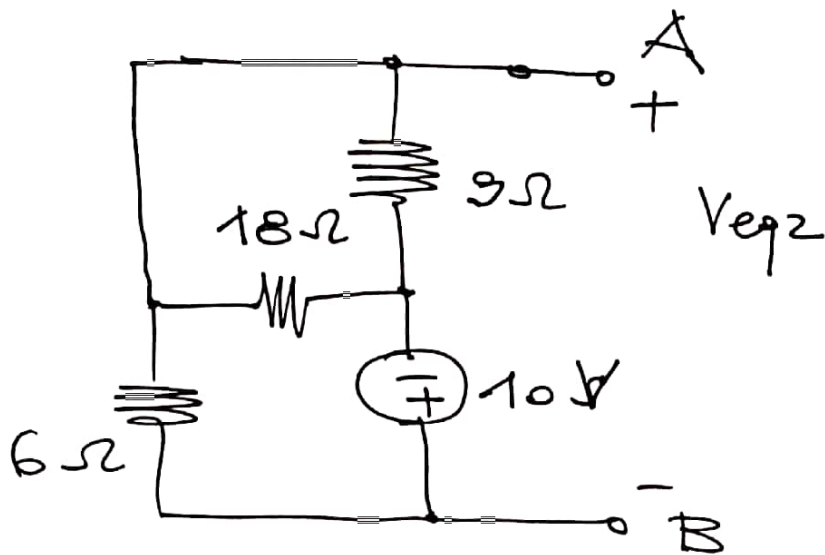

$$V_{eq2} = -10 \times \frac{6}{6+6} = -5 \text{ V}$$

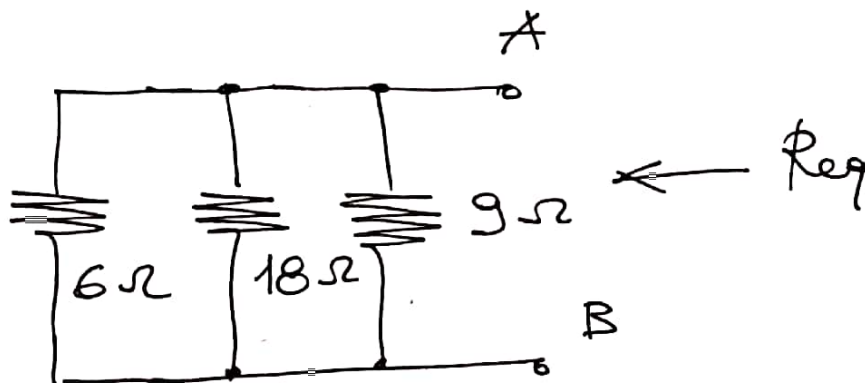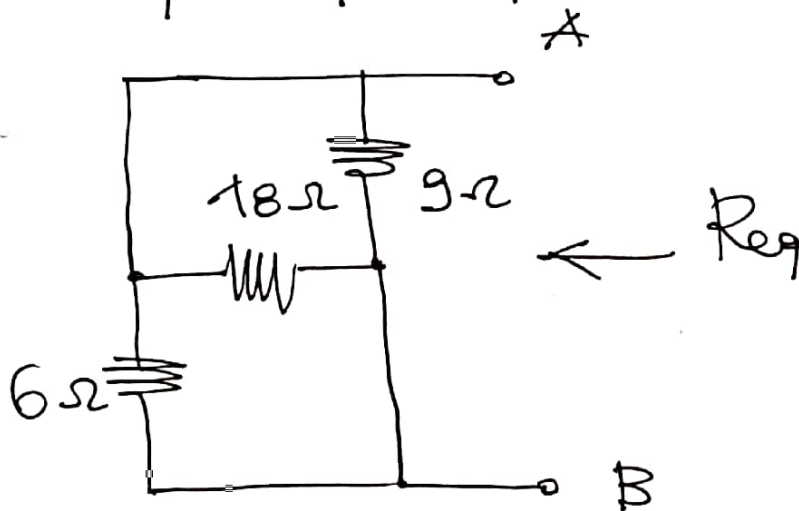
$$V_{eq} = V_{eq1} + V_{eq2} = 15 \text{ V.}$$



$$G_{eq} = \frac{1}{6} + \frac{1}{18} + \frac{1}{9} = \frac{3+1+2}{18} = \frac{1}{3} \Omega^{-1}$$

$$R_{eq} = 3 \Omega ; i_{cc} = G_{eq} V_{eq} = 5 \text{ A.}$$


Esempio ? Thevenin, Norton bipolo AB ①

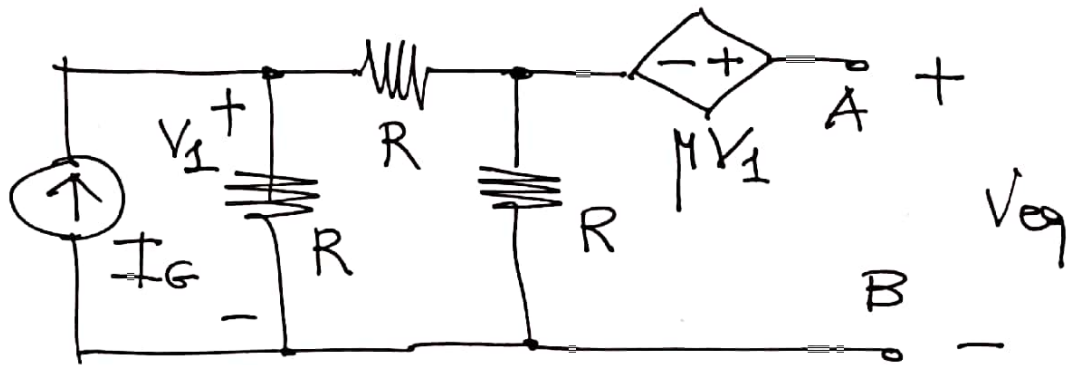


Soluzione Utilizziamo la definizione di V_{eq} e R_{eq} .

Usando partitore di corrente

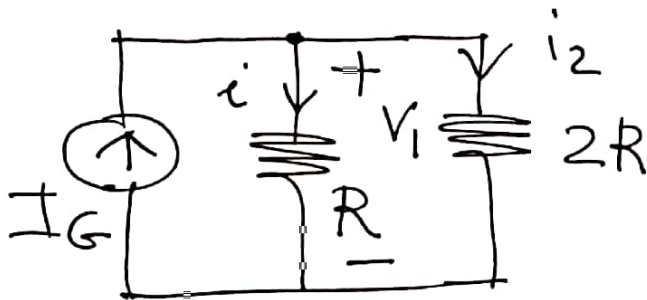
$$i_1 = \frac{2}{3} I_G, \quad i_2 = \frac{1}{3} I_G$$



quindi $V_1 = \frac{2}{3} R I_G$.

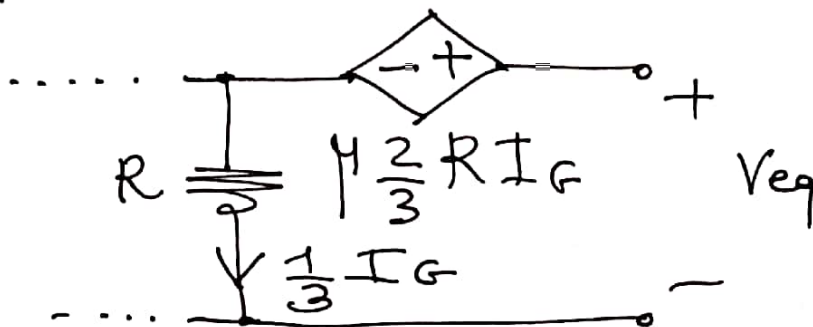
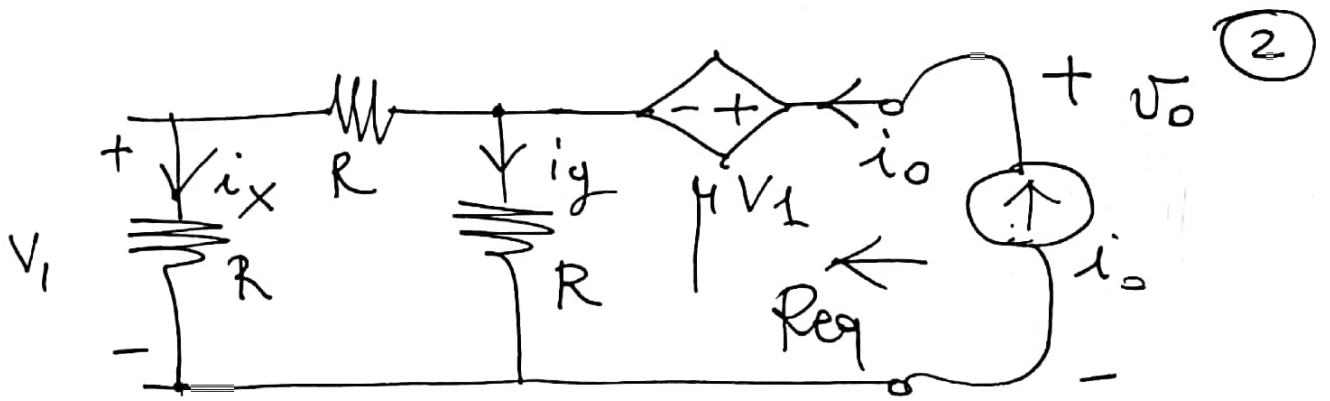
$$V_{eq} = \frac{2}{3} M R I_G + \frac{1}{3} R I_G$$



Partitore di corrente:

$$i_x = \frac{1}{3} i_o \Rightarrow V_1 = \frac{1}{3} R i_o$$

$$i_y = \frac{2}{3} i_o \Rightarrow$$


$$V_o = \mu V_1 + R i_y = \frac{1}{3} \mu R i_o + \frac{2}{3} R i_o$$

$$\Rightarrow R_{eq} = \frac{V_o}{i_o} = \frac{1}{3} \mu R + \frac{2}{3} R.$$


In fine:

$$i_{c.c.} = \frac{V_{eq}}{R_{eq}} = I_G \frac{1 + 2\mu}{2 + \mu}.$$

Esempio ? Thevenin, Norton rispetto AB ①

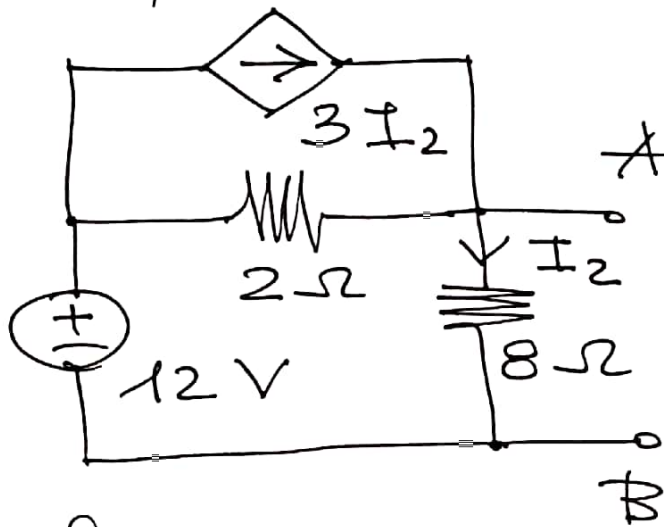

Soluzione

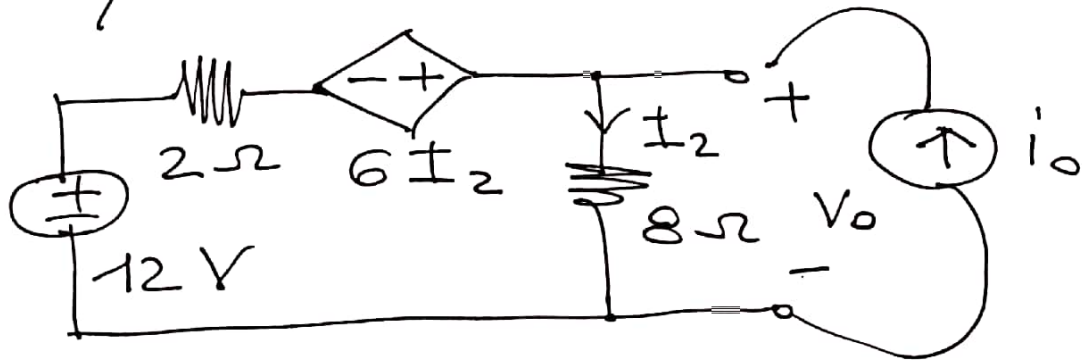

$$I_2 = \frac{V_0}{8}$$

$$\text{Millmann: } V_0 = \frac{\frac{12 + 6 \times \frac{V_0}{8}}{2} + i_0}{\frac{1}{2} + \frac{1}{8}} =$$


$$= \frac{6 + \frac{3}{8}V_0 + i_0}{\frac{5}{8}} =$$

$$= \frac{48 + 3V_0 + 8i_0}{5}$$

$$5V_0 = 48 + 3V_0 + 8i_0; \quad 2V_0 = 48 + 8i_0$$

$$V_0 = \underbrace{24}_{V_{eq}} + \underbrace{4i_0}_{R_{eq}}; \quad i_{c.c.} = \frac{V_{eq}}{R_{eq}} = 6A.$$

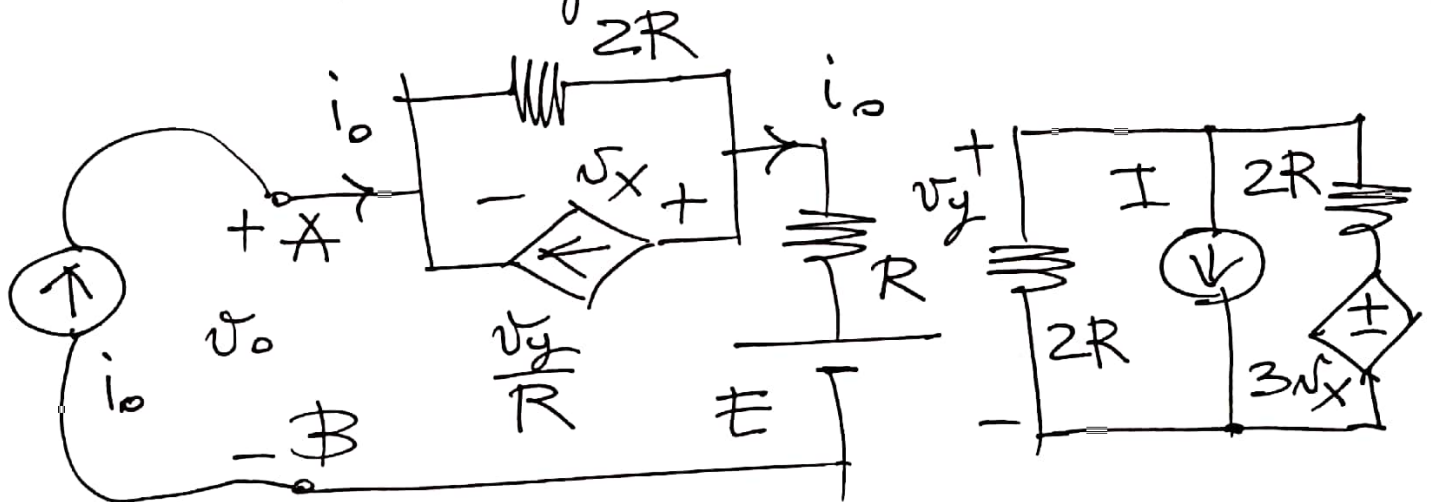Esercizio ? Thevenin di circuito AB con metodo rapido.




Potenzione

$$v_0 = -5x + Ri_0 + E \Rightarrow$$

$$5x = -v_0 + Ri_0 + E$$

$$\text{Millmann: } v_y = \frac{\frac{3v_x}{2R} - I}{\frac{1}{2R} + \frac{1}{2R}} = \frac{3}{2} v_x - RI$$
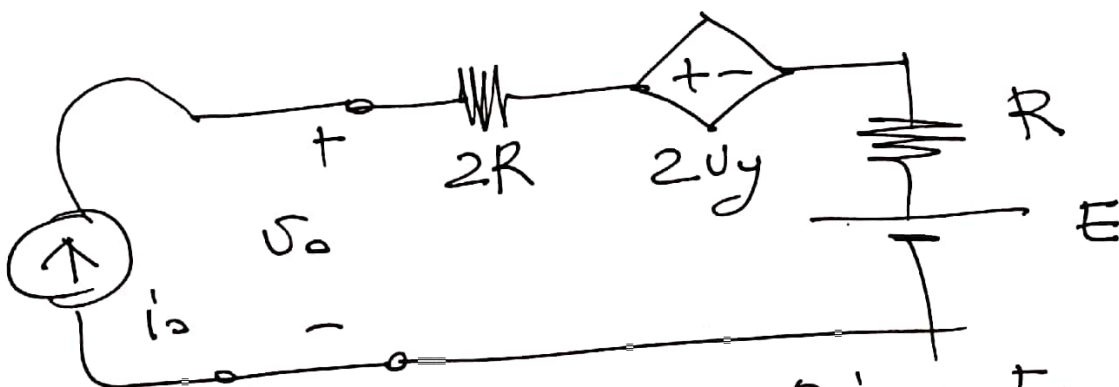
$$\Rightarrow v_y = -\frac{3}{2} v_0 + \frac{3}{2} Ri_0 + \frac{3}{2} E - RI$$



$$v_0 = 2Ri_0 + 2v_y + Ri_0 + E$$

Sostituendo v_y stesso

$$v_0 = \underbrace{\frac{3}{2} Ri_0}_{R_{eq}} + \underbrace{E - \frac{RI}{2}}_{V_{eq}}$$