
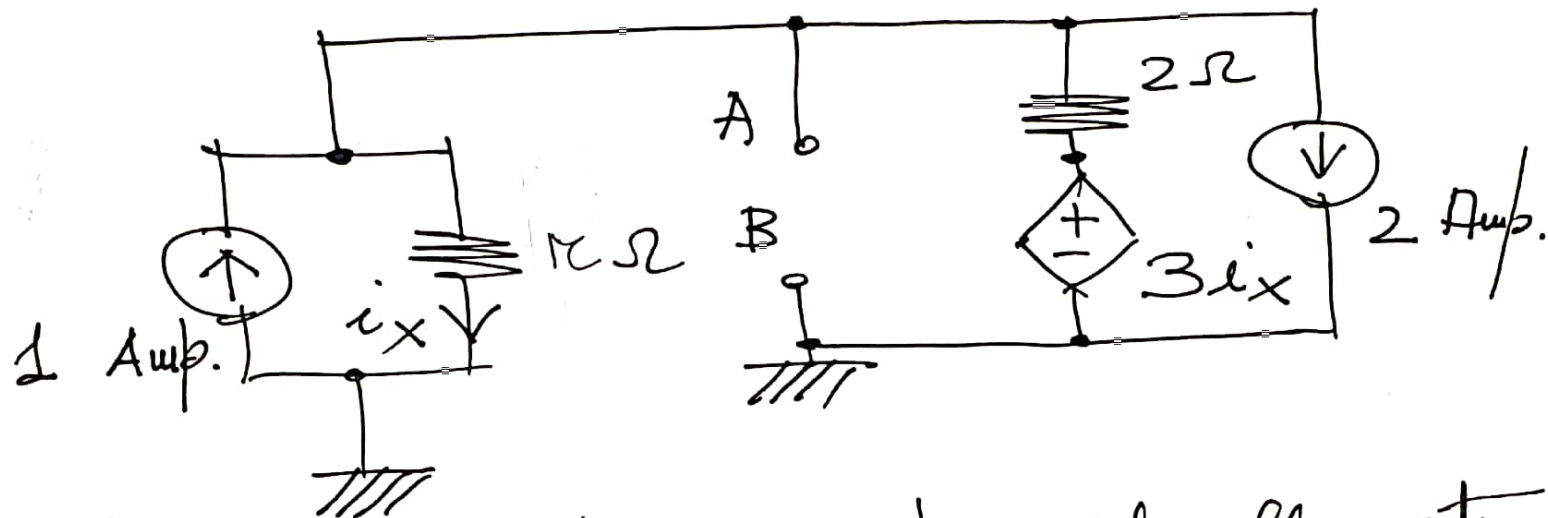


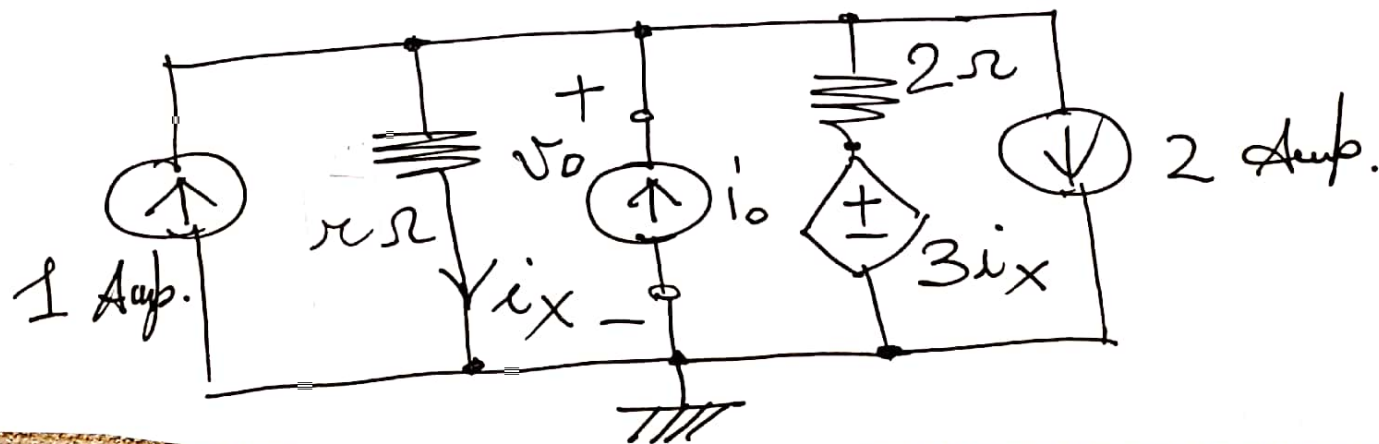Esempio Determinare l'equivalente di ①  
 Thevenin del bipolo A-B per  $\alpha \in \mathbb{R}$ .



Soluzione. Ridisegna usando un solo collegamento  
 di terra.



$$g = \frac{1}{\pi} \quad \text{Per Millmann}$$

(2)

$$v_o = \frac{1 - 2 + \frac{3}{2}ix + i_o}{g + \frac{1}{2}} = \frac{-1 + \frac{3}{2}ix + i_o}{g + \frac{1}{2}}$$

$$(g + \frac{1}{2})v_o = -1 + \frac{3}{2}ix + i_o$$

$$ix = gv_o$$

$$(g + \frac{1}{2})v_o = -1 + \frac{3}{2}gv_o + i_o$$

$$(\frac{1}{2} - \frac{1}{2}g)v_o = -1 + i_o$$

$$g \neq 1 \Rightarrow$$

$$v_o = \underbrace{-\frac{1}{\frac{1}{2} - \frac{1}{2}g}}_{v_{eq}} + \underbrace{\frac{1}{\frac{1}{2} - \frac{1}{2}g} i_o}_{R_{eq}}$$

$$g = 1$$


$$0 = -1 + i_o \Rightarrow$$

$$i_o = 1 \Rightarrow$$

il bipolo non è controllabile in corrente.

# Esercizio ? Thevenin bipolo ab

(3)

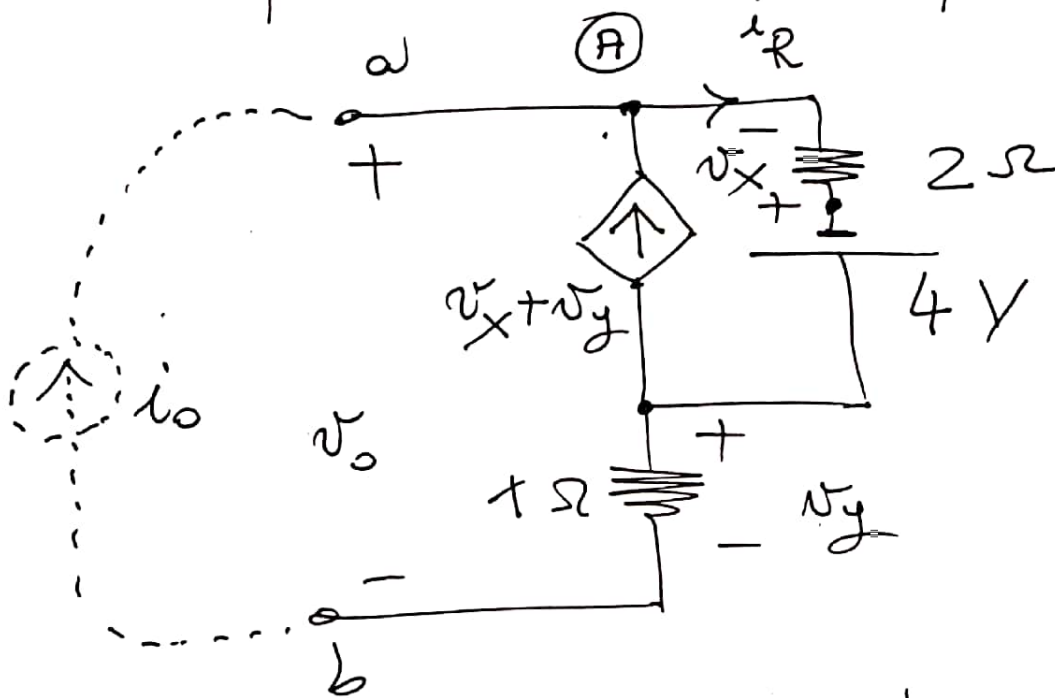

Soluzione: con metodo rapido...

$$v_y = 1 \cdot i_o$$

KI nodo  $(A)$ :

$$i_o + v_x + v_y = i_R = -\frac{v_x}{2}$$


$$i_o + \frac{3}{2}v_x = -v_y = -i_o$$

$$\frac{3}{2}v_x = -2i_o \Rightarrow v_x = -\frac{4}{3}i_o$$


$$v_o = -v_x - 4 + v_y = \frac{4}{3}i_o - 4 + i_o$$

$$v_o = \underbrace{\frac{7}{3}i_o}_{R_{eq}} - \underbrace{4}_{v_{eq}}$$

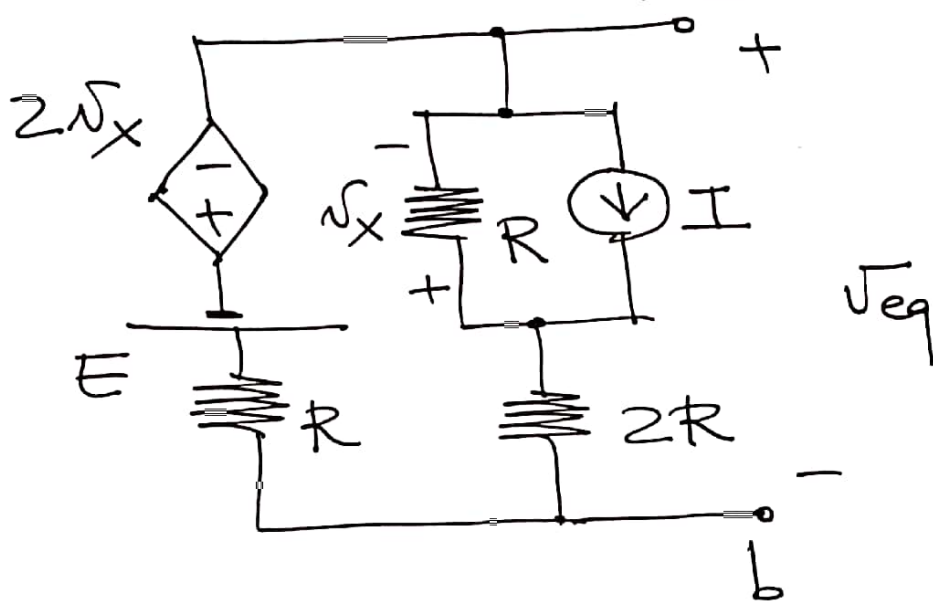Esempio ? Thevenin bipolo ab usando ④  
definizione di  $V_{eq}$  e  $R_{eq}$



Soluzione: Determiniamo  $V_x$

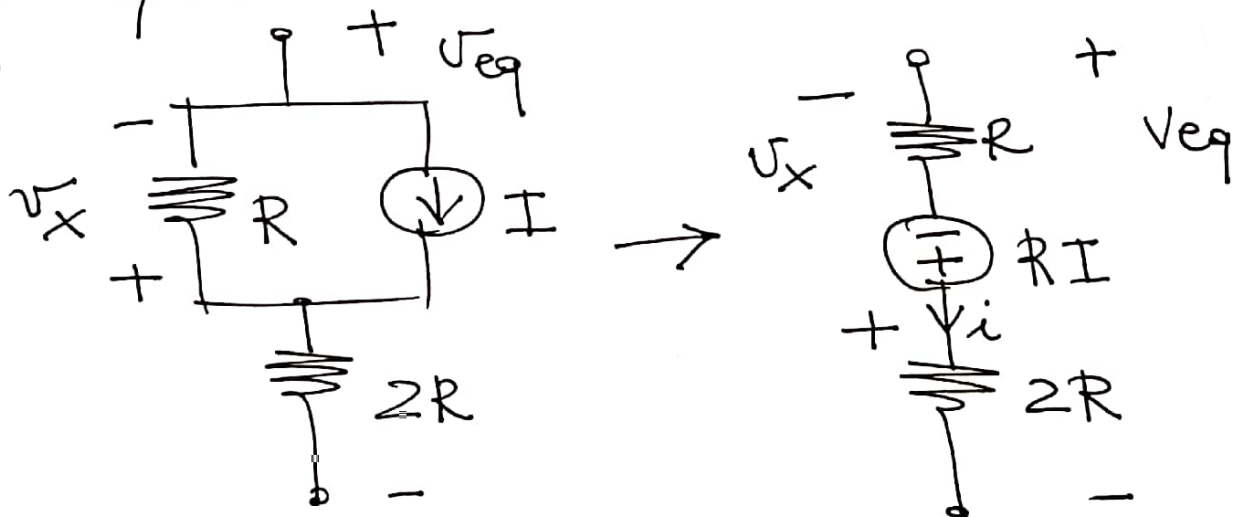


$$V_{eq} = R i - R I + 2 R i = 3 R i - R I \Rightarrow$$

$$i = \frac{V_{eq} + R I}{3 R}$$

$$V_x = -R i + R I = -\frac{1}{3} V_{eq} - \frac{R I}{3} + R I$$
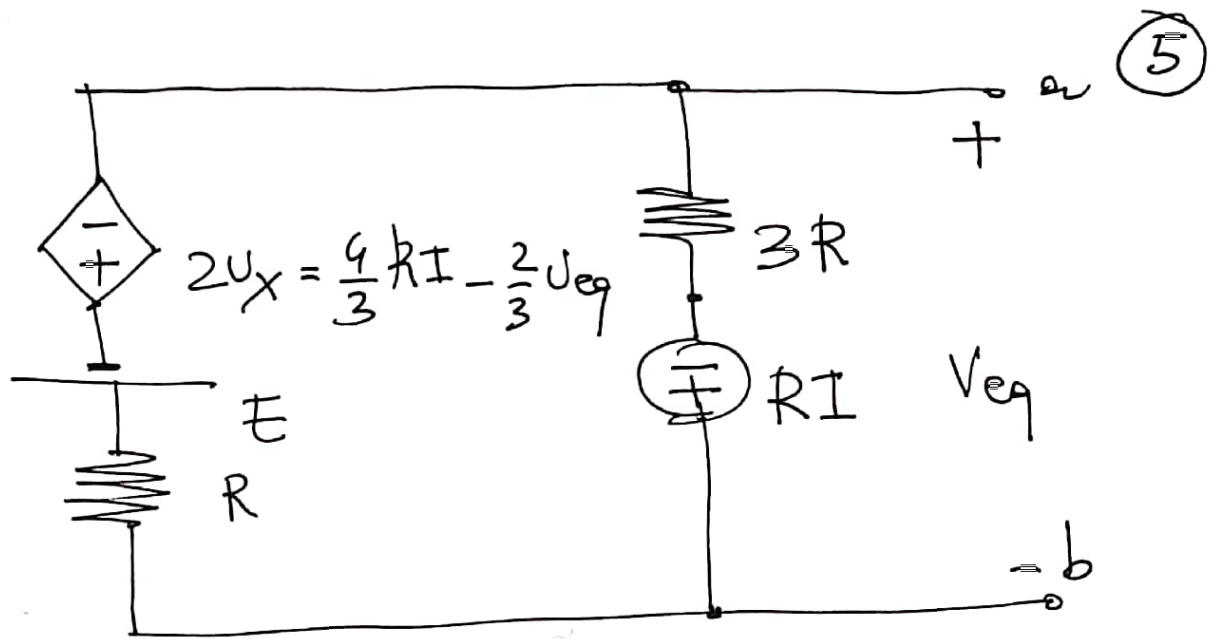
$$\boxed{V_x = \frac{2}{3} R I - \frac{1}{3} V_{eq}}$$




Millmann :

$$V_{eq} = \frac{E + \frac{4}{3}RI - \frac{2}{3}V_{eq}}{\frac{1}{R} + \frac{1}{3R}}$$

..... risolvendo

$$V_{eq} = -\frac{3}{2}E - \frac{5}{2}RI.$$

Resistenza equivalente :

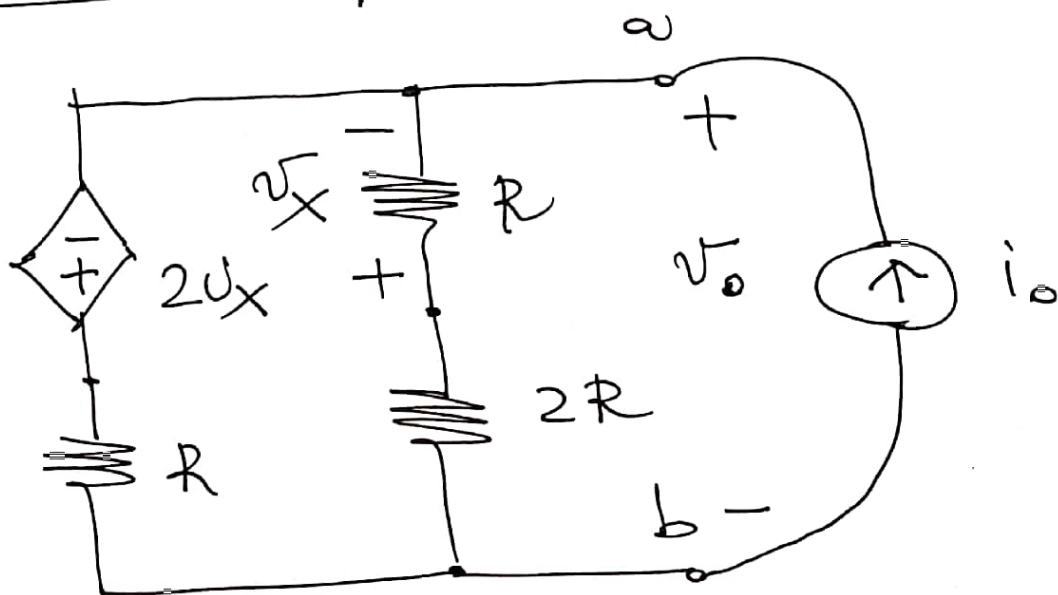

Hillmann:

6

$$v_o = \frac{-\frac{2v_x}{R} + i_o}{\frac{1}{R} + \frac{1}{3R}} = -\frac{3}{2}v_x + \frac{3}{4}Ri_o$$


$$v_x = -v_o \frac{R}{3R} = -\frac{v_o}{3}$$

Sostituendo:

$$v_o = -\frac{3}{2}\left(-\frac{v_o}{3}\right) + \frac{3}{4}Ri_o = \frac{v_o}{2} + \frac{3}{4}Ri_o$$


$$v_o = \frac{3}{2}Ri_o \Rightarrow$$

$$R_{eq} = \frac{3}{2}R$$

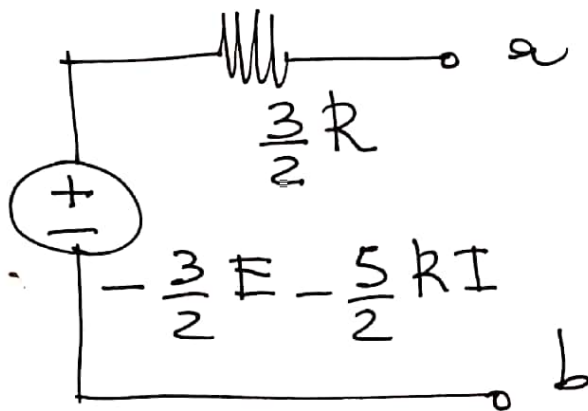

Esempio ? Thevenin bipolo ab

⑦

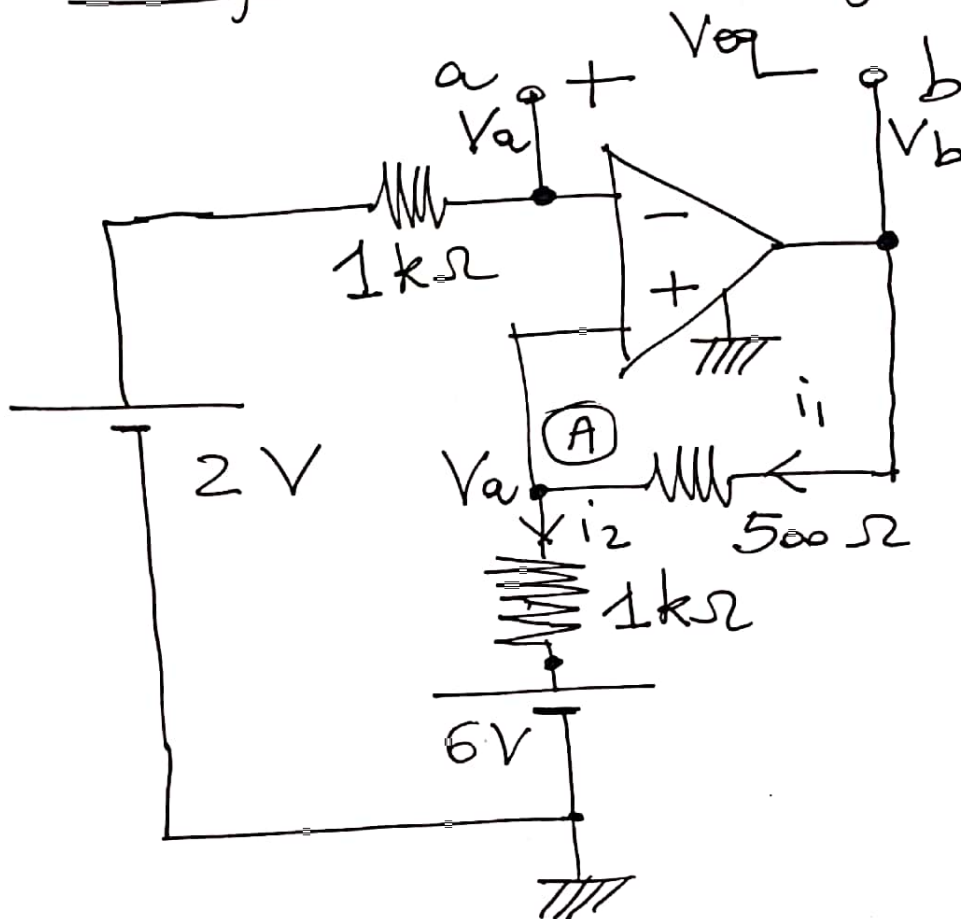

Soluzione

$$V_{eq} = V_a - V_b ; V_a = 2V$$


$$\text{KCL nodo (A)} : i_1 = i_2$$

$$\frac{V_b - 2}{500} = \frac{2 - 6}{1000}$$

$$2V_b - 4 = -4 \Rightarrow V_b = 0 \Rightarrow$$

$$\boxed{V_{eq} = V_a - V_b = 2V}$$

8

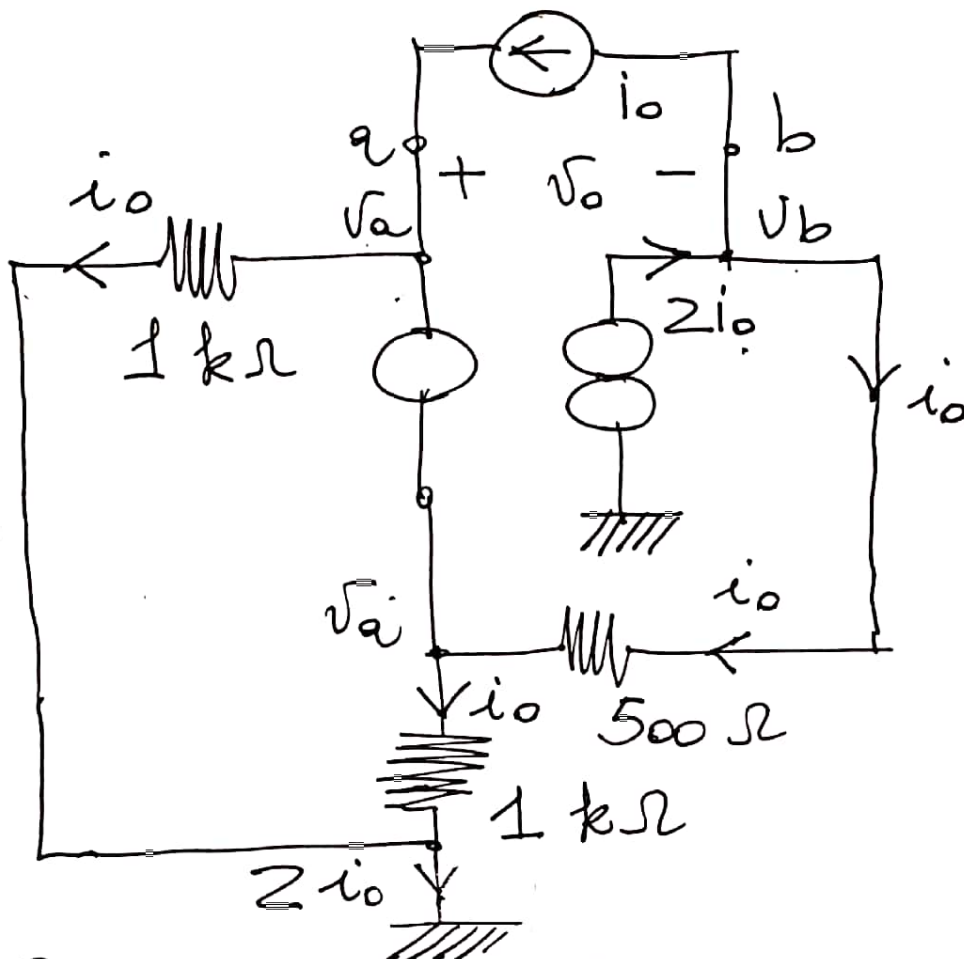

$$R_{eq} = \frac{V_0}{i_0} = \frac{V_a - V_b}{i_0}$$

$$V_a = 1000 i_0 ; \quad V_b = 1000 i_0 + 500 i_0 = 1500 i_0$$

$$V_a - V_b = -500 i_0 \Rightarrow$$

$$R_{eq} = \frac{V_0}{i_0} = -500 \Omega.$$