


ES1) $\frac{1}{2} \mu_n C_{ox} = 100 \frac{\mu A}{V^2}$, $L_n = 0.8 \mu m$, $V_{TH} = 0.8 V$, $W_n = 8 \mu m$

$\frac{1}{2} \mu_p C_{ox} = 30 \frac{\mu A}{V^2}$, $L_p = 0.8 \mu m$, $V_{TH} = 0.8 V$

$V_I = 1.5 V$

? W P

$V_{GS1} = 1.5 V > 0.8 V$ conduco

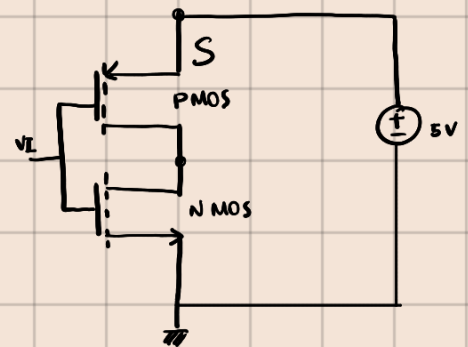

SUPPONGO SATURI ENTRAMBI

$$\frac{K_n}{2} (V_I - V_{TH})^2 = \frac{K_p}{2} (V_{DD} - V_I - V_{TP})^2$$

$$\frac{1}{2} \mu_n C_{ox} W_n \cdot 0.7^2 = \frac{1}{2} \mu_p C_{ox} W_p \cdot (2.7)^2$$

$$W_p = \frac{\frac{1}{2} \mu_n C_{ox} W_n}{\frac{1}{2} \mu_p C_{ox}} \left(\frac{0.7}{2.7} \right)^2 [\mu m] \approx 1.8 \mu m$$

ES2) Si calcoli il guadagno di amplificazione

$R_1 = 1 M\Omega$

$R_I = 10 K\Omega$

$K_n = \frac{1 mA}{V^2}$


$R_2 = 200 K\Omega$

$V_{TH} = 1 V$


$C_1 = 1 \mu F$

$R_d = 4 K\Omega$

$V_{DD} = 12 V$

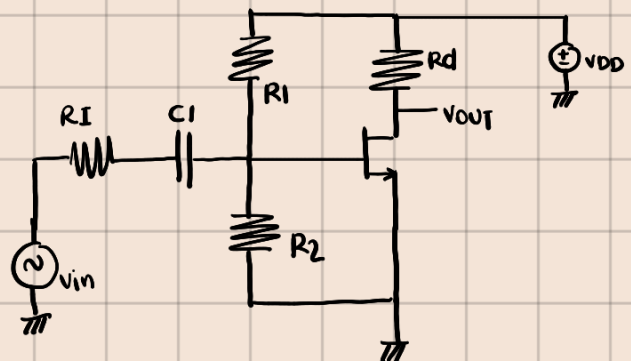

IN CONTINUA

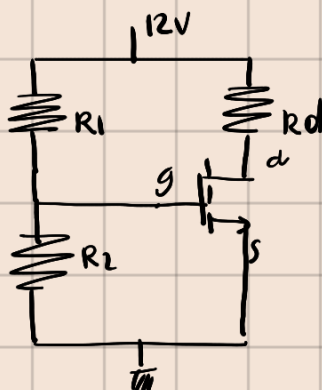


$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{200}{1200} \cdot 12 = 2 V > 1 V$$

$$I_{DS} = \frac{K_n}{2} (2 - 1)^2 = 0.5 mA$$

$$V_{DS} = 12 - R_d I_{DS} = 12 - 2 = 10 V > 1 V \text{ SAT}$$

$$Q^* = (0.5 mA, 10 V)$$


IN ALTERNATA (analisi a centro banda)

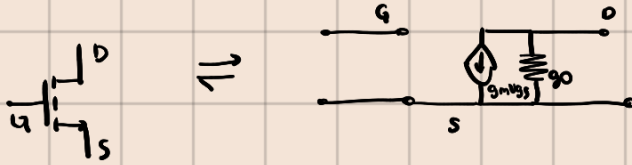

$$g_m = \left. \frac{\partial i_{DS}}{\partial v_{GS}} \right|_{Q^P} = \left. \frac{\partial}{\partial v_{GS}} \left(\frac{k_n}{2} (v_{GS} - v_{TH})^2 (1 + \lambda v_{DS}) \right) \right|_{Q^P}$$

$$= \frac{2 I_{DS^P}}{(V_{GS} - V_{TH})} = \frac{1 \text{ mA}}{1 \text{ V}} = 1 \text{ mS}$$
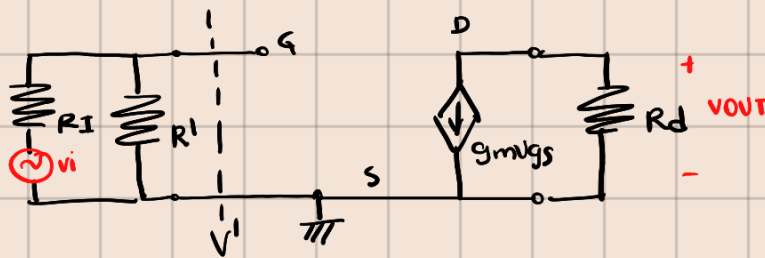
$$g_o \approx \lambda I_{DS^P} \rightarrow 0$$



$$R' = \frac{R_I R_L}{R_I + R_L} = \frac{1000 \cdot 100}{6100} \cdot 10^3 \approx 167 \text{ k}\Omega$$

$$v_{GS} = \frac{R'_1}{R_I + R'_1} v_i \quad v_{OUT} = -g_m v_{GS} R_D$$

$$v_{OUT} = -g_m \frac{R'_1 R_D}{R_I + R'_1} v_i$$

$$\frac{v_O}{v_i} = - \cancel{10^3} [\text{S}] \cdot \frac{167 \cdot 10^3 \cdot 4 \cdot 10^3}{177 \cdot 10^3}$$

$$= - \frac{167 \cdot 4}{177} \approx -3.77$$

COMPITO 05.02.2019


1) BJT identici

$$R_1 = 10 \text{ k}\Omega$$

$$R_L = 5 \text{ k}\Omega$$

$$\beta_F = 100$$

$$V_{CC} = 12 \text{ V}$$

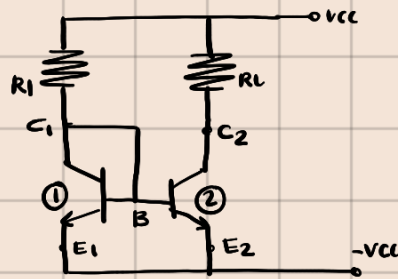

SONO IDENTICI ED HANNO STESSA $V_{BE} \rightarrow I_1 = I_2$
IN SAT

PER IL PUNTO DI LAVORO LI SUPPONGO IN RAD $V_{BE} \approx 0.6 \text{ V}$

$$V_B - V_E = 0.6 \rightarrow V_B = 0.6 + V_E = 0.6 - 12 = -11.4 \text{ V}$$

$$\rightarrow V_{C1} = V_B = -11.4 \text{ V} \rightarrow I_1 = \frac{V_{CC} - V_{C1}}{R_1} = \frac{12 + 11.4}{10} \text{ mA} = 2.34 \text{ mA}$$


$$V_{CE1} = -11.4 + 12 = 0.6 \text{ V} > 0.2 \text{ V} \\ \text{RAD}$$

$$I_2 = I_1 \rightarrow V_{C2} = 12 - R_L I_2 = 12 - 5 \cdot 2.34 = 0.3 \text{ V}$$

$$V_{CE2} = 0.3 + 12 = 12.3 \text{ V} \rightarrow \text{RAD}$$

$$Q_1 = (2.34 \text{ mA}, 0.6 \text{ V}) \quad Q_2 = (2.34 \text{ mA}, 12.3 \text{ V})$$

ES2)


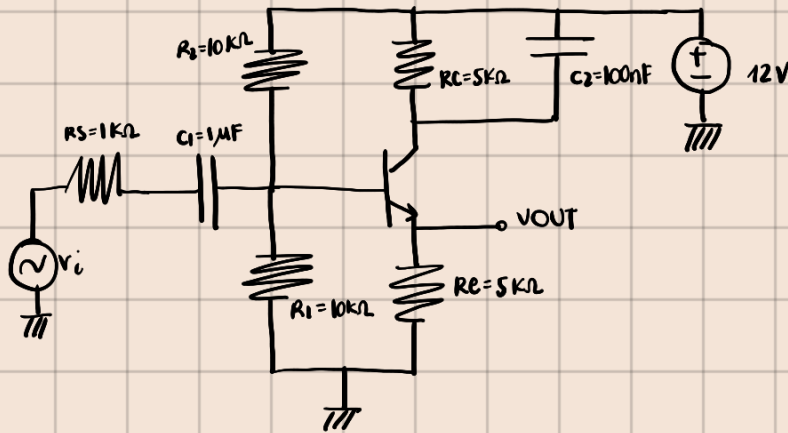


$$f \rightarrow 0$$

$$h_{ie} = 5 \text{ k}\Omega$$

$$h_{fe} = 300$$

IN CONTINUA

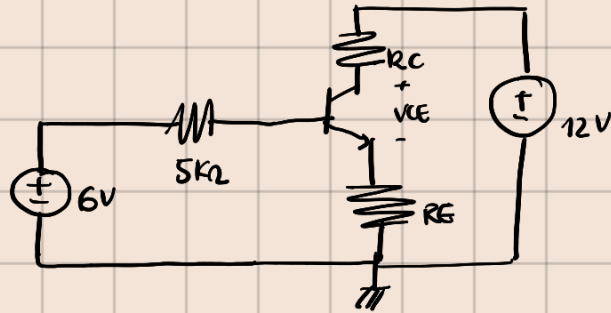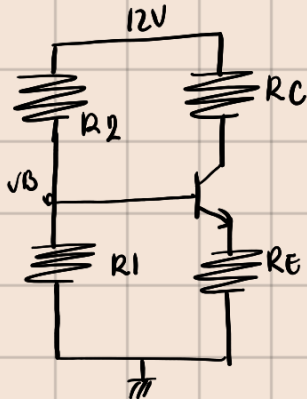

$$12 = R_C \cdot I_C + V_{CE} + R_E \cdot I_E$$

$$6 - 5 \cdot 10^3 \cdot I_B = 0.6 + R_E \cdot I_E$$

$$(R_E (pF11) + 5 \cdot 10^3) I_B = 5.4$$



$$V_E = 5 \cdot 301 \cdot \frac{1.08}{302} \approx 5.38 \text{ V}$$

$$I_B = \frac{108 \cdot 10^{-3}}{(pF12)}$$

$$V_{CE} = 12 - \frac{5.4}{pF12} \approx 12 - \frac{5.4}{302} \approx 11.9 \text{ V} > 0.2 \text{ V}$$

$$V_{BC} = V_{BE} - V_{CE} = 0.6 - 11.9 < 0.6 \text{ OK}$$

IN ALTERNATA

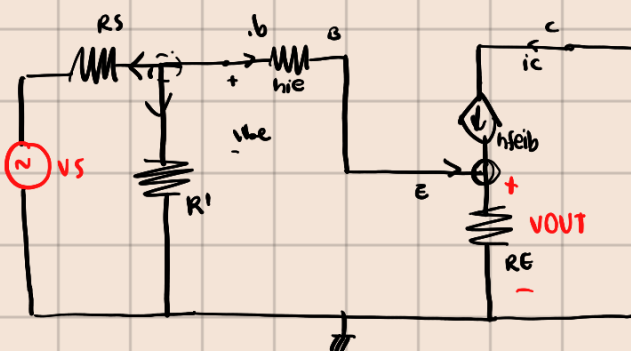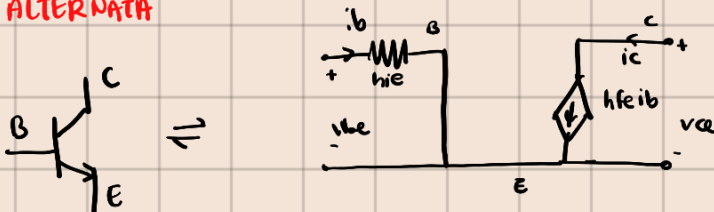

$$V_O = R_i I_b$$

$$R_S I_1 + V_i = R_1 I_2 + I_2 = \frac{R_S I_1 + V_i}{R_1}$$

$$h_{ie} I_b + V_O = R_1 I_2$$

$$I_1 + I_2 = -I_b$$

$$R_s i_1 + v_i = R' i_2 \rightarrow -R_s (i_2 + i_b) + v_i = R' i_2 \rightarrow (R' + R_s) i_2 = v_i - R_s i_b \rightarrow i_2 = \frac{v_i - R_s i_b}{R' + R_s}$$

$$h_{ie} i_b + v_o = R' i_2 \rightarrow h_{ie} i_b + v_o = \frac{R'}{R' + R_s} v_i - \frac{R' R_s}{R' + R_s} i_b \rightarrow (h_{ie} + \frac{R' R_s}{R' + R_s}) i_b = \frac{R'}{R' + R_s} v_i - v_o$$

$$i_1 + i_2 = -i_b \rightarrow i_1 = -i_2 - i_b$$

$$(h_{ie} (R' + R_s) + R' R_s) i_b = R' v_i - (R' + R_s) v_o$$

$$i_b = \frac{10^{-3} v_i - \frac{6}{35} 10^{-3} v_o}{\frac{7}{7} + \frac{6}{35}} = \frac{1}{7} 10^{-3} v_i - \frac{6}{35} 10^{-3} v_o$$

$$v_o = R i_b = \frac{R}{7} 10^{-3} v_i - \frac{6 R}{35} 10^{-3} v_o$$

$$R = 5 \cdot 301 \cdot 10^3$$

$$v_o = \frac{5 \cdot 301}{7} v_i - \frac{301 \cdot 6}{7} v_o$$

$$\rightarrow 7 + 301 \cdot 6 v_o = 5 \cdot 301 v_i \rightarrow \frac{v_o}{v_i} = \frac{5 \cdot 301}{7 + 301 \cdot 6} = 0.83$$

ES 3

$$V_{TH} = 1V$$

calcolare punto di lavoro

$$k_n = 2 \frac{mA}{V^2}$$

$$V_{CC} = 13V$$


$$R_1 = 1K\Omega$$

$$C_1 = C_2 = 100nF$$


$$R_C = 1K\Omega$$

$$R_2 = R_3 = 10M\Omega$$
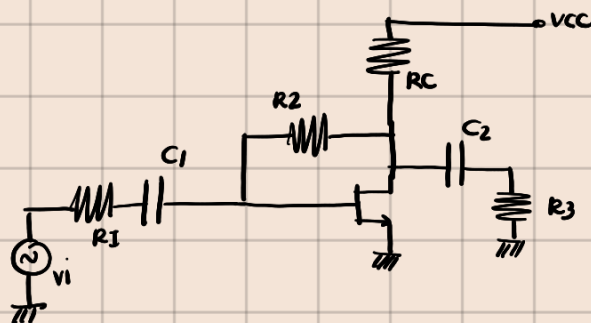
$$v_i = 10V + \sin(2\pi f t) \quad f = 1kHz$$



PER IL PUNTO DI LAVORO SIAMO IN CONTINUA

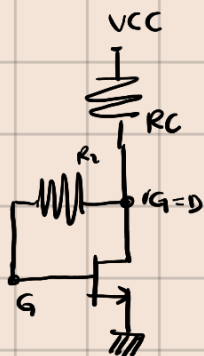

se $V_G > V_{TH}$ SONO SEMPRE IN SATURAZIONE

$$I_{DS} = \frac{k_n}{2} (V_{GS} - V_{TH})^2 \rightarrow V_{GS}^2 - 2V_{TH}V_{GS} + V_{TH}^2 = \frac{2}{k_n R_C} V_{CC} - \frac{2}{k_n R_C} V_{GS}$$

$$I_{DS} = \frac{V_{CC} - V_{GS}}{R_C}$$

$$V_{GS}^2 - 2V_{GS} + 1 - 13 + V_{GS} = 0$$

$$V_{GS}^2 - V_{GS} - 12 = 0$$

$$V_{GS} = \frac{1 \pm \sqrt{1+48}}{2} = \frac{1 \pm 7}{2} \rightarrow \begin{cases} 4V \\ 3V \end{cases}$$

$$I_{DS} = \left(\frac{mA}{V^2} \right) \cdot 9V^2 = 9mA$$

$$V_{DS} = V_{GS} = 4V$$

$$Q^P = (9mA, 4V)$$

COMPITO 14.11.2018

ES1


$$I_S = 10^{-16} \text{ A}$$

$$\alpha_F = 0.95$$

$$V_C = 5 \text{ V}$$

$$I_B = 100 \mu\text{A}$$

? I_C, I_E, V_{BE}

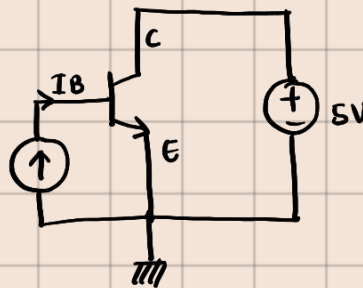

$$I_C = \beta_F I_B \rightarrow I_C = 1.9 \text{ mA}$$

$$I_E = (\beta_F + 1) I_B \rightarrow I_E = 2 \text{ mA}$$

$$\alpha_F = \frac{I_C}{I_E} = \frac{\beta_F}{\beta_F + 1}$$

$$I_B = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right)$$

$$\frac{I_B}{I_S} + 1 = e^{\frac{V_{BE}}{V_T}} \rightarrow V_{BE} = V_T \ln \left(\frac{I_B + I_S}{I_S} \right)$$

$$= 25 \cdot 10^{-3} [\text{V}] \cdot \ln \left(\frac{0.1 + 10^{-13}}{10^{-11}} \right)$$

$$\approx 0.69 \text{ V}$$


se $V_{BC} < 0.6$ allora sono in RAO

$$V_C = 5 \text{ V}$$

$$V_B = 0.69 \text{ V} \rightarrow V_{BC} = 0.69 - 5 = -4.31 < 0.6$$

ES2

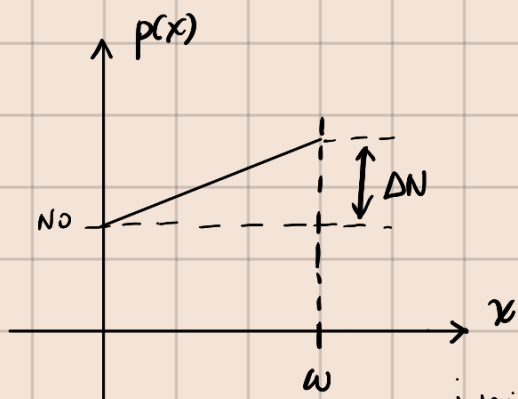calcolare la distribuzione di carica non compensata e di campo elettrico.



$$p(x) = mx + c$$

$$p(0) = c = N_0$$

$$p(w) = mw + N_0 = N_0 + \Delta N$$

$$m = \frac{\Delta N}{w}$$

$$\rightarrow p(x) = \frac{\Delta N}{w} x + N_0$$

$$= \frac{\Delta N}{w} \left(x + \frac{w}{\Delta N} N_0 \right)$$

j deriva = j diff

$$\frac{q}{\mu_p E} = \frac{q}{p} \frac{\partial p(x)}{\partial x} \rightarrow E(x) = V_T \frac{1}{x + \frac{w}{\Delta N} N_0}$$

$$\nabla \cdot E(x) = \frac{\rho(x)}{\epsilon}$$



$$\rho(x) = \epsilon \frac{\partial E(x)}{\partial x} = -\epsilon \frac{V_T}{\left(x + \frac{w}{\Delta N} N_0 \right)^2}$$

$$E \cdot S = \frac{Q}{\epsilon} \rightarrow E(x) = \frac{\sigma(x)}{\epsilon} \rightarrow \sigma(0) = \epsilon V_T \frac{1}{\frac{w}{\Delta N} N_0}$$

$$\sigma(w) = -\epsilon \frac{V_T}{\frac{w}{\Delta N} N_0 + \frac{w}{\Delta N} N_0}$$

COMPITO 11.09.2018

ES1

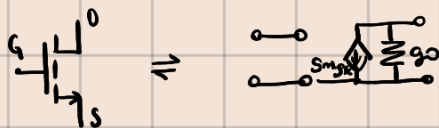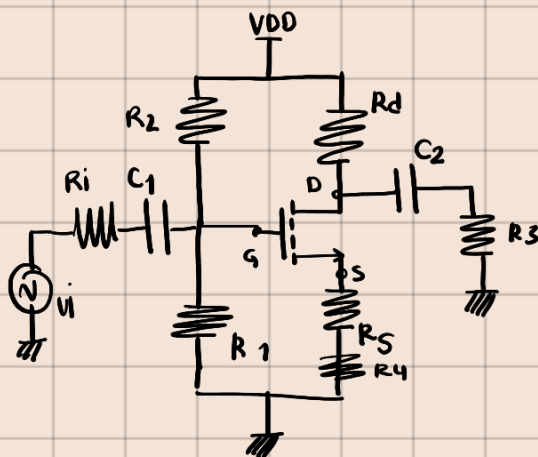

$$g_m = \frac{2 I_{DQ}}{V_{GS} - V_{TH}} \approx 0.5 \text{ mS}$$

$$g_o \approx 3.2 \mu\text{S}$$

$$k_n = 0.5 \frac{\text{mA}}{\text{V}^2}$$

$$V_{TH} = 1\text{V}$$

$$\lambda = 0.0133 \frac{1}{\text{V}}$$

$$Q = (0.241 \text{ mA}, 3.81\text{V})$$

$$R_1 = 1\text{ k}\Omega$$

$$R_D = 22\text{ k}\Omega$$

$$R_2 = 1.5\text{ M}\Omega$$

$$R_4 = 10\text{ k}\Omega$$

$$R_3 = 2.2\text{ M}\Omega$$

$$R_5 = 100\text{ k}\Omega$$

$$R_S = 2\text{ k}\Omega$$


$$V_{DD} = 12\text{V}$$

$$C_1, C_2: Z_{C1}, Z_{C2} \rightarrow 0 \text{ per } \omega \rightarrow 0$$

$$\frac{k_n}{2} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) = I_{DQ}$$

$$V_{GS} - V_{TH} = \sqrt{\frac{2 I_{DQ}}{k_n (1 + \lambda V_{DS})}}$$
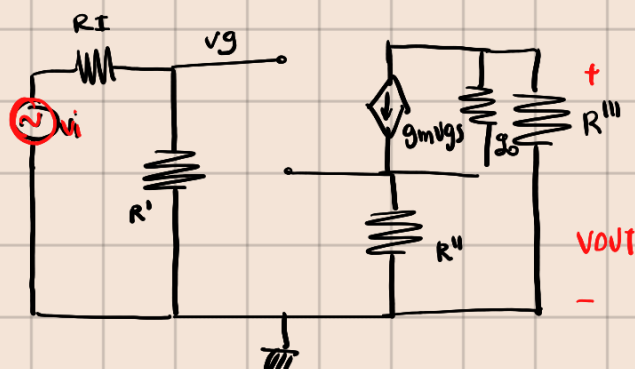
$$V_{GS} = V_{TH} + \sqrt{\frac{2 I_{DQ}}{k_n (1 + \lambda V_{DS})}} = 1 + \sqrt{\frac{4 \cdot 0.241 \cdot 10^{-3}}{10^{-3} (1 + 0.0133 \cdot 3.81)}} \approx 1.96\text{V}$$



$$R^I = \frac{R_1 R_2}{R_1 + R_2} = 892\Omega$$

$$R'' = R_4 + R_5 = 12\text{ k}\Omega$$

$$R''' = \frac{R_3 R_D}{R_3 + R_D} = 18\text{ k}\Omega$$

$$v_g = \frac{R^I}{R^I + R_I} v_i = \frac{0.89}{1.89} v_i \approx 0.47 v_i$$

$$v_s = R'' (g_m (v_g - v_s) + g_o (v_o - v_s))$$

$$(1 + R'' (g_m + g_o)) v_s = R'' g_m v_g + R'' g_o v_o$$

$$(1 + 12 \cdot 10^3 (0.5 \cdot 10^{-3} + 3.2 \cdot 10^{-6})) v_s = 6 v_g + 12 \cdot 3.2 \cdot 10^{-3} v_o$$

$$v_s = \frac{6}{7.04} v_g + \frac{12 \cdot 3.2}{7.04} \cdot 10^{-3} v_o = 0.85 v_g + 0.005 v_o$$

$$v_o = -R''' (g_m (v_g - v_s) + g_o (v_o - v_s))$$

$$= -R''' (g_m (0.15 v_g - 0.005 v_o) + g_o \cdot 0.995 v_o - g_o (0.85) v_g)$$

$$v_o = -R''' (g_m \cdot 0.15 v_g - g_o (0.85) v_g) - R''' (-g_m 0.005 v_o + g_o \cdot 0.995 v_o)$$

$$(1 + R''' (g_o \cdot 0.995 - g_m 0.005)) v_o = -R''' (g_m \cdot 0.15 - g_o (0.85)) v_g$$

$$[1 + 18 \cdot 10^3 (3.2 \cdot 10^{-6} \cdot 0.995 - 0.5 \cdot 10^{-3} \cdot 0.005)] v_o = -18 \cdot 10^3 (0.5 \cdot 10^{-3} \cdot 0.15 - 3.2 \cdot 10^{-6} \cdot 0.85) v_g$$

$$1.01 v_o = -1.30 v_g$$

$$v_o \approx -1.29 v_g = -1.29 \cdot 0.47 v_i \approx -0.6 v_i$$

$$v_{gs} < 2 (V_{GS} - V_{TH})$$

$$v_g - v_s = 0.47 v_i - 0.89 \cdot 0.47 v_i + 0.005 \cdot 0.6 v_i$$

$$\approx 0.078 v_i$$

$$0.078 v_i < 2 (0.96) \rightarrow v_i < 24.6 V$$

2) Si calcoli corrente DEL TRANSISTOR e k_n sapendo che:

$$V_{GS} = 1V$$

$$V_{DS} = 0.1V$$

$$V_{GS} < V_{TH} \text{ NON CONDUCE}$$

$$V_{TH} = 1.5V$$

$$W = 10 \mu m$$

$$L = 1 \mu m$$

$$d = 25 nm$$

$$\mu_n = 500 \frac{cm^2}{V \cdot s}$$

$$\epsilon_{OX} = 3.9$$

$$\epsilon_0 = 8.854 \cdot 10^{-14} \frac{F}{cm}$$

$$k_n = \frac{C_{OX} \mu_n W}{L}$$

$$-12+9 -6+4$$


$$= \frac{\epsilon}{d} \cdot \frac{W \mu_n}{L} = \frac{(3.9)(8.854 \cdot 10^{-12}) \left[\frac{F}{m} \right]}{25 \cdot 10^{-9} [m]} \cdot \frac{10 \cdot 10^{-6} [m] \cdot 500 \cdot 10^4 \left[\frac{m^2}{V \cdot s} \right]}{10^{-6} [m]}$$

$$F = \frac{C}{V}$$

$$\approx 6.9 \cdot 10^{-3} \left[\frac{C}{V^2 \cdot s} \right] = 6.9 \frac{mA}{V^2}$$

COMPITO 13.02.2018

ES1

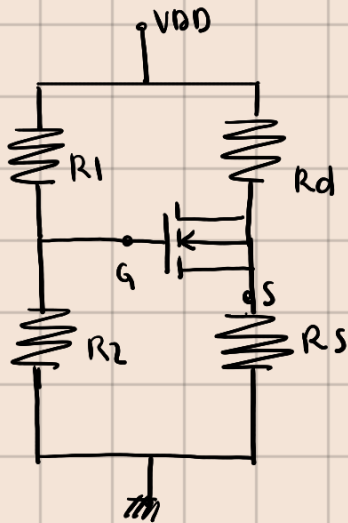

$$V_{DD} = 18V$$

$$R_1 = 5.6 \text{ k}\Omega$$

$$R_2 = 4.7 \text{ k}\Omega$$

$$R_S = 1.2 \text{ k}\Omega$$

$$R_D = 2.2 \text{ k}\Omega$$

$$k_n = 0.4 \frac{\text{mA}}{\text{V}^2}$$

$$V_{TH} = 3V$$

? Si calcoli il punto di lavoro

$$V_G = \frac{4.7}{10.1} 18 \approx 8.38V$$

Suppongo in SAT

$$V_S < 5.38$$

$$\frac{k_n}{2} (5.38 - V_S)^2 = \frac{V_S}{R_S}$$

$$(5.38)^2 - 2 \cdot 5.38 \cdot V_S + V_S^2 - \frac{2}{k_n R_S} V_S = 0$$

$$V_S^2 - 15 V_S + 29 = 0$$


$$\frac{15 \pm \sqrt{109}}{2} = \begin{cases} 12.7V \\ 2.28V \end{cases}$$

$$I_{DS} = 0.2 \left(\frac{\text{mA}}{\text{V}^2} \right) (3.1)^2 = 1.92 \text{ mA}$$

$$V_D = 18 - 2.2 \cdot 1.92 \approx 13.78V$$

$$\rightarrow V_{DS} \approx 11.5V > 3.1V \quad \checkmark$$

ES 2

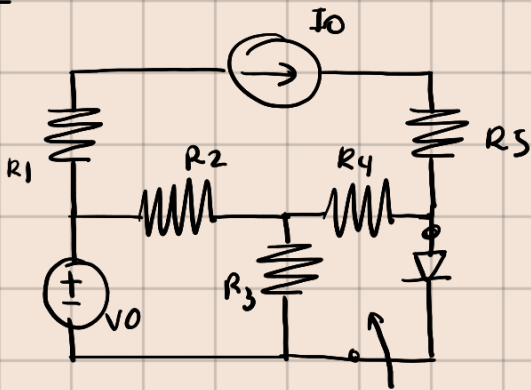

$$V_0 = 2.5V$$

? Si calcoli corrente diodo

$$I_0 = 65\mu A$$

$$R_1 = 10K\Omega$$


$$R_3 = 20K\Omega$$

$$R_5 = 15K\Omega$$




$$R_2 = 10K\Omega$$

$$R_4 = 15K\Omega$$

$$V_{TH} = 0.7V$$

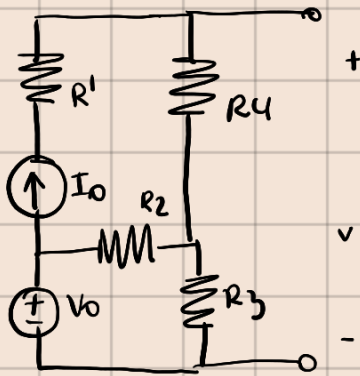

$$V = \theta_1 + \theta_2$$

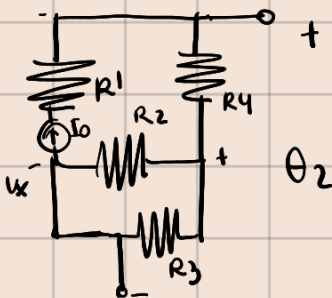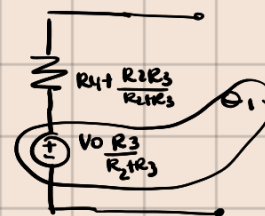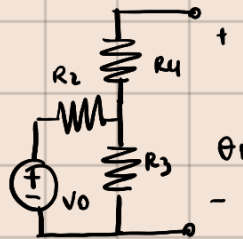

$$V_X = (R_1 + R_4)I_0$$


$$V = \frac{R_3}{R_2 + R_3} V_0 + (R_1 + 2R_4)I_0$$

$$\theta_2 = (R_1 + 2R_4)I_0$$

$$= 1.66V + 3.57V = 5.23V$$

$$R_{eq} = R_4 + \frac{R_2 R_3}{R_2 + R_3}$$

$$= 21.6K\Omega$$

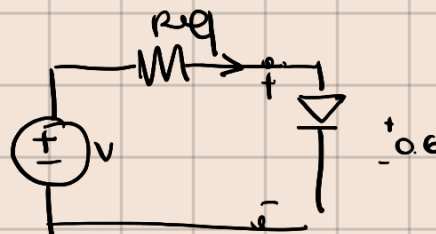

$$I_D = \frac{V - 0.6}{R_{eq}} = \frac{5.23 - 0.6}{21.67} \text{ mA} = 0.21 \text{ mA}$$

ES 3

DiODO PN a sezione circolare

$$r = 2 \text{ nm}$$

$$N_A = 10^{17} \frac{1}{\text{cm}^3}$$

$$N_D = 10^{18} \frac{1}{\text{cm}^3}$$

$$q = 1.6 \cdot 10^{-19} \text{ C}$$



$$\epsilon = 80 \cdot 10^{-14} \frac{\text{F}}{\text{cm}}$$

$$E_G = 1.12 \text{ V}$$

$$r = 5 \cdot 10^{-18} \frac{1}{\text{s} \cdot \text{cm}^3}$$

$$\mu_n = 1350 \frac{\text{cm}^2}{\text{V} \cdot \text{s}}$$

! corrente del diodo

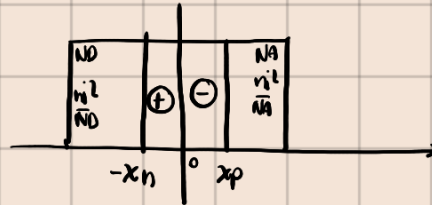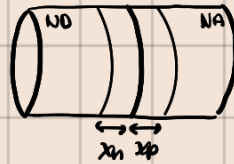

$$\phi = V_T \ln \left(\frac{N_D \cdot N_A}{n_i^2} \right) = 25 \cdot 10^{-3} [\text{V}] \cdot \ln \left(10^{25} \right) \approx 1.44 \text{ V}$$

$$n_i \approx e^{\frac{E_G}{2V_T}} \approx 0.5 \cdot 10^{10}, n_i^2 \approx 10^{20}$$

$$W = \sqrt{\frac{2\epsilon}{q} \phi \left(\frac{1}{N_A} + \frac{1}{N_D} \right)} = \sqrt{\frac{2 \cdot 80 \cdot 10^{-14} \left(\frac{\text{F}}{\text{cm}} \right) \cdot 1.44 [\text{V}] \cdot \left(10^{-17} + 10^{-18} \right) [\text{cm}^3]}{1.6 \cdot 10^{-19} [\text{C}]}}$$

$$= \sqrt{27.72 \cdot 10^{-12} [\text{cm}^2]} = 5.26 \cdot 10^{-6} [\text{cm}]$$

$$\approx 52.6 \text{ nm}$$

$$S = \pi r^2 \approx \pi \cdot 4 \cdot 10^{-18} [\text{m}^2]$$


$$q S \sqrt{\frac{\mu_n V_T r}{N_A}} n_i^2 = 1.6 \cdot 10^{-19} [\text{C}] \cdot 4\pi \cdot 10^{-18} [\text{cm}^2] \sqrt{\frac{1350 \left(\frac{\text{cm}^2}{\text{V} \cdot \text{s}} \right) \cdot 25 \cdot 10^{-3} [\text{V}] \cdot 5 \cdot 10^{-18} \left(\frac{1}{\text{cm}^3 \cdot \text{s}} \right)}{10^{17} \left(\frac{1}{\text{cm}^3} \right)}} \cdot 10^{20} \left(\frac{1}{\text{cm}^3} \right)$$

$$= 1.6 \cdot 4\pi \cdot 10^{-13} \left(\frac{\text{C}}{\text{cm}^2} \right) \sqrt{1687 \cdot 10^{-34} \left(\frac{\text{cm}^2}{\text{s}} \right)}$$

$$= 82.58 \cdot 10^{-13} \cdot 10^{-17} \text{ A}$$

$$\approx 0.82 \cdot 10^{-28} \text{ A}$$


ES1)

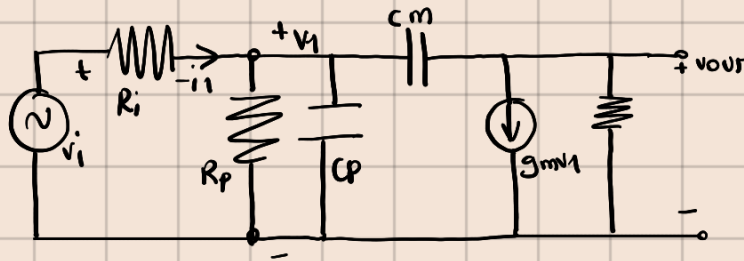

? Z_{in}, Z_{out} , guadagno

TEOREMA DI MILLNER O ABOWITZ

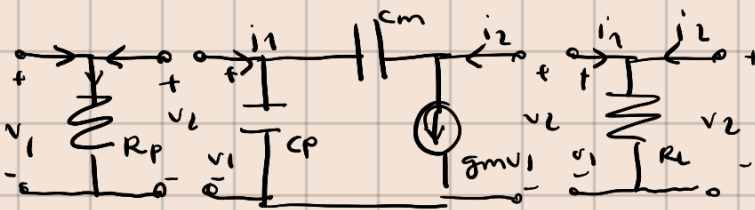Parametri di trasmissione in cascata si moltiplicano



$$T = \begin{bmatrix} 1 & 0 \\ \frac{1}{R_p} & 1 \end{bmatrix}$$

$$T = \begin{bmatrix} 1 & 0 \\ \frac{1}{R_L} & 1 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = T \begin{bmatrix} v_{out} \\ i_{out} \end{bmatrix}$$

$$v_1 = v_i - R_i i_1$$

$$t_{11} v_{out} = v_i - R_i t_{21} v_{out}$$

$$\rightarrow v_{out} = \frac{-v_i}{R_i t_{21} - t_{11}} \rightarrow A = \frac{1}{R_i t_{21} - t_{11}}$$

$$Z_{in} = \frac{t_{11}}{t_{21}} \rightarrow Y_{in} = \frac{t_{21}}{t_{11}}$$

$$Z_{out} = \frac{t_{21} R_L}{t_{21} R_L + t_{22}} \quad Y_{out} = \frac{t_{21}}{t_{22}} + \frac{1}{R_L}$$

$$\frac{1}{A} = R_i t_{21} - t_{11} = R_i \left(t_{21} - \frac{t_{11}}{R_i} \right)$$

$$v_1 = t_{11} v_2 - t_{12} i_2$$

$$i_1 = t_{21} v_2 - t_{22} i_2$$


$$v_2 = \frac{i_1 + t_{21} i_2}{t_{21}}$$

$$v_1 = \frac{t_{11} i_1}{t_{21}} + \frac{t_{11} t_{22}}{t_{21}} i_2 - t_{12} i_2$$

$$\frac{v_1}{i_1} = \frac{t_{11}}{t_{21}} \quad \frac{v_o}{i_o} = \frac{t_{22}}{t_{21}} \parallel \frac{1}{R_L}$$

$$V = \frac{1}{t_{21}} \begin{bmatrix} t_{11} & \det T \\ 1 & t_{22} \end{bmatrix}$$

ES2)

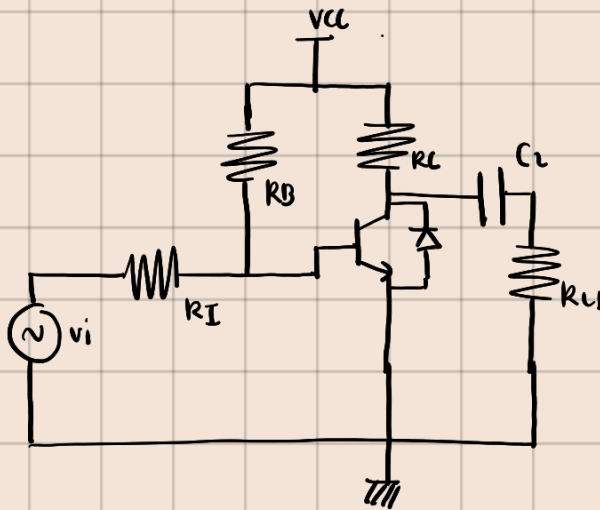

$$\beta_F = 30$$

$$V_{CC} = 12V$$

$$R_I = 2k\Omega$$

$$R_1 = 360k\Omega$$


$$R_2 = 750k\Omega$$

$$R_E = 8k\Omega$$

$$R_C = 4k\Omega$$

? Punto di lavoro,
Corrente I_B, I_E .

DC

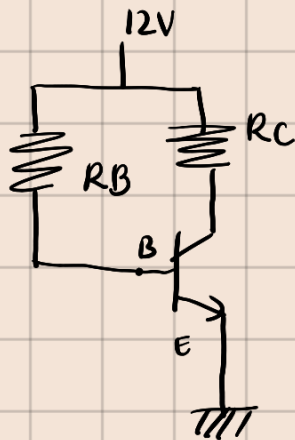

Tensione diodo 0.6V

Se conduce $V_{CE} = -0.6V$

→ NON SONO IN RAD

SUPPONGO $V_B = 0.6V$

$$\rightarrow I_B = \frac{12 - 0.6}{8} [mA] = 1.42 mA$$

$$\rightarrow I_C = \beta_F \cdot I_B = 128 mA$$

$$V_C = 12 - R_C I_C = 12 - 4 \cdot 128 \approx -500V$$

NO RAD

$$V_C > 0.2$$

$$I_C < \frac{12 - 0.2}{4} = 2.95 mA$$

$$\rightarrow I_B < 33 \mu A$$

$$I_B = \frac{12 - V_B}{R_B} < 33 \mu A$$

$$12 - V_B < 33 \cdot 10^{-6} \cdot R_B$$

$$\rightarrow V_B > 12 - 33 \cdot 10^{-6} R_B = 11.74 V, \text{ ma di solito}$$

$$V_{BE} \approx 0.6, 0.8$$

$$I_B < 33 \mu A$$

$$V_C > 0.2V$$

$$I_C < 2.95 mA$$

$$V_B > 11.74V$$

$$I_E < 3 mA$$

ES 3)

$$N_A = 10^{17} \frac{1}{\text{cm}^3}$$

$$N_D = 10^{10} \frac{1}{\text{cm}^3}$$

$$q = 1.6 \cdot 10^{-19} \text{ C}$$

$$\epsilon \approx 80 \cdot 10^{-14} \frac{\text{F}}{\text{cm}}$$

$$E_G = 1.12 \text{ V}$$

$$W = 100 \mu\text{m} \quad ? \text{ non so a che mi serve}$$

? ϕ, w

$$n_i \propto e^{-\frac{E_c - E_F}{kT}} \propto e^{+\frac{E_G}{2V_T q}} \propto 10^{10}$$

$$n_i^2 \propto 10^{20} \frac{1}{\text{cm}^3}$$

$$E_G = E_c - E_v$$

$$E_F = \frac{E_c + E_v}{2}$$

La parte svuotata sarà maggiore nella parte P

in quanto $N_d x_d = N_a x_p$

$$\Rightarrow x_p = \frac{N_d}{N_A} x_n = 10^3 x_n$$

$$\phi = V_T \ln \left(\frac{N_D \cdot n_A}{n_i^2} \right) = 25 \cdot 10^{-3} (\text{V}) \ln (10^{17})$$

$$\approx 0.98 \text{ V}$$


$$W = \sqrt{\frac{2\epsilon}{q} \phi \cdot \left(\frac{1}{N_A} + \frac{1}{N_D} \right)}$$

$$= \sqrt{\frac{160 \cdot 10^{-14} \frac{\text{F}}{\text{cm}}}{1.6 \cdot 10^{-19} \text{ C}} \cdot 0.98 [\text{V}] \cdot 10^{-17} (1 + 10^{-3}) [\text{cm}^3]}$$

$$= \sqrt{98 \cdot 10^{-12}} = 9.9 \cdot 10^{-6} \text{ (cm)}$$

$$\approx 100 \text{ nm} = 0.1 \mu\text{m}$$

20.06.2018

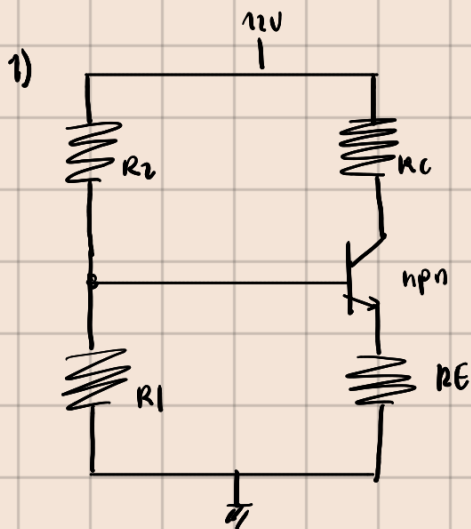


$$R_1 = 180 \text{ k}\Omega$$

$$R_2 = 360 \text{ k}\Omega$$

$$R_E = 16 \text{ k}\Omega$$

$$R_C = 22 \text{ k}\Omega$$

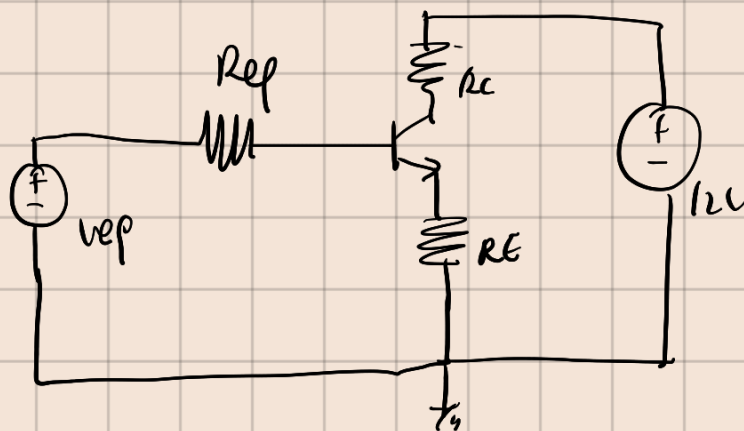Suppon go in RAD $V_{BE} = 0.7 \text{ V}$



$$R_{eq} = 120 \text{ k}\Omega$$

$$V_{eq} = 4 \text{ V}$$

$$\beta \in (10, 50) \\ \beta \in (50, 200)$$

$$V_{eq} = (R_{eq} + (\beta + 1)R_E)I_B + 0.7 \rightarrow I_B = \frac{V_{eq} - 0.7}{R_{eq} + (\beta + 1)R_E} = \frac{4 - 0.7}{120 + (\beta + 1)16} \cdot 10^{-3}$$

$$12 = R_C \beta I_B + V_{CE} + R_E (\beta + 1)I_B$$

$$V_{CE} = 12 - (R_C \beta + R_E (\beta + 1))I_B$$

$$\beta = 50 \\ V_{CE} = 12 - (50 \cdot 22 + 16 \cdot 51) \cdot 3.5 \cdot 10^{-3} \approx 5.3 \text{ V}$$

$$\beta = 200 \\ V_{CE} = 12 - (200 \cdot 22 + 16 \cdot 201) \cdot 0.58 \cdot 10^{-3} \approx 4.54 \text{ V}$$

$$I_B = \frac{3.3}{120 + 51 \cdot 16} \cdot 10^{-3} = 3.5 \mu\text{A} \rightarrow I_C = 0.17 \text{ mA}$$

$$I_B = \frac{3.3}{120 + 201 \cdot 16} = 0.58 \mu\text{A} \rightarrow I_C = 0.3 \text{ mA}$$

$$E_g = 1.12 \text{ eV} = 1.12 \cdot q \cdot J$$

$$k = 8.62 \cdot 10^{-5} \cdot q \cdot \frac{J}{K}$$

$$B = 10^{31} \frac{1}{K^3 \text{ cm}^6}$$

$$T = 35^\circ\text{C}$$

$$\mu_e = 1350 \frac{\text{cm}^2}{\text{Vs}}$$

$$\mu_p = 500 \frac{\text{cm}^2}{\text{Vs}}$$

$$V_a = -\mu E$$

$$j = \sigma E = NqV = -\mu NqE$$

$$T_K = 35 + 273.15 = 308.15$$

$$V_T = \frac{kT}{q} = 8.62 \cdot 10^{-5} \cdot 308.15 \text{ V} = 26.55 \text{ mV}$$



$$n_i \propto e^{-\frac{E_g}{2kT}} = e^{-\frac{1.12}{2 \cdot 26.55} \cdot 10^3} \approx 7 \cdot 10^{10}$$

$$\sigma = niq(\mu_n + \mu_p) = 7 \cdot 10^{10} \cdot 1.6 \cdot 10^{-19} \cdot 1850 \approx 20.7 \left(\frac{\text{A}}{\text{cm}} \right)$$

$$\rho = 48262 \Omega \text{ cm}$$

06.01.2024

ES 2)

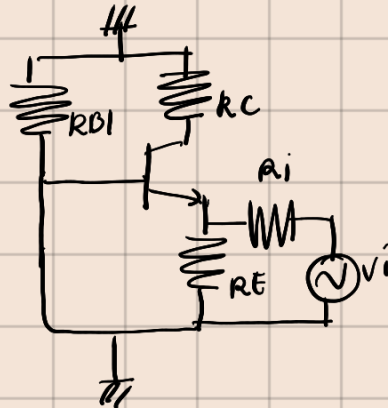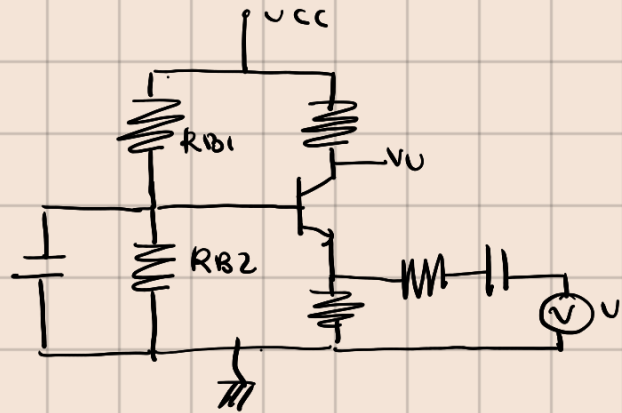

$$I_C^Q = 1 \text{ mA}$$

$$\beta_F = 150$$

$$V_{BE} = 0.7 \text{ V}$$

$$r_{bb'} = 100 \, \Omega$$

$$V_T = 26 \text{ mV}$$


$$g_o \rightarrow 0 \text{ S}$$

$$h_{fe} = 200$$

$$V_{DD} = 15 \text{ V}$$


$$g_m = 38.5 \text{ mS}$$
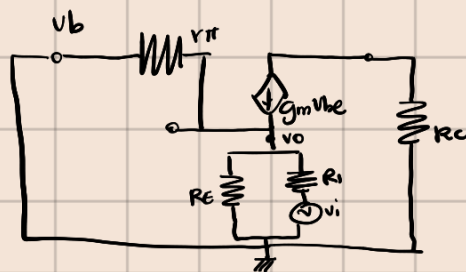
$$g_{\pi} = \frac{g_m}{\beta_0} = \frac{38.5 \text{ mS}}{200} = 192.5 \, \mu\text{S} = 5.19 \text{ k}\Omega$$



$$V_O = \frac{R_E V_b}{R_E + R_i}$$

$$\frac{V_b - V_O}{r_{\pi}} = i_b$$

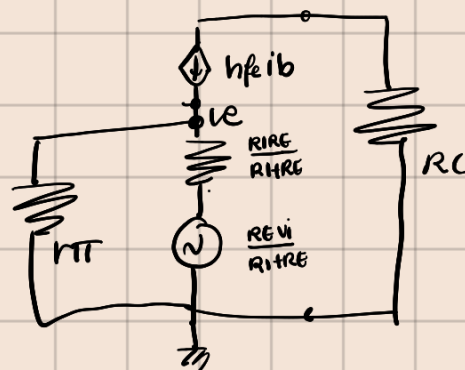

$$V_O = \frac{\frac{R_E V_i}{R_i + R_E} \cdot \frac{R_i + R_E}{R_i + R_E}}{\frac{1}{r_{\pi}} + \frac{R_i + R_E}{R_E}} = \frac{R_E r_{\pi} V_i}{r_{\pi} R_E + r_{\pi} R_i + R_i R_E}$$

$$\frac{V_O}{V_i} =$$