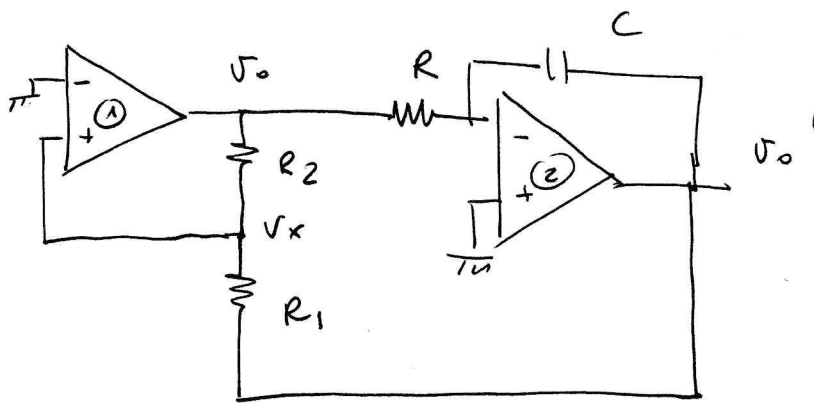


9/9/2020

Elettronica II

(1)

1)




$$v_x = v_o \beta + v_o' (1 - \beta)$$

→ segnale di scelta ① = 0V

$$v_x = v_o \beta + v_o' (1 - \beta) = 0 \Rightarrow v_o' = -v_o \frac{\beta}{(1 - \beta)}$$

$$\beta = \frac{R_1}{R_1 + R_2}, \quad 1 - \beta = \frac{R_2}{R_1 + R_2} \Rightarrow \frac{\beta}{1 - \beta} = \frac{R_1}{R_2}$$

$$v_o = \begin{cases} 12V = V_o \\ -12V = -V_o \end{cases} \Rightarrow |v_o'|_{\text{MAX}} = 6V \Leftrightarrow \boxed{\frac{R_1}{R_2} = \frac{1}{2}}$$

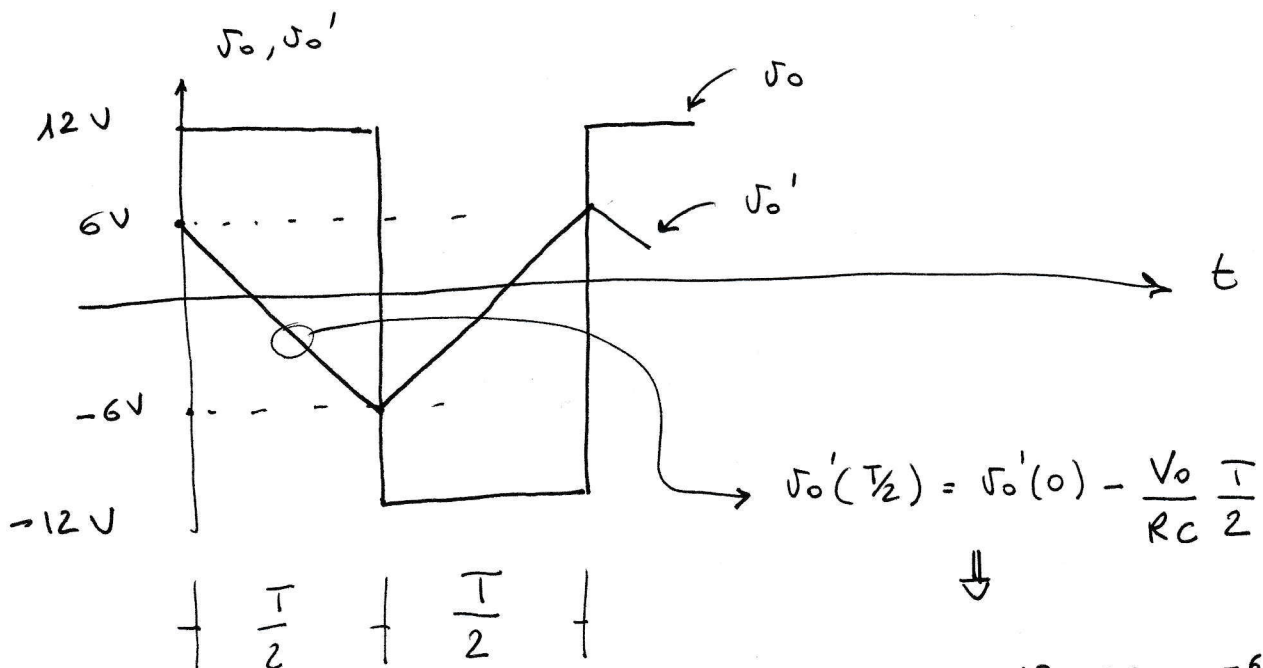

$$-6 = 6 + \frac{12}{RC} 50 \cdot 10^{-6}$$

$$\frac{12}{RC} \cdot 50 \cdot 10^{-6} = 12 \Rightarrow RC = 50 \cdot 10^{-6}$$

(2)

Possibile soluzione, tenendo conto che la max corrente erogata dall'AO (1) è

$$\begin{aligned} \frac{V_o - (-6V)}{R_1 + R_2} + \frac{V_o}{R} &= \frac{18V}{R_1 + R_2} + \frac{12V}{R} = \frac{18V}{3R_1} + \frac{12V}{R} = \\ &= \frac{6V}{R_1} + \frac{12V}{R} \end{aligned}$$


$$R_1 = 10 k\Omega$$

$$R_2 = 20 k\Omega$$

$$R = 10 k\Omega$$

$$C = \frac{50 \cdot 10^{-6}}{10 \cdot 10^3} = 5 nF$$

2)

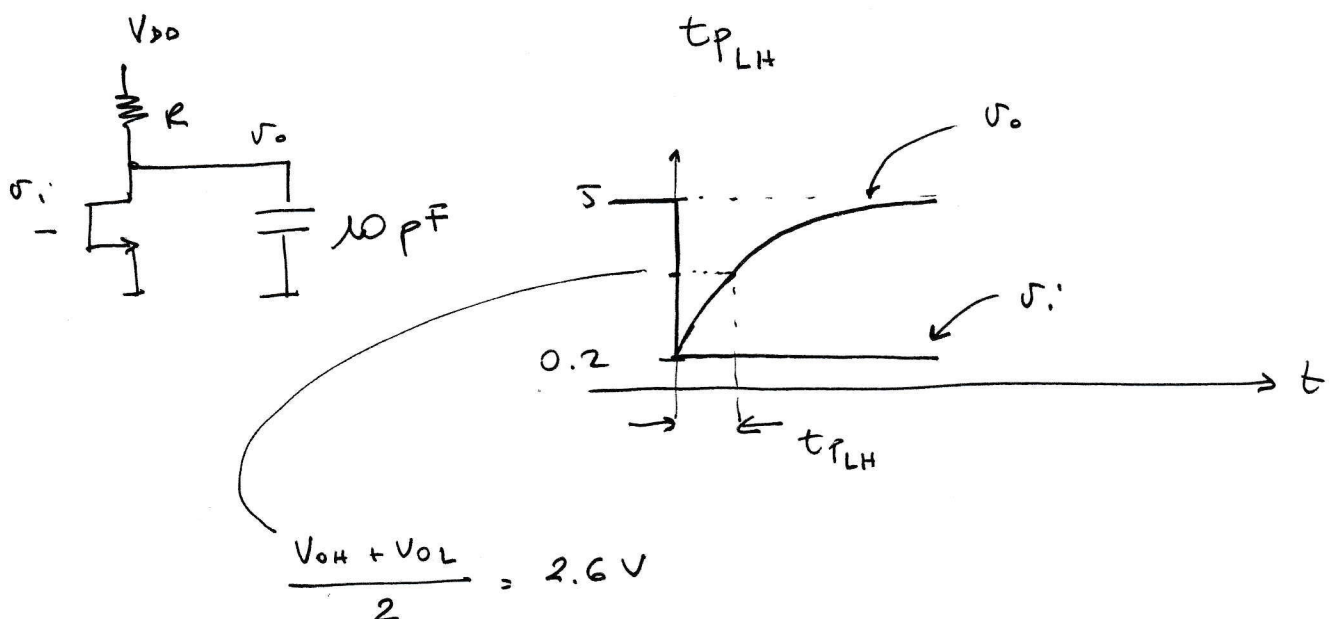

legge di carica del condensatore

$$v_o(t) = [v_o(\infty) - v_o(0)](1 - e^{-t/RC}) + v_o(0)$$

$$V_o(t_{PLH}) = 2.6 \text{ V} = \cancel{4.8} \text{ V} \cdot (1 - e^{-\frac{t_{PLH}}{RC}}) + 0.2 \text{ V}$$

③

$$(1 - e^{-\frac{t_{PLH}}{RC}}) = \frac{2.4}{\cancel{4.8}} = \frac{1}{2}$$

$$e^{-\frac{t_{PLH}}{RC}} = \frac{1}{2} \Rightarrow -\frac{t_{PLH}}{RC} = -\ln 2$$

$$\Rightarrow t_{PLH} = RC \ln 2$$

$$t_{PLH} = 10 \cdot 10^{-9} \text{ s} \Rightarrow RC = \frac{10 \cdot 10^{-9}}{\ln 2} =$$

$$\text{e, with } C = 10 \cdot 10^{-12} \text{ F} \Rightarrow R^* = \frac{\cancel{10} \cdot \cancel{10^{-9}}}{\ln 2 \cdot \cancel{10} \cdot 10^{-12/3}} = \frac{10^3}{\ln 2} = 1.442 \text{ k}\Omega$$


$$R < R^* \text{ guarantee } t_{PLH} < 10 \text{ ns}$$

3 Half Adder



A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\rightarrow S = A \oplus B = \bar{A} \cdot B + \bar{B} \cdot A$$

$$C = A \cdot B$$

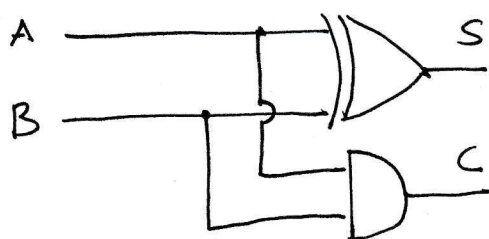


6

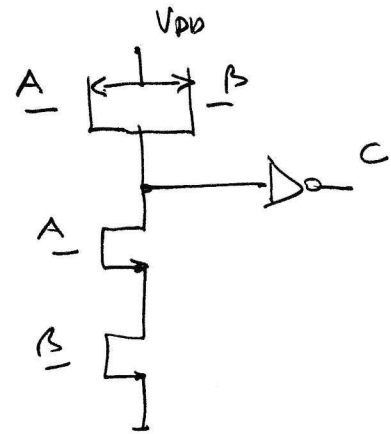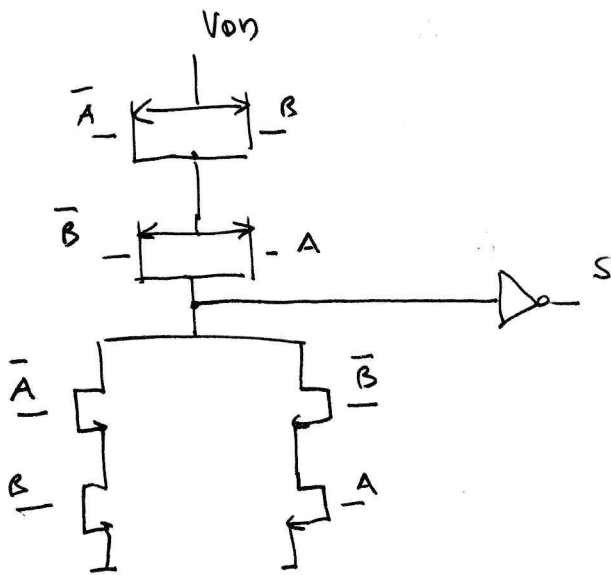


$$A \rightarrow \neg A$$

$$B \rightarrow \neg B$$

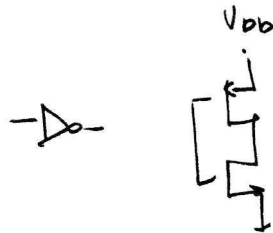

Opposite, megalis
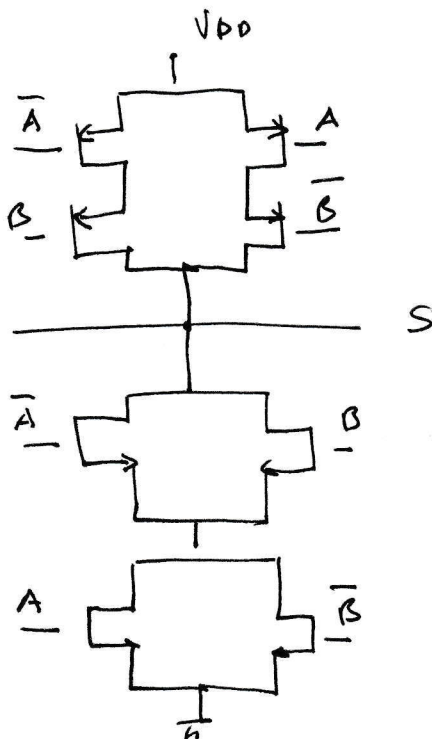
$$S = A\bar{B} + \bar{A}B = \overline{\bar{A} + B} + \overline{A + \bar{B}} = (\bar{A} + B) \cdot (A + \bar{B})$$



$$C = AB = \overline{\bar{A} + \bar{B}}$$

