
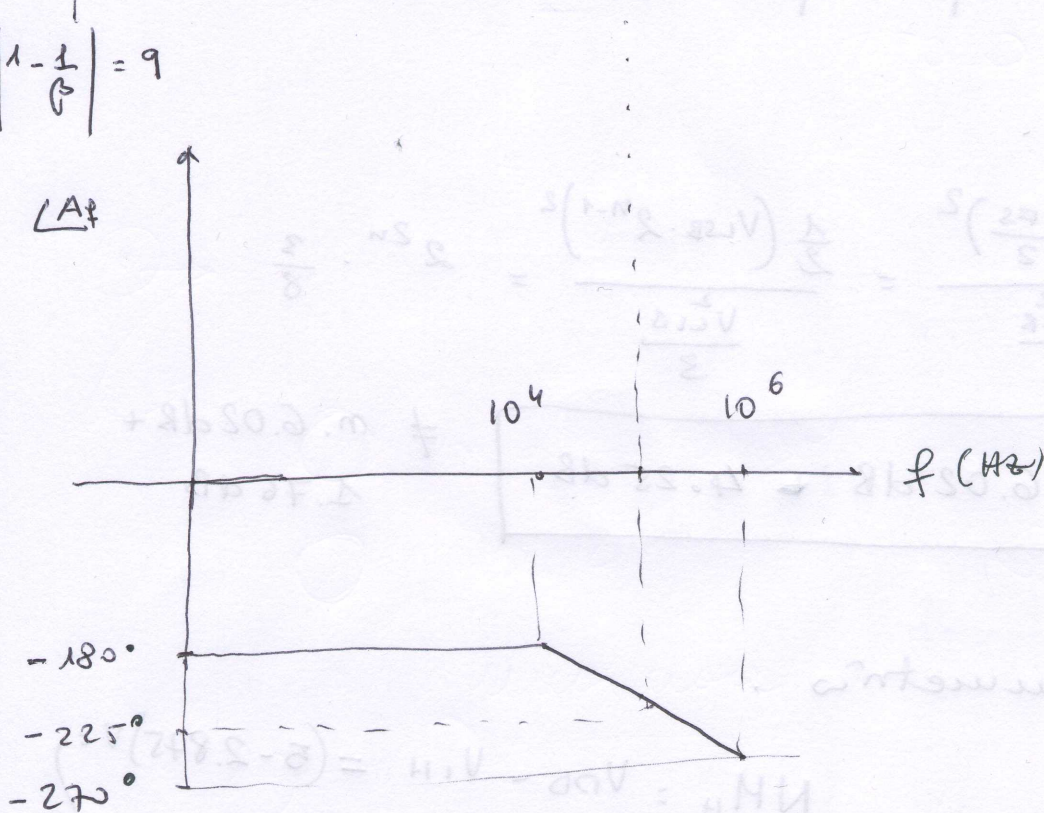
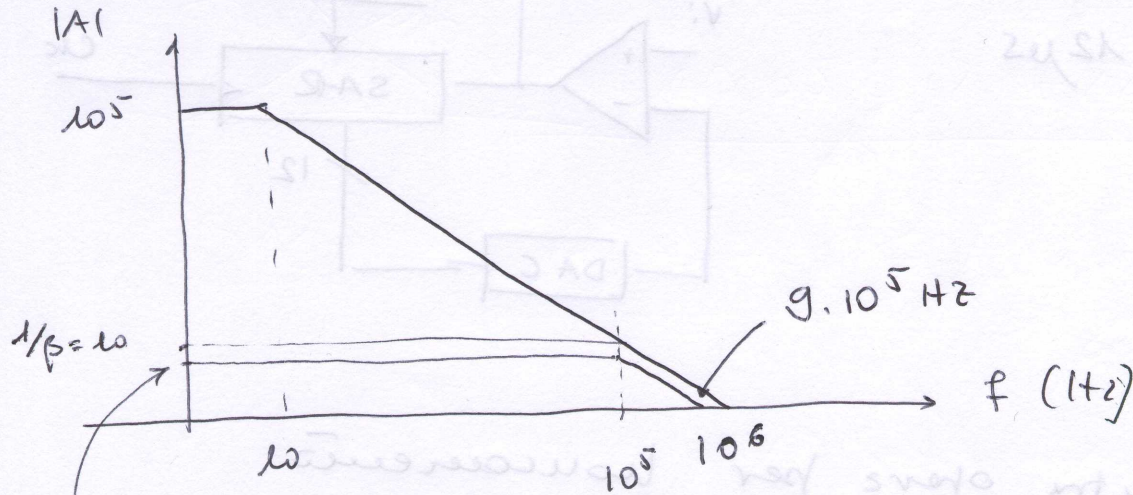


23/6/2020
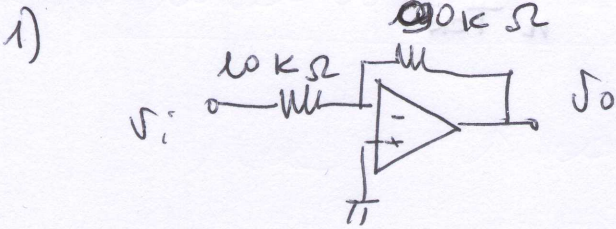
$$\beta = \frac{1}{10} \rightarrow \frac{1}{\beta} = 10$$




2) Tempo di conversione di un ADC di tipo SAR ed n bit e $n T_{ck}$

$$n = 12$$

$$T_{ck} = 1/f_{ck} = 10^{-6} s$$

$$T_{conv} = 12 \mu s$$

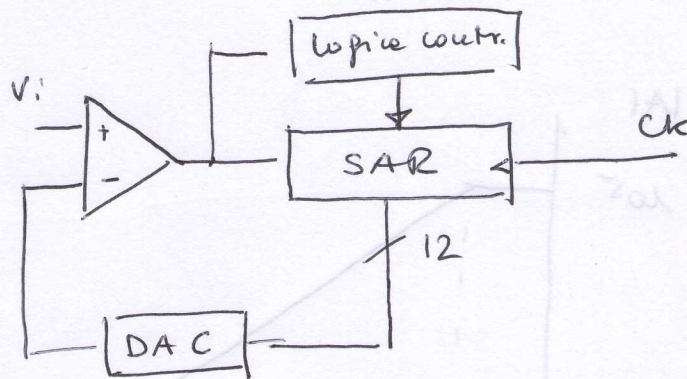

Il convertitore opera per confronto


$$\bar{e} = \frac{V_{LSB}^2}{3}$$

$$SNR_{max} = \frac{\frac{1}{2} \left(\frac{V_{FS}}{2} \right)^2}{\frac{V_{LSB}^2}{3}} = \frac{\frac{1}{2} (V_{LSB} \cdot 2^{n-1})^2}{\frac{V_{LSB}^2}{3}} = 2^{2n} \cdot \frac{3}{8}$$

$$SNR_{max} = m. 6.02 \text{ dB} + 4.25 \text{ dB}$$

$$\neq m. 6.02 \text{ dB} + 1.76 \text{ dB}$$

3) Inverter simmetrico

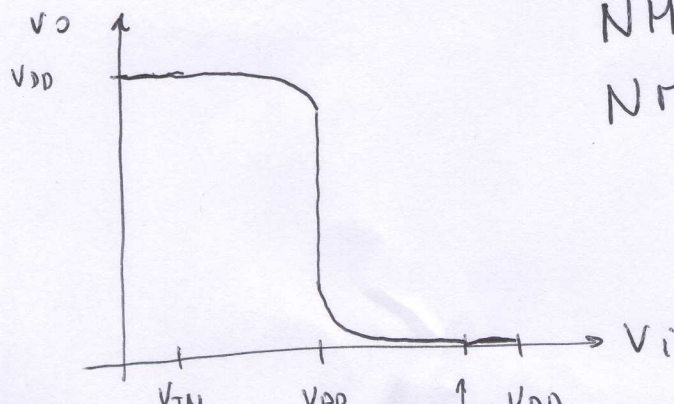

$$NM_H = V_{DD} - V_{IH} = (5 - 2.875) V =$$

$$NM_L = V_{IL} = NM_H$$

$$= 2.125 V$$

la corrente di picco I_P ha per
 $V_i = V_{DD}/2$, quando entrambi i MOS sono
in saturazione

$$I_P = K_n (V_{DD}/2 - V_{Th})^2 =$$

$$= 50 \cdot 10^{-6} \cdot (2.5 - 1)^2 \text{ A} =$$

$$= 112.5 \cdot 10^{-6} \text{ A} = 112.5 \mu\text{A}$$