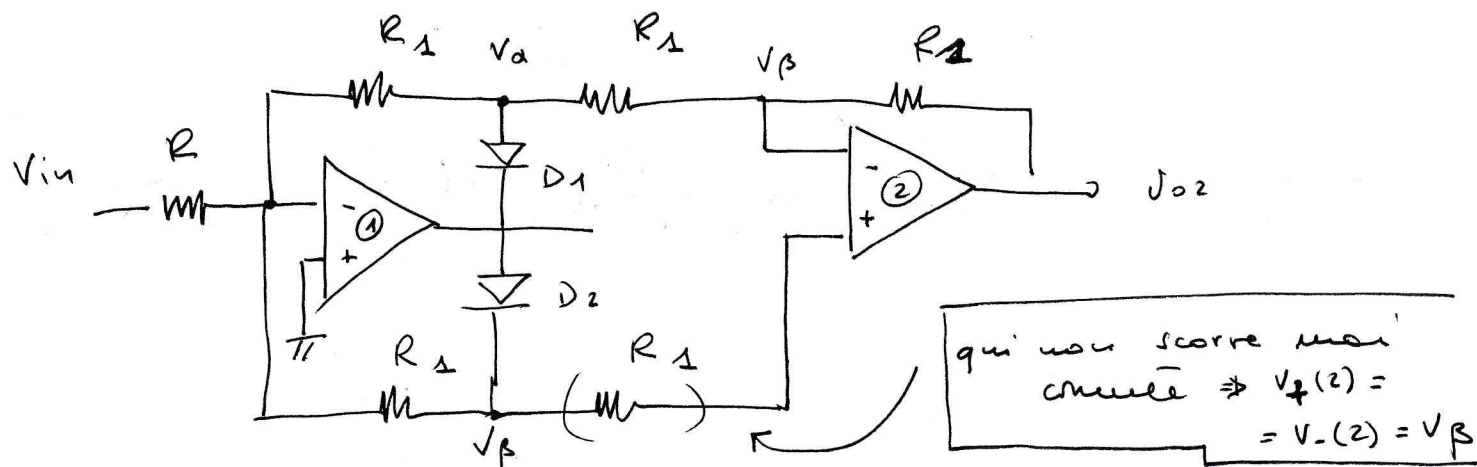


24/9/2020

ES-1



$$\underline{V_{in} > 0} \rightarrow V_{02} = -\frac{R_2}{R_1} V_{\alpha} = +\frac{R_2}{R} V_{in} \quad (D_1 \text{ ON})$$

↓
sul ramo
inferiore non
scorre corrente.

$$\underline{V_{in} < 0} \rightarrow D_2 \text{ ON}$$

$$\frac{V_{in}}{R} = -\frac{V_{\beta}}{2R_1} - \frac{V_{\beta}}{R_1}$$

$$\Rightarrow 3V_{\beta} = -\frac{2R_1}{R} V_{in} \Rightarrow V_{\beta} = -\frac{2}{3} \frac{R_1}{R} V_{in}$$

$$V_{02} = V_{\beta} \cdot \left(1 + \frac{R_1}{2R_1}\right) = \frac{3}{2} V_{\beta} = -\frac{R_1}{R} V_{in}$$

Per le specifiche $\frac{R_1}{R} = 2$

una soluzione possibile è $R_1 = 20 \text{ k}\Omega$
 $R = 10 \text{ k}\Omega$

(le cui vista dagli AO è dell'ordine di R_1)

```

graph LR
    SCT[SCT] --> SH[S&H]
    SH --> ADCFlash[ADC Flash 5bit]
    ADCFlash --> MSB[5 MSB]
    ADCFlash --> DAC5bit[DAC 5bit]
    DAC5bit --> Sum((+))
    SH --> Sum
    Sum --> Gain[x 2^5]
    Gain --> ADC5bit[ADC 5bit]
    ADC5bit --> LSB[5 LSB]


```

$$SNR_{MAX} = 6.02 n \uparrow + 1.76 \text{ dB} :$$

PS-3

$$Y = A + BCD + E$$

$$\rightarrow WC t_{P_{LH}} =$$

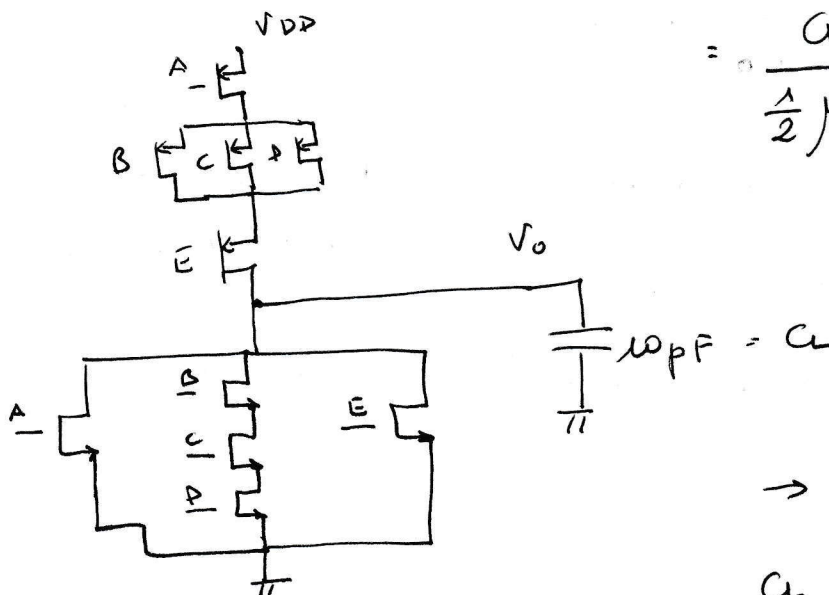

$$= \frac{C_L \frac{V_{DD}}{2}}{\frac{1}{2} \mu_P C_{ox} \cdot \frac{1}{3} (V_{DD} + V_{TP})^2}$$

$$\rightarrow WC + PH_2 =$$

$$\therefore \frac{C_L V_{DD}/2}{\frac{1}{2} \mu_n C_{ox} \frac{1}{3} (V_{DD} - V_{TN})^2} =$$

$$= \frac{C \cdot \frac{V_{DD}}{2}}{\frac{1}{2} \cdot 2 \mu_p C_{ox} \cdot \frac{1}{3} (V_{DD} - V_{th})^2}$$

essendo $V_{th} = -V_{TP}$, ed essendo $\mu_n = 2\mu_p$

$$t_{PLH_{wc}} = 2 t_{PHL_{wc}}$$

$$t_{PHL_{wc}} = \frac{10^{-11} \cdot 2.5}{25 \cdot 10^{-6} \cdot \frac{1}{3} \cdot 16} \text{ s} =$$

$$= \frac{3}{16} \cdot 10^{-6} \text{ s} = \frac{3}{16} \mu\text{s}$$

$$t_{p_{wc}} = \frac{t_{PLH_{wc}} + t_{PHL_{wc}}}{2} = \frac{1}{2} \left[\frac{3}{16} + \frac{6}{16} \right] \mu\text{s} =$$

$$= \frac{1}{2} \frac{9}{16} \mu\text{s} = \frac{9}{32} \mu\text{s} = 0.28125 \mu\text{s}$$