


ES. 1

a) $V_0 = 5V_1 - 9V_2$ con AO correttamente de

Guadagno asintotico

$$A_{OL} = \frac{10^5}{1 + jf/15}$$

$$I_{O_{MAX}} = 20 \text{ mA}$$

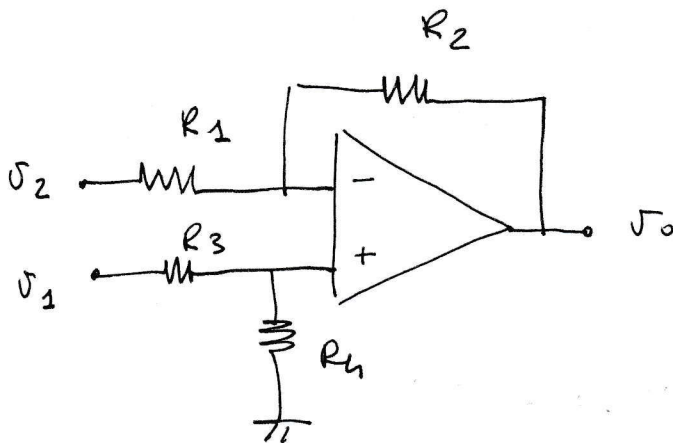

↳ con AO ideale $V_0 = V_1 \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) +$
 $- V_2 \frac{R_2}{R_1}$

$$\boxed{\frac{R_2}{R_1} = 9} \Rightarrow \frac{R_4}{R_3 + R_4} \cdot \left(1 + \frac{R_2}{R_1} \right) = \frac{R_4}{R_3 + R_4} \cdot 10 = 5$$

$\frac{R_2}{R_1} = 9$

$$\Rightarrow \frac{R_4}{R_3 + R_4} = \frac{1}{2} \Rightarrow \boxed{R_3 = R_4}$$

Soluzioni possibili $R_3 = R_4 = R_1 = 1 \text{ k}\Omega$

$$R_2 = 9 \text{ k}\Omega$$

b) la larghezza di banda dipende dal fattore β (2)

$$v_o = \left[\left(1 - \frac{1}{\beta}\right) v_2 + \frac{v_1}{2} \cdot \frac{1}{\beta} \right] \frac{\beta A_o}{1 + \beta A_o} \cdot \frac{1}{1 + j \frac{f}{f_H(1 + \beta A_o)}}$$


con $\beta = \frac{R_1}{R_1 + R_2} = 10^{-1}$

$A_o = 10^5$

$\rightarrow f_{Hf} = f_H (1 + \beta A_o)$

$\approx 15 \cdot 10^4 \text{ Hz}$

ES. 2

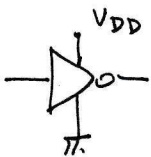


$V_{DD} = 5V$

$NM_H = 3V \quad NM_L = 1.25V$

$V_{SL} = 1.625V$

$V_{TN} = -V_{TP} = 1V$

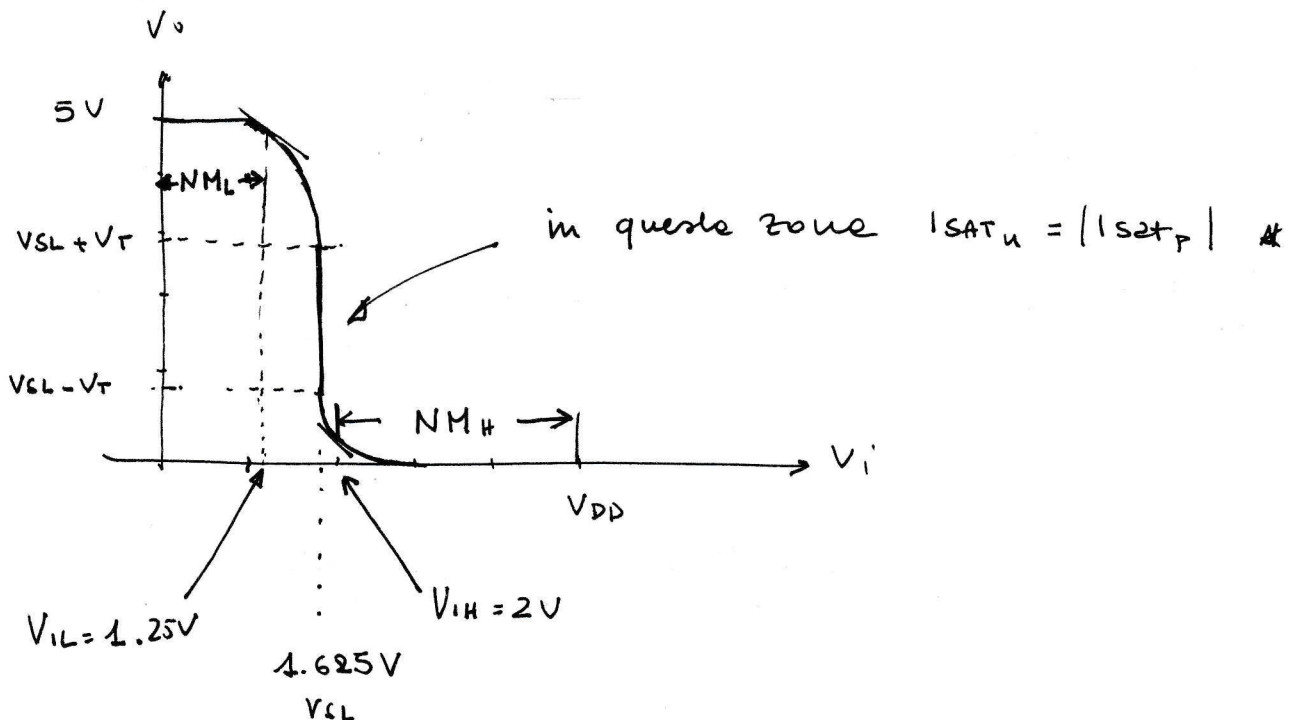

* $K_n (V_{SL} - V_T)^2 = K_p (V_{DD} - V_{SL} - V_T)^2$

$K_n (0.625)^2 = K_p (2.375)^2 \Rightarrow \frac{K_n}{K_p} = \frac{(2.375)^2}{(0.625)^2} = 14.44$

Quindi l'inverter, come risulta chiaro dai dati del problema, è fortemente dissimetrico.

(3)

b) ricordando che

$$t_{PHL} = \frac{C_L V_{DD}/2}{K_n (V_{DD} - V_T)^2}, \quad t_{PLH} = \frac{C_L V_{DD}/2}{K_p (V_{DD} - V_T)^2}$$

$$K_n t_{PHL} = K_p t_{PLH} \Rightarrow t_{PLH} = \frac{K_n}{K_p} t_{PHL} = 14.44 t_{PHL}$$